

Total number of printed pages-5

53 (EC-401) DGEL

2015

DIGITAL ELECTRONICS

Paper : EC 401

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) Why are NAND and NOR gates called universal gates? 2
- (b) What are the basic operations in Boolean algebra? 2
- (c) Why is a demultiplexer called a distributor? 2
- (d) How does a J-K flip flop differ from an S-R flip flop in its operation? 2
- (e) What do you mean by an invalid (illegal) state? Give examples. 3

Contd.

- (f) What do you mean by toggling? 2
- (g) What are PRESET and CLEAR inputs? 3
- (h) Write the procedure to simplify the Boolean expressions using K-maps. 4
2. (a) Implement a full-adder using two 4 : 1 multiplexer. 5
- (b) Implement the following expression using a single 8 : 1 multiplexer
 $Y(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 9, 12, 14)$ 5
- (c) Draw the simplest possible logic diagram that implements the output of the logic diagrams shown below : 5+5=10

 


Fig 1(c)

 


Fig. 2(c)

3. (a) What is a comparator? Design a 2-bit. comparator using logic gates.

2+8=10

- (b) Minimize the following Boolean functions and implement it using basic gates only.

10

(i) $Y(A,B,C,D) = \sum m(1, 3, 5, 8, 9, 11, 15) + d(2, 13)$

(ii) $f(P, Q, R, S) = \sum m(2, 3, 5, 13, 14) + d(8, 9, 10, 11)$

4. (a) Draw a neat circuit diagram of clocked J-K flip-flop using NAND gates. Give its truth table and explain race around condition.

10

(b) Explain how a J-K flip-flop is converted into S-R flip-flop and T flip-flop. 10

5. (a) Find the outputs of the given logic circuit. 6

 


Fig. 5(a) logic circuit

(b) Design and implement a Mod-5 synchronous counter using J-K flip-flop. 8

(c) Design a circuit to generate the sequence $0 \rightarrow 2 \rightarrow 5 \rightarrow 4 \rightarrow 7 \rightarrow 3$. 6

6. (a) Draw the Block diagram of PLA and implement a full adder circuit using PLA having three inputs eight product terms and two outputs. 10

(b) Design a 3 bits Binary to Gray code converter using a suitable PLA. 10

7. (a) Make the excitation tables of J-K, S-R and T flip-flops. 6
- (b) Explain the functional diagram of a $2K \times 8$ memory chip. 6
- (c) Define the following parameters of logic families $2 \times 4 = 8$
- (i) Propagation delay
 - (ii) Fanout
 - (iii) Noise margin
 - (iv) Figure of merit.