

Total number of printed pages-4

53 (EC 602) VLDG

2015

VLSI

Paper : EC 602

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.


Answer **any five** questions.

1. (a) What do you mean by Channel length modulation? Describe and derive the expression for output conductance 'g_{ds}' parameter. Draw the Small-Signal model of an n-MOS including Channel length-model. 5
- (b) Write a short note on Metallization process. 5
- (c) Implement the following function in CMOS and draw the corresponding layout. 10
$$f = \overline{A \cdot B + C \cdot D}$$

Contd.

2. (a) Discuss the operation of CMOS SRAM cell for reading, writing and holding data. 10
- (b) Write a short-note on Bi-CMOS-technology. 5
- (c) Write the masking steps required for an n -well CMOS technology. 5
3. (a) Derive the expression for threshold voltage of a n -MOSFET. 5
- (b) Discuss the operation of Bi-COMS inverter using proper circuit diagram. 10
- (c) Derive an expression for rise time for an CMOS inverter. 5
4. (a) What do you mean by a data path element? Draw the Architecture for Array multiplier for 4 bit word multiplication. 10
- (b) Write down the design-rules for an Active area containing poly layers (λ -based). 5
- (c) Write a short note on probe testing. 5

 5. (a) Why scaling is important in IC-design? Mention the types of scaling and discuss each parameter due to scaling. 10
- (b) Draw a typical structure of an FPGA and discuss the Xilinx SRAM based FPGA. 10
6. (a) Write down VHDL code for an 4 : 1 MUX using 2 : 1 Muxes using structural model. 10
- (b) Calculate Elmore's Delay of the following RC-network shown at nodes 'A' & B, C & 'D'. 10



7. (a) Implement the following function in CMOS logic & draw layout for that $f = \overline{A + B \cdot C}$. 10

- (b) Write a short note on capacitors in CMOS. 5
- (c) Show the internal parasitic capacitances in an n-MOS Transistor using cross-sectional view. 5
-