

Total number of printed pages-8

53 (IE 301) Nwth

2016

NETWORK THEORY

Paper : IE 301


Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.


Answer **any five** questions.

1. (a) Convert the following current source circuit to a single voltage circuit. 6

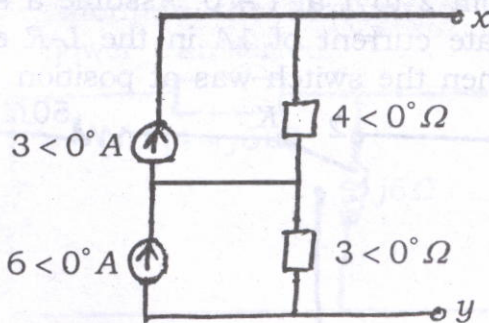


Contd. 88

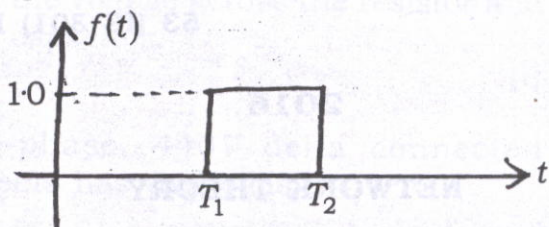
- (b) Obtain the Laplace transform of the pulse shown in following fig. 6



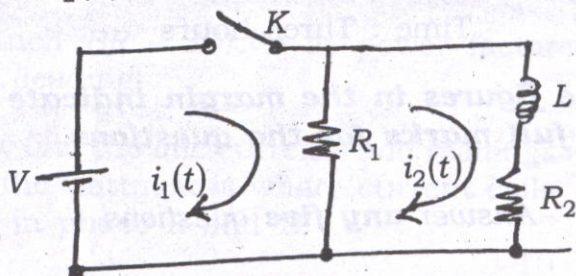- (c) A two mesh network is shown below. Obtain the expression for $I_1(S)$ and $I_2(S)$ when the switch is closed. 8




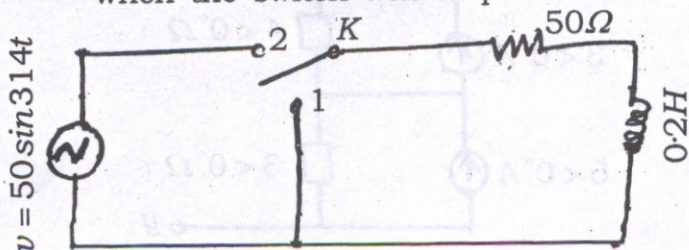2. (a) Obtain the current at $t > 0$; if a.c. voltage ' v ' is applied when switch ' K ' is moved from 2 to 1 at $t = 0$. Assume a steady state current of 1A in the L - R circuit when the switch was at position 1. 7




- (b) Calculate the time taken by a capacitor of $2\mu F$ and in series with $2M\Omega$ resistance to be charged upto 60% of its final value. 5

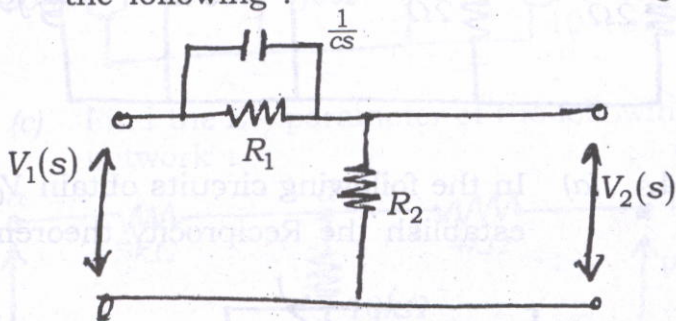- (c) Obtain the Transfer Function $\frac{V_2(s)}{V_1(s)}$ in the following : 8




3. (a) A function is given by $Z(s) = \left(\frac{3s}{s^2 + 16} \right)$. Draw its pole-zero plot. 6


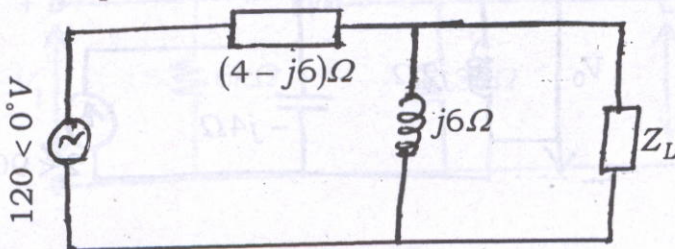
- (b) Find the load impedance for maximum power transferred to the load. Also calculate the amount of maximum power transferred. 7



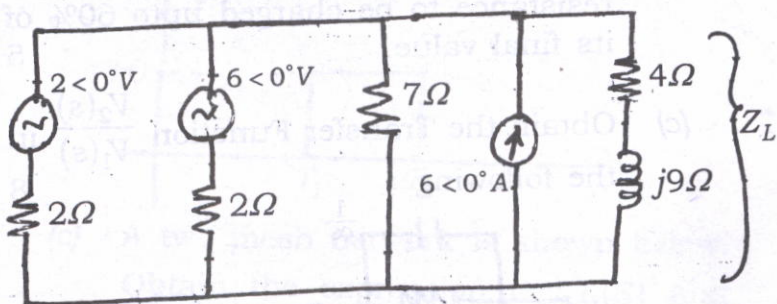
- (c) Using Millman's Theorem, find the current through Z_L . 7



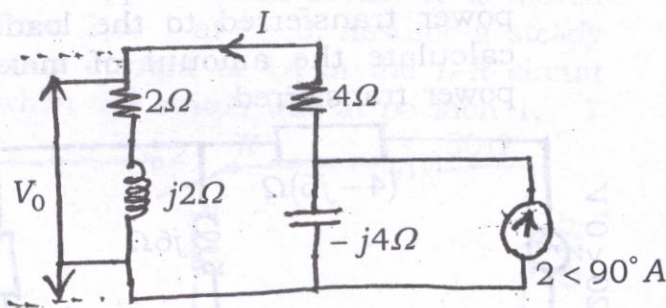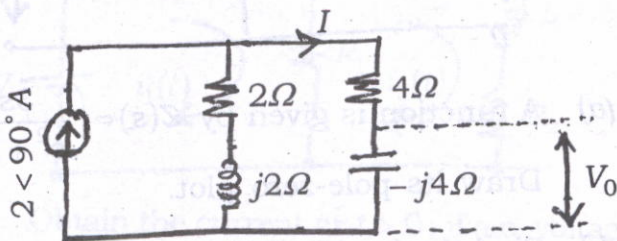
4. (a) In the following circuits obtain V_0 and establish the Reciprocity theorem. 8



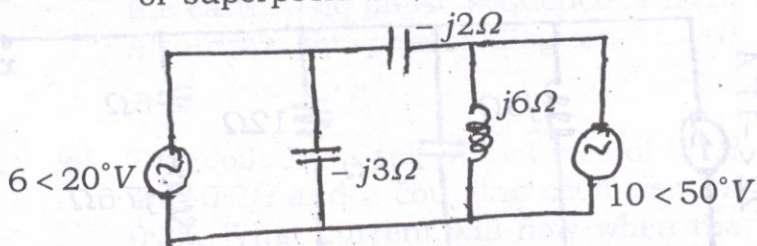
- (b) Find the current through $j5\Omega$ inductive reactance using the principle of superposition. 6



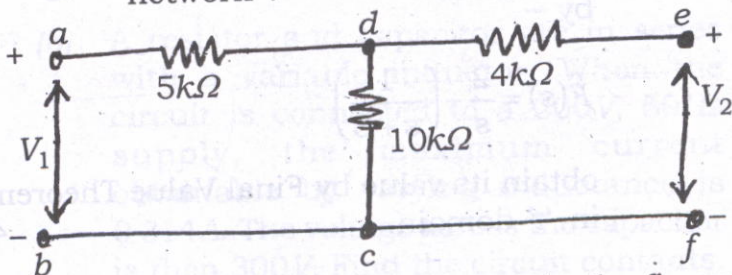
- (c) Find the Z-parameter of the following network : 6



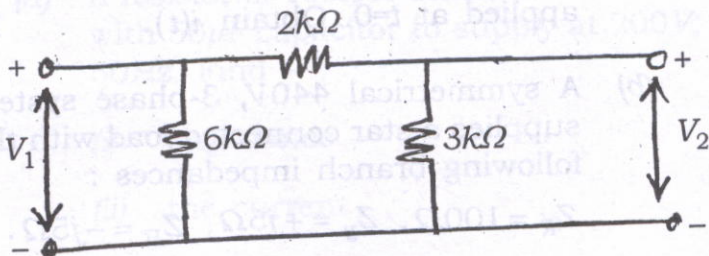5. (a) A π -attenuator is shown in the figure. Find the Y-parameters and draw equivalent Y-parameter circuit. 8



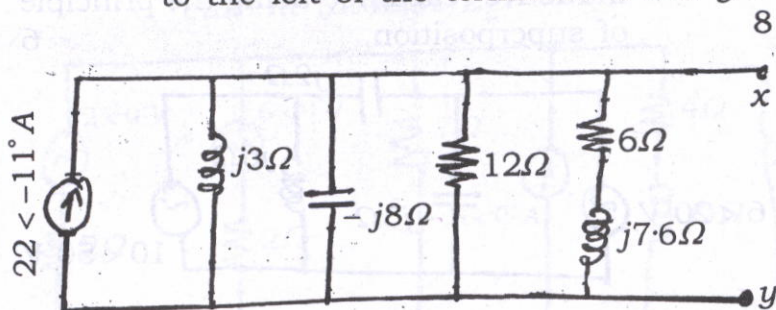- (b) Find the Thevenin's equivalent circuit to the left of the terminals x and y :



- (c) A function in Laplace domain is given by -

$$F(s) = \frac{2}{s} - \left(\frac{1}{s+3} \right)$$

obtain its value by Final Value Theorem in t domain. 4

6. (a) In a series RLC circuit $R = 6\Omega$, $L = 2H$ and $C = 3F$. A dc voltage of $30V$ is applied at $t=0$. Obtain $i(t)$. 10

- (b) A symmetrical $440V$, 3-phase system supplies a star connected load with the following branch impedances :

$$Z_R = 100\Omega, \quad Z_Y = +j5\Omega, \quad Z_B = -j5\Omega.$$

Calculate the voltage drop across each branch and potential of the neutral to the earth. The phase sequence is *RYB*. Also draw the phasor diagram. 10

7. (a) Two coils have self inductance of $0.1H$ and $0.2H$ and a coupling coefficient of 0.35 . What current will flow when the coils are joined in series across a $125V$, $50Hz$ circuit? 10

(b) A resistor and capacitor are in series with a variable inductor. When the circuit is connected to a $200V$, $50Hz$ supply, the maximum current obtainable by varying inductance is $0.314A$. The voltage across the capacitor is then $300V$. Find the circuit constants. 10

8. (a) A resistor of 100Ω is connected in series with $50\mu F$ capacitor to supply at $200V$, $50Hz$. Find -

(i) impedance

(ii) the current

(iii) the power factor

(iv) the phase angle, and

(v) the voltage across the resistor and capacitor.

10

(b) A 3-phase, 440V delta connected systems has the loads :

Branch *RY* - 20kW at power factor 1

Branch *YB* - 30kVA at power factor 0.8 (lagging)

Branch *BR* - 20kVA at power factor 0.6. (leading)

Now find the line currents and readings on the wattmeters where current coils are in phase *R* and *B*.

10