

Total number of printed pages-4

53 (EC 602) VLSI

2016

VLSI

Paper : EC 602

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions out of **seven**.


1. (a) Implement the following Boolean function in CMOS :

$$f(A,B,C,D) = \overline{(A \cdot B + C \cdot D)}$$

and draw its complete layout. 2+8

Contd.

 - (b) Calculate the Elmore's delay for the RC tree below,



at nodes : a, b, c, d

$$2\frac{1}{2} + 2\frac{1}{2} + 2\frac{1}{2} + 2\frac{1}{2}$$

2. (a) Write a short note on Ion-implantation of diffusion process. 4+3
- (b) Consider an N-MOS transfer having aspect ratio $\left(\frac{8\mu\text{m}}{0.5\mu\text{m}}\right)$ is made in a process having $\mu_n C'_{ox} = 180 \mu\text{A}/\text{V}^2$, $V_{TH} = 0.7\text{V}$ and calculate the on resistance of MOSFET ; if $V_{DD} = 3\text{V}$, gate is connected to a battery of 4V and source is at ground. 3

(c) Describe the blocks of a 4-bit MPU and its function with neat diagrams. 10

3. (a) Consider a CMOS process having following parameters :

$$\mu_n C'_{ox} = 150 \mu A/V^2, \quad V_{TH,n} = 0.8V$$

$$\mu_p C'_{ox} = 70 \mu A/V^2, \quad V_{TH,p} = -0.8V$$

Calculate the switching threshold for an inverter designed in the CMOS process : where aspect ratio of N-MOS

and P-MOS are $\left(\frac{20 \mu m}{1 \mu m}\right)$ and $\left(\frac{10 \mu m}{1 \mu m}\right)$ respectively and the supply voltage used is +3V. 4

(b) Prove that the transition frequency of a N-MOS transistor in saturation is directly proportional to transconductance and inversely proportional to gate capacitance. 6

(c) Draw the circuit diagram of an inverter in various different integration technologies and describe the fabrication process steps for an N-MOS technology. 3+7

4. (a) Implement an SR-latch (using NAND gate) in CMOS logic and draw the layout for the same circuit. 4+6

- (b) Describe the importance of Noise Margin while cascading inverters. 5
- (c) Draw the layout of the 2 input XNOR gate. 5
5. (a) Describe the rotation operation for a 4bit binary word 'B' ($b_3 b_2 b_1 b_0$) used for 4bit ALU and hence draw the N-MOS switch matrix for 4 bit rotate right operation. 2+6
- (b) Describe the ROM operation and draw the implementation of ROM array. 2+6
- (c) Mention the effect of constant field scaling on these parameters : Intrinsic delay, on-resistance, Acceptor impurity concentration, area. 4
6. (a) Describe the operation of DRAM cell (1 bit) with proper circuit diagram and compare the features of SRAM and DRAM. 6+4
- (b) Write VHDL code for a full-Adder using 2-Half Adders in a structural model. 10
7. (a) Describe the 4 bit multiplication for an 4 bit ALU and implement an array based multiplier for this. 10
- (b) Describe the operation of Bi-CMOS inverter with circuit diagram. 10