

Total No. of printed pages = 3

**Et-304/EEtE/3rd Sem/Electrical/2017/M**

**ELEMENTS OF ELECTRONICS  
ENGINEERING**

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks  
for the questions.

Answer any *five* questions.

1. (a) What is electron emission ? What are the different types of electron emission ? 2+3=5
- (b) What are the active and passive components in electronic circuits ? 4
- (c) A resistor has a colour band sequence : Red, Black, Green and Silver. Find the range in which its value must be depending upon the manufacturer's tolerance to suit a circuit. 5
2. (a) Describe the construction and working of a vacuum diode. 7

[Turn over

- (b) What are the different vacuum tube constants ?  
Define them and also derive a relationship between them. 7
3. (a) What is a semiconductor ? What are intrinsic and extrinsic semiconductors ? 2+4=6
- (b) Draw the V-I characteristic of a semiconductor diode and explain it. 4
- (c) Why is zener diode used as a voltage regulator ? 4
4. (a) Explain the input and output characteristic of a transistor in CB configuration. 6
- (b) Define  $\alpha$  and  $\beta$  for a transistor. 4
- (c) Derive the relationship between  $\alpha$  and  $\beta$ . 4
5. (a) Explain the following terms : 2×2=4
- (i) Peak inverse voltage
- (ii) Ripple factor.
- (b) Why feter circuits are used at the rectifier output ? 2
- (c) Describe with circuit diagram, the operation of a full wave bridge rectifier. 8



6. (a) Classify amplifiers. 6

(b) With a neat diagram, explain the working of push-pull amplifier. 8

7. Write short notes on any *two* of the following :  
7×2=14

(i) Zener diode

(ii) Cathode ray tube

(iii) Formation of P-N Junction

(iv) Hartley oscillator.