

2017

NETWORK THEORY

Paper : IE 301

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) What are active and passive elements ?
A series circuit with $R = 2\Omega$, $L = 2mH$, $C = 500\mu F$ has a current which increases linearly from zero to 10A in the interval $0 \leq t \leq 1ms$, remains at 10A for $1ms \leq t \leq 2ms$ and decreases linearly from 10A at $t = 2ms$ to zero at $t = 3ms$. Sketch V_R , V_L and V_C . 2+7=9

Contd.


(b) The coefficient of coupling between two coils is 0.75. There are 250 turns in coil 1. The total flux linking coil 1 is 0.4 mWb , when the current in this coil is 3A. When i_1 is changed from 3A to zero linearly in 3 milliseconds, the voltage induced in coil 2 is 70V. Calculate L_1, L_2, M, N_2 . 5

(c) What are the advantages of three phase systems ? 4

(d) Three impedances each having a resistance of 20Ω and an inductive reactance of 15Ω are star connected across a 400V, three phase supply. Calculate 6


- (i) The line current
- (ii) The power factor
- (iii) The total power in kW.

(b)

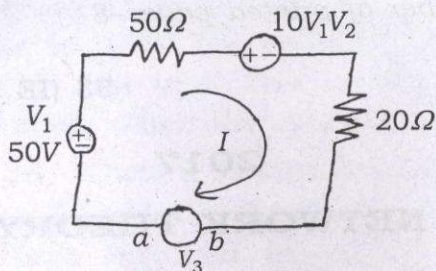


find V_3 and its polarity if the current I in the circuit is 0.40A . 4

(c)

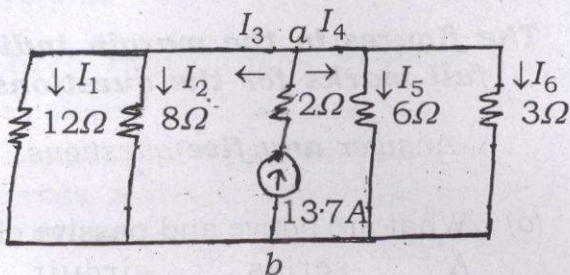

Find all branch currents in the network. 7

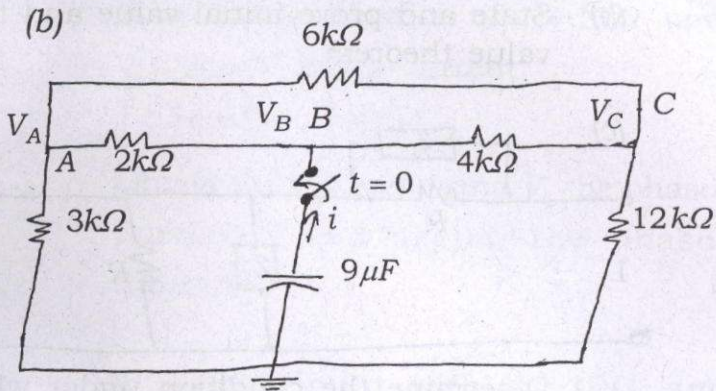2. (a) A $4\mu\text{F}$ capacitor with an initial voltage of $V(O^-) = 2\text{V}$ is connected to a 12V battery through a resistor $R = 5\text{k}\Omega$ at $t = 0$. Find the voltage across and current through the capacitor for $t > 0$. 5



The 9 μF capacitor is connected to the circuit at $t=0$. At this time capacitor voltage is $V_0 = 17\text{V}$. Find $V_A, V_B, V_C, i_{AB}, i_{AC}, i_{BC}$ for $t > 0$.

12


(c) Obtain the current $i(t)$ in RL circuit for unit impulse input.

3


3. (a) A series RLC circuit with $R = 200\Omega$, $L = 0.1\text{H}$ and $C = 13.33\mu\text{F}$, has an initial charge on the capacitor of $Q_0 = 2.67 \times 10^{-3}\text{C}$. A switch is closed at $t=0$, allowing the capacitor to discharge. Obtain the current transient.

6

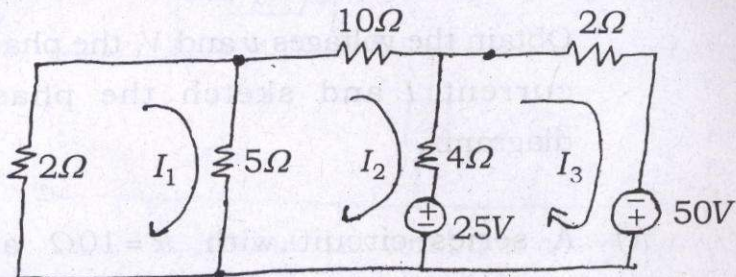
- (c) Write the mesh current matrix equation for the network by inspection and solve for the currents. 5



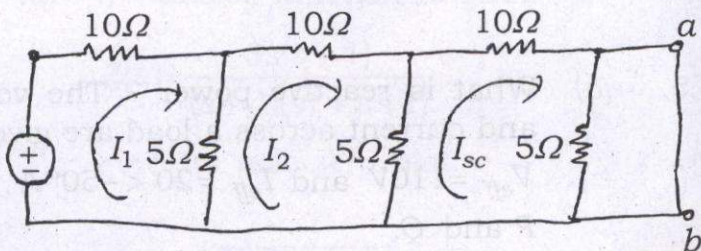
- (d) Obtain the Thevenin's equivalent for the circuit to the left of terminal ab . 5



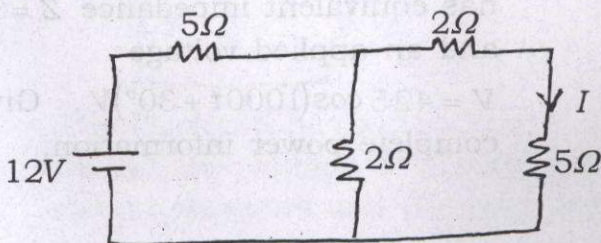6. (a) Determine the current I in the circuit by using the Norton's theorem 5



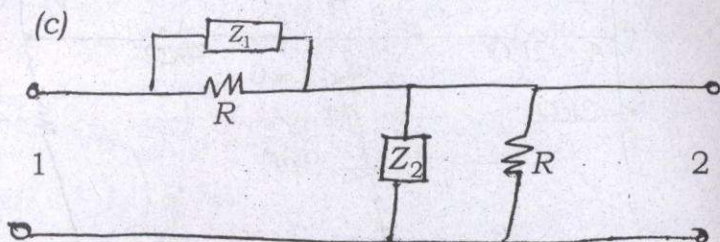- (b) State and prove initial value and final value theorem. 6




Determine the condition under which the driving point impedance at port 1 of the network is R . 4

- (d) A transfer function is given as,

$$Z(s) = \frac{3s(s+4)}{(s+2)(s^2+s+1)}$$

Find its pole-zero plot. 4

4. (a)

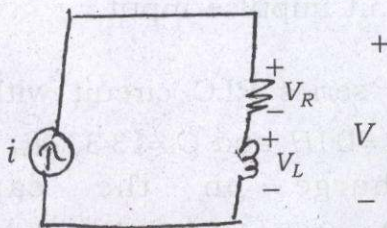

The RL circuit has a current $i = I \sin \omega t$ obtain the voltage V across the two circuit elements and sketch V and i .

8

- (b) A series combination of $R = 10\Omega$ and $L = 20mH$ has a current $i = 5\cos(500t + 10^\circ)A$.


Obtain the voltages v and V_1 , the phasor current I and sketch the phasor diagram. 8

- (c) A series circuit with $R = 10\Omega$ and $L = 20mH$, has a current $i = 2\sin 500t$. Obtain total voltage V and the angle by which i lags V . 4

5. (a) What is reactive power? The voltage and current across a load are given by $V_{eff} = 110V$ and $I_{eff} = 20 \angle -50^\circ A$. Find P and Q . 5


- (b) A certain passive network has equivalent impedance $Z = 3 + j4\Omega$ and an applied voltage $V = 42.5\cos(1000t + 30^\circ)V$. Give complete power information. 5

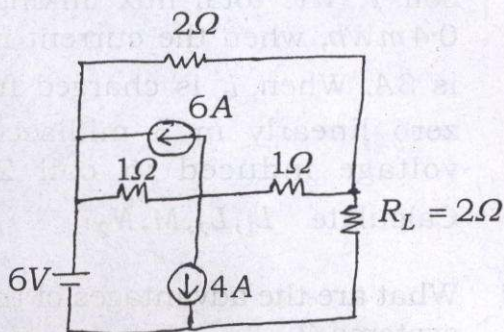- (b) State and explain the compensation theorem and Tellegen's theorem. 10
- (c)



Determine the current through R_L in the circuit using super position theorem. 5

7. (a) What is mutual inductance? 5

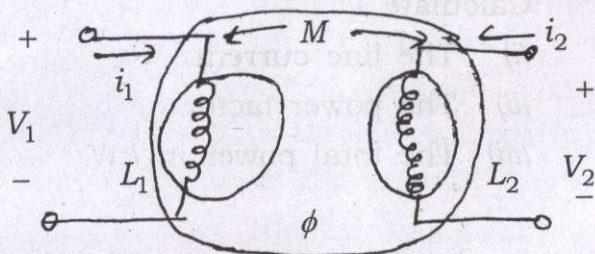

In the circuit $L_1 = 0.1H$ $L_2 = 0.5H$ and $i_1(t) = i_2(t) = \sin \omega t$. Find $V_1(t)$ and $V_2(t)$ for (a) $M = 0.01H$ (b) $M = 0.2H$ (iii) $M = -0.2H$.