

Total number of printed pages-4

53 (EC 602) VLSI

2017

VLSI

Paper : EC 602

Full Marks : 100

Time : Three hours


The figures in the margin indicate full marks for the questions.

Answer **any five** questions out of **Seven**.

- (a) Implement the Boolean function $f(A,B,C,D) = \overline{A \cdot (B + C + D)}$ using CMOS logic ϕ draw the schematics. 4
- (b) What do you mean by noise margin for an inverter ? Explain the importance of noise margin in an inverter. How can we maximise the noise margin for an inverter ? 1+2+2


Contd.

 - (c) Draw the diagram of inverters in various integration technologies, describe the operation of CMOS and BiCMOS inverters. 1+10
2. (a) Calculate the maximum speed of an NMOS technology. 5
- (b) Draw the layout for 2 input XOR gate and 2 input XNOR gate with necessary label for the layers. 10
- (c) Explain the operation of a Binary Comparator with proper logic diagram. 5
3. (a) Explain the operation of 1 bit DRAM cell, and compare the performance with 1bit SRAM cell. 6+4
- (b) Describe the lithographic sequences required to pattern the oxide as shown below : 5



- (c) Draw the NMOS cross-bar switch matrix for implementing 4-bit right rotation operation. 5


 
4. (a) Calculate the expressions for elmore's delay for the following RC-tree at 'A', 'B', 'C', 'D' nodes. 10



- (b) Describe the effect of constant voltage scaling on the various parameters for digital systems. 5

- (c) Write a short note on the Ion implantation process. 5

5. (a)

  

- (i) Calculate the drain-to-source current for the biased NMOS transistor implemented in a technology having

$$\mu_n C_{ox} = 100 \mu A/v^2 \text{ and } V_{THn} = +1V$$

and $V_A = +40V$ fig (a).

- (ii) Find the operating modes of NMOS and PMOS of an inverter if $V_{in} = 0.5V$ and V_{out} is $4.5V$.

2+2

- (b) Explain the operation of 4bit binary no. multiplication and draw the architecture for 4×4 multiplier array.

2+9

- (c) Calculate the rise time for an inverter (CMOS).

5

6. (a) Draw the CMOS schematic of a full-Adder.

6

- (b) Describe the fabrication process steps for Bi-polar technology and draw the corresponding layout.

8+2

- (c) Explain the logical implementation of Zero/one detector and its operation.

4

7. (a) Write a short note on oxidation process.

6

- (b) Explain the operation and architecture of NOR based ROM.

8

- (c) Describe the internal parasitics of a MOS transistor and draw the high frequency modes of an NMOS transistor in saturation mode.

4+2