

Total No. of printed pages = 5

Et-304/EEtE/3rd Sem/2017/N

**ELEMENTS OF ELECTRONICS
ENGINEERING**

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer Q. No. 1 and any *three* from the rest.

1. Fill in the blanks : 1×25=25

(a) A signal that varies continuously is known as
_____ signal.

(b) Resistance, capacitance and inductance is
known as _____ component.

(c) An electronic component that can modify a
signal is known as _____ component.

(d) A vacuum tube extract electrons from cathode
by _____ emission.

[Turn over

- (e) A pentode has _____ electrodes.
- (f) In resistance colour code, the fourth band indicates _____.
- (g) Silicon is a _____.
- (h) Germanium is a _____ valent material.
- (i) A pure semiconductor is also known as _____ semiconductor.
- (j) The process of adding impurity in pure semiconductor to make it an extrinsic semiconductor is known as _____.
- (k) To make N-type semiconductor, _____ valent impurity is added to pure semiconductor.
- (l) Free electrons are present in _____ band.
- (m) The conductivity of a material can be explained by _____ band diagram.
- (n) A junction _____ can be constructed by using P and N type semiconductor.
- (o) A _____ has three terminals viz. base, emitter and collector.

- (p) A PN junction diode can be used as a _____.
- (q) A zener diode is used in _____ biased condition.
- (r) A _____ can be used as an amplifier.
- (s) 180° phase reversal of a signal occurs in a single stage _____.
- (t) In common emitter amplifier, the base emitter circuit is forwardly biased and the collector circuit is _____ biased.
- (u) Depending on biasing, a _____ can be operated in cut-off, active and saturation condition.
- (v) In an oscillator the basic circuit which produces the oscillation is called _____ circuit.
- (w) Hartley oscillator or Colpitts oscillator generates _____ wave.
- (x) A crystal generates oscillation based on _____ effect.
- (y) The full form of CRO is _____.

2. (a) What do you mean by emission of electrons ?
What are the different types of electron
emission ? Describe with suitable diagram. 8
- (b) With neat diagram explain the operating
principle of a vacuum triode. 7
3. (a) With the help of V-I characteristic, explain
the operating principle of a semiconductor
diode. 8
- (b) Explain how a zener diode can be used as a
voltage regulator. 7
4. (a) Draw the different types of transistor biasing
circuit for NPN transistor. 8
- (b) With circuit diagram explain the working
principle of a transistor as an amplifier. 7
5. (a) Classify amplifier with the help of its output
characteristic and load line. 8
- (b) Draw the circuit of a push pull amplifier and
explain its operation. 7

6. (a) What is an oscillator ? Explain the basic principle of an oscillator with the help of a circuit. 8
- (b) With circuit diagram explain the operation of a Hartley oscillator. 7
7. Write short notes on any two : $7\frac{1}{2} \times 2 = 15$
- (a) Cathode Ray Oscilloscope
- (b) Energy band diagram
- (c) R-C coupled amplifier.