

Total No. of printed pages = 10

CAI-401/BEC/4th Sem/2017/N

BASIC ELECTRICAL CIRCUITS

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

The Question Paper consists of two parts : Part-A and Part-B. Both are compulsory.

PART – A

Marks – 25

All questions are compulsory.

1. Answer the following questions within one sentence each : 1×5=5

- (i) Why parallel connection is used in domestic wiring ?
- (ii) What is the commercial unit of electrical energy ?
- (iii) Should the resistance of an ammeter be low or high ?

[Turn over

(iv) What is the resistance of an electric bulb having rating as 220V, 200W ?

(v) Potential difference across the end of a wire is 0.6V, which carries a current of 8A. Find the resistance of the wire.

2. Choose the correct answer : $1 \times 10 = 10$

(i) Resistivity of a wire depends on

- (a) Length
- (b) Material
- (c) Cross-section area
- (d) None of the above.

(ii) Two bulbs marked 200 watt - 250 volts and 100 watt - 250 volts are joined in series to 250 volts supply. Power consumed in circuit is

- (a) 33 watt
- (b) 67 watt
- (c) 100 watt
- (d) 300 watt.

(iii) A circuit contains two un-equal resistances in parallel

- (a) Current is same in both
- (b) Large current flows in larger resistor
- (c) Potential difference across each is same
- (d) Smaller resistance has smaller conductance.

(iv) Two resistances R1 and R2 give combined resistance of 4.5 ohms when in series and 1 ohm when in parallel. The resistances are

- (a) 3 ohms and 6 ohms
- (b) 3 ohms and 9 ohms
- (c) 1.5 ohms and 3 ohms
- (d) 1.5 ohms and 0.5 ohms.

(v) Ohm's law is not applicable to

- (a) DC circuits
- (b) High currents
- (c) Small resistors
- (d) Semi-conductors.

(vi) A fuse is always installed in a circuit in

- (a) Series
- (b) Parallel
- (c) Delta connection
- (d) None of the above.

(vii) The rating of fuse wire is expressed in terms of

- (a) ohms (b) mhos
- (c) amperes (d) watts.

(viii) In the color code for resistances black color represents the number

- (a) 0 (b) 1
- (c) 2 (d) 3.

(ix) Production of heat due to current is related by

- (a) Ohm's law (b) Joule's law
- (c) Kelvin's law (d) Maxwell's law.

(x) A 1 k, 1 W resistor can safely pass a current of

- (A) 30mA (B) 100mA
- (C) 150 mA (D) 500 mA.

3. Match the following statements in column A with the correct answer from column B : $1 \times 5 = 5$

Column A	Column B
Electric heater coil	$\pm 5\%$
Filaments of electric bulbs	$\pm 10\%$
The tolerance for silver stripe	Tungsten
The tolerance for gold stripe	Conductance
Good conductors have high	Nichrome.

4. Read the following statements. Write TRUE or FALSE against each. $1 \times 5 = 5$

- (i) The resistivity of all pure metals increases with increase in temperature.
- (ii) Thevenin's theorem replaces a complicated circuit facing a load by an ideal voltage source and series resistor.

- (iii) Maximum power is transferred if load resistance is equal to internal resistance of the source.
- (iv) The Norton current is sometimes called the shorted-load current.
- (v) An ideal voltage source has zero internal resistance.

PART – B

Marks – 45

Answer any *five* 5 questions.

5. (a) Convert the constant voltage source shown in Fig.1 to a constant current source. 4

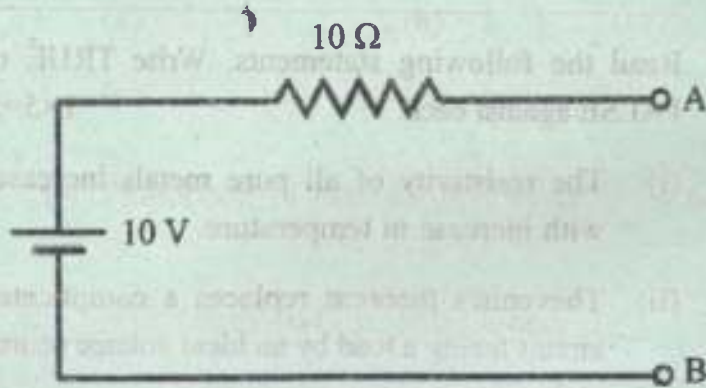


Fig. 1

- (b) Calculate the value of load resistance R_L to which Maximum Power can be transferred by the circuit shown in Fig. 2. 5

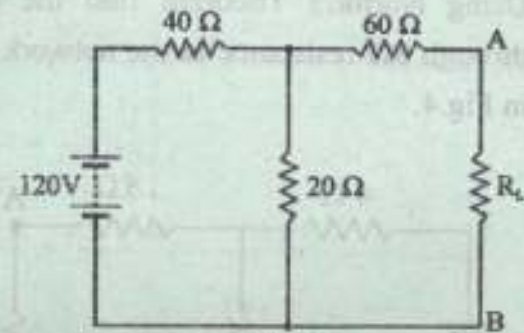


Fig. 2

6. State and prove the "Maximum Power Transfer Theorem" mathematically as applicable to DC networks. 9
7. (a) Using Thevenin's theorem find out the current flowing through the 100Ω resistance in Fig.3 6

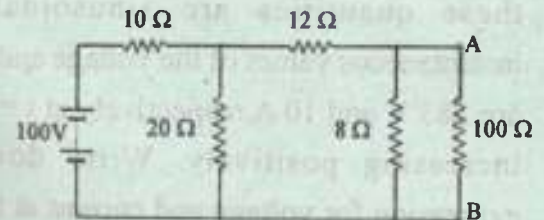


Fig. 3

(b) State and explain Kirchhoff's Laws with suitable examples. 3

8. (a) Using Norton's Theorem find the current through 8Ω resistance in the network shown in Fig.4. 6

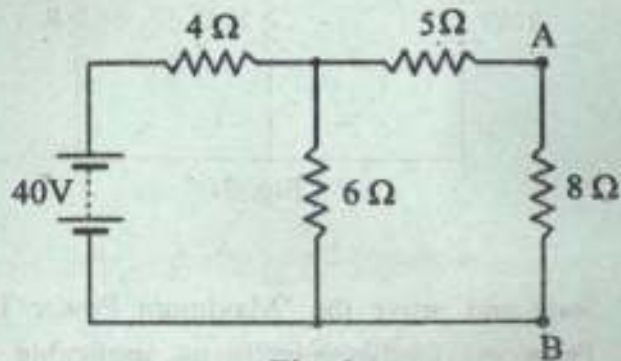


Fig. 4

(b) The maximum values of the alternating voltage and current are 400 V and 20 A respectively in a circuit connected to 50 Hz supply and these quantities are sinusoidal. The instantaneous values of the voltage and current are 283 V and 10 A respectively at $t = 0$, both increasing positively. Write down the expression for voltage and current at time t . 3

9. (a) Prove that the current in the 50Ω resistance of the network shown in Fig.5 is 0.1A, using any suitable method of your convenience 6

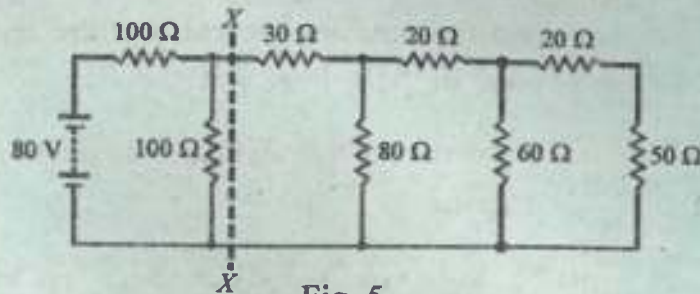


Fig. 5

(b) Find the form-factor of the wave form given in Fig.6. 3

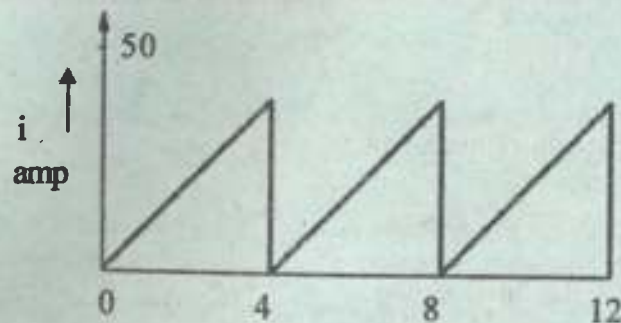


Fig.6

10. (a) A 60-Hz voltage of 115 V (r.m.s.) is impressed on a 100Ω resistance :

(i) Write the time equations for the voltage and the resulting current. Let the zero point of the voltage wave be at $t = 0$.

(ii) Show the voltage and current on a time diagram.

(iii) Show the voltage and current on a phasor diagram. 6

(b) A $50\text{-}\mu\text{F}$ capacitor is connected across a 230-V, 50-Hz supply. Calculate the reactance offered by the capacitor and the maximum current. 3

11. Write short notes on : $3 \times 3 = 9$

(a) Power factor

(b) Resonance

(c) Form and Peak factor.