

Total No. of printed pages = 5

ET-403/DE/4th Sem/2017/N

DIGITAL ELECTRONICS

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks
for the questions.

PART – A

Marks – 25

1. State whether the following are true or false :
1×10=10
 - (a) TTL is used in electronic calculator.
 - (b) In signed numbers, MSB is the sign bit.
 - (c) Gray code of 1011011 is 1110110.
 - (d) NAND gate can work as inverter if both inputs are not connected together.

[Turn over

- (e) In a sequential logic circuit the output depends on the present input only.
- (f) A positive edge triggered flip-flop changes state on the high to low transition of the clock pulse.
- (g) In synchronous counter, the clock inputs are connected separately.
- (h) For M memory location we need P address line where $2^P = M$.
- (i) Most commonly used D/A converter is the binary ladder network.
- (j) K-map cannot be drawn when the number of variables is more than 4.

2. Fill in the blank :

$$1 \times 10 = 10$$

- (a) Serial loading means entering _____ bit per clock pulse.
- (b) The process of entering information into memory is called _____.
- (c) In X-OR gate, the same input gives the _____ output.

- (d) EPROM can be erased by using _____ light.
- (e) In a multiplexer the particular input appearing at the output depends on the status of _____ lines.
- (f) A _____ can be used as demultiplexer.
- (g) Each term in POS form is called _____ term.
- (h) $1111.10_2 + 10.011_2 = \underline{\hspace{2cm}}$.
- (i) The _____ family has good noise immunity.
- (j) Decimal number 90 equals _____ in 2's complement.

3. Write the full form of :

$$1 \times 5 = 5$$

- (i) EEPROM
- (ii) EBCDIC
- (iii) CMOS
- (iv) ASCII
- (v) ECL

PART – B

Marks – 45

1. Convert the following : $2 \times 2\frac{1}{2} = 5$
 - (a) $FA5_{16}$ into octal.
 - (b) 7.2_{10} into excess-3 code.
2. Minimize logic function 5
 $F(A,B,C,D) = m(0,1,4,5,7,8) + d(10,11,14)$
using k-map.
3. What is race around condition ? Describe the logic circuit of a clocked J-K flip-flop with Preset/Clear input and truth table. 5
4. State De Morgan's theorems and explain with logic diagram. 5
5. Realize the logic equation : $2 \times 2\frac{1}{2} = 5$
 - (a) $Y = A\bar{B} + BC + \bar{C}\bar{A}$ by using NAND gate only
 - (b) Convert $Y = ABC + A\bar{B}D + BC + AD$ into standard SOP form.

6. Explain the operation of a 5 bit serial out shift register. 5
7. Classify various types of semiconductor memory devices and the principles of operation of physical characteristics. 5
8. Explain difference between : $2 \times 2\frac{1}{2} = 5$
 - (a) TTL and CMOS circuit.
 - (b) Synchronous and Asynchronous counter.
9. Write short notes on any one : 5
 - (a) 8:1 Multiplexer
 - (b) Ring counter
 - (c) A/D converter.