

2018

NETWORK THEORY

Paper : IE 301

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) How a voltage source can be converted into a current source and vice versa ? 4

- (b) Determine the resistance between the terminals A and B of the following network : 5

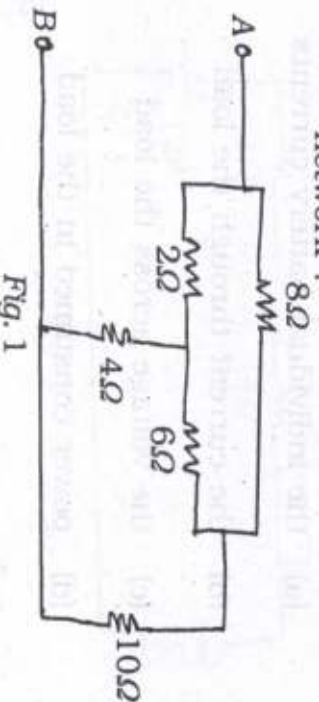


Fig. 1

Contd.

- (c) Determine the current in the 1Ω resistor in the circuit : 6

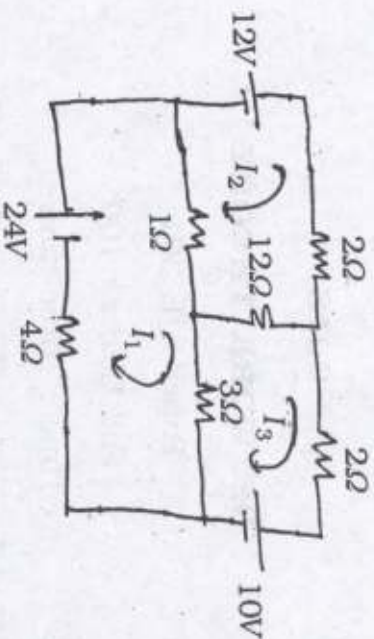


Fig. 2

- (d) Two batteries having *emf* of 10V and 7V and internal resistance of 2Ω and 3Ω respectively, are connected in parallel across a load resistance 1Ω . Calculate —

- the individual battery currents
- the current through the load
- the voltage across the load
- power consumed in the load.

5

2. (a) State the prove initial value and final value theorem. 6

- (b) How a series RLC circuit will respond to

- Step function ?
 - Impulse function ?
- 7+7=14

3. (a) The dc voltage is applied to the circuit shown in Fig. 3 keeping the switch K open so that steady state is reached. Determine the complete response for the circuit after closing the switch K. 6

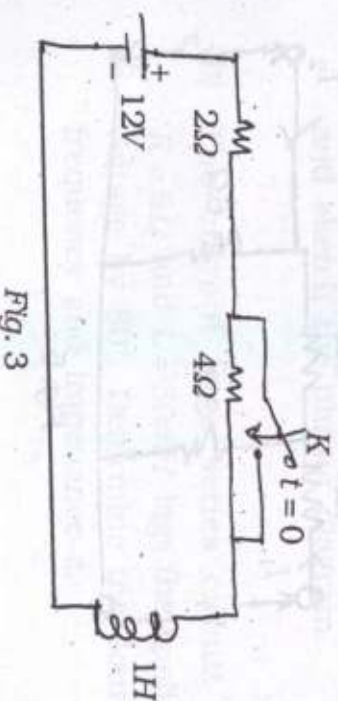


Fig. 3

- (b) In the circuit shown in Fig. 4 the switch K is thrown from position A to position B at time $t = 0$, the current having previously reached its steady state. Determine $i(t)$ after switching.

4

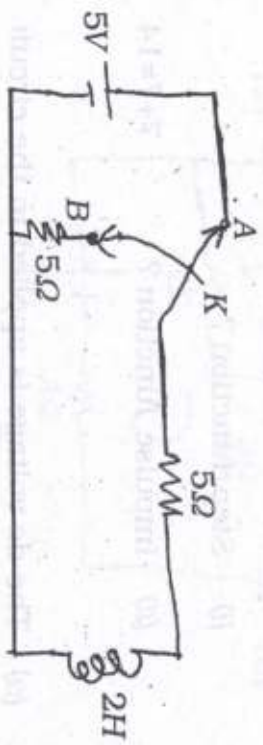


Fig. 4

- (c) Determine the z -parameters of the network shown in Fig. 5.

6

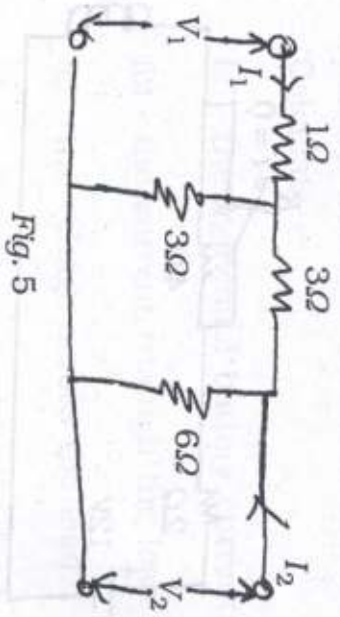


Fig. 5

- (d) Determine the condition under which the input impedance of the network shown in Fig. 6 will be equal to R .

4

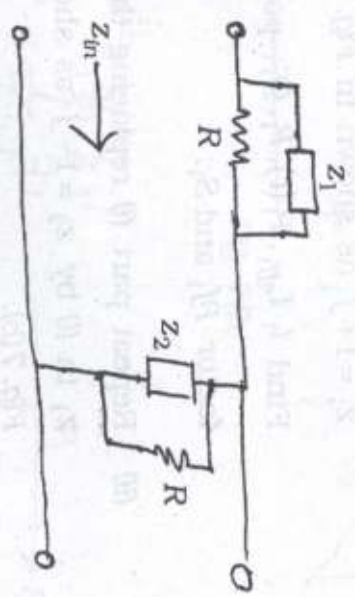


Fig. 6

4. (a) A series combination of $R = 10\Omega$ and $L = 20mH$ has a current $i = 5.0 \cos(500t + 10^\circ)$ A. Obtain the voltages v and V , the phasor current I and sketch the phasor diagram.

6

- (b) The current in a series circuit of $R = 5\Omega$ and $L = 30mH$ lags the applied voltage by 80° . Determine the source frequency and impedance z .

4

- (c) (i) A sinusoidal voltage with

$V_{eff} = 10V$ is connected across

$z_1 = 1 + j$ as shown in Fig. 7(a).

Find i_1 , I_{eff} , $P_1(t)$, P_1 , Q_1 , power




factor P_f and S_1 .

- (ii) Repeat part (i) replacing the load

z_1 in (i) by $z_2 = 1 - j$ as shown in Fig. 7(b).


- (iii) Repeat part (i) after connecting in parallel z_1 in (i) and z_2 in (ii) as shown in Fig. 7(c).

10

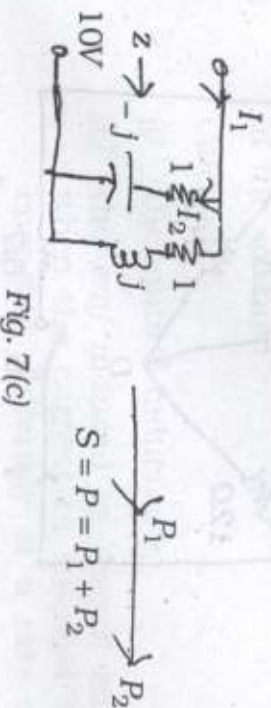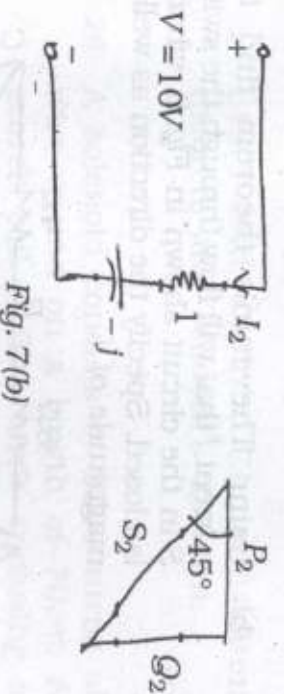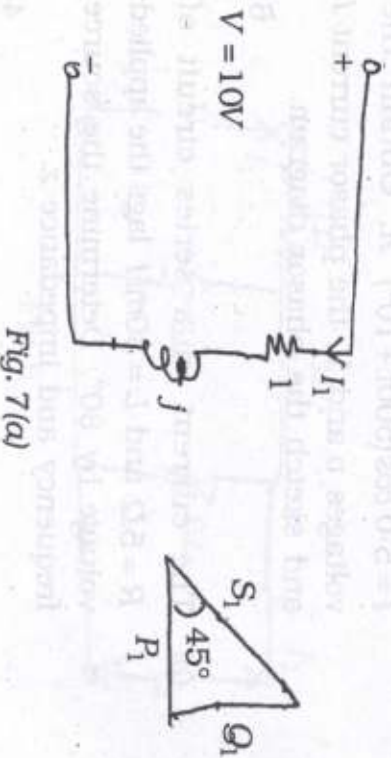

5. (a) Determine the current through the 3Ω resistor in the circuit shown in Fig. 8 by using Superposition theorem

5

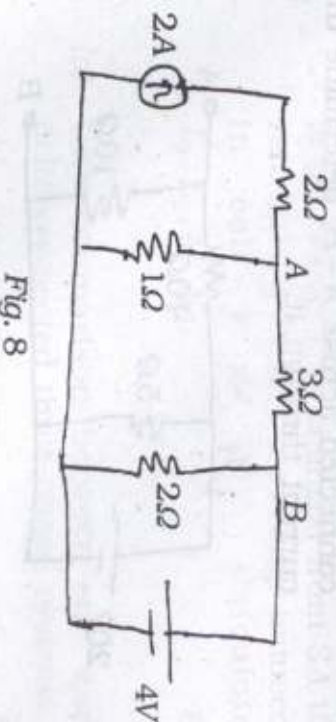

- (b) Using Thevenin's theorem find the current I that will flow through the switch S in the circuit shown in Fig. 9, when it is closed. Specify the direction as well as magnitude of I .

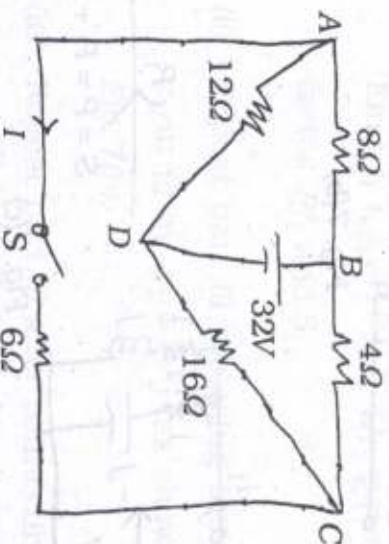


Fig. 9

- (c) Draw the Norton's equivalent circuit at the terminals $A-B$ for the given circuit of Fig. 10. If a 2Ω resistance is connected across $A-B$, determine the current through it.

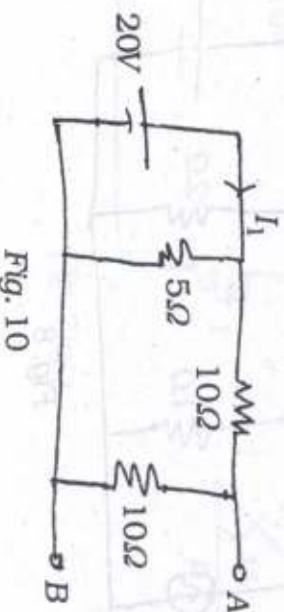


Fig. 10

6. (a) State and explain Compensation theorem and Tellegen's theorem.

10

- (b) A solenoid consists of 2000 turns of wire wound on a length of 70cm. A search coil of 500 turns enclosing a mean area of 30cm^2 is placed centrally in the solenoid.

Calculate :

- (i) the mutual inductance
(ii) the emf induced in search coil when the current in solenoid is changing uniformly at a rate of 260A/sec .

4

- (c) The coefficient of coupling between two coils is 0.75. There are 250 turns in coil 1. The total flux linking coil 1 is 0.4mWb , when the current in this coil is 3A. When i_1 is changed from 3A to zero linearly in 3ms, the voltage induced in coil 2 is 70V. Calculate L_1, L_2, M, N_2 .

6

7. (a) Give comparison between star and delta-connected three-phase systems.

7

(b) A 220V, three-phase voltage is applied to a balanced, delta-connected three-phase load by phase impedance $(15 + j20)\Omega$.

Find —

- (i) the current in each line
- (ii) the power consumed per phase
- (iii) the phasor sum of the three line currents.

(c) State the advantages of Three-phase systems. 7