

Total number of printed pages-6

53 (IT 303) DLDG

2018

DIGITAL LOGIC DESIGN

Paper : IT 303

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions.

1. (a) Convert the following : $1 \times 3 = 3$

(i) $(41)_8 = ()_2$

(ii) $(DF2)_{16} = ()_2$

(iii) $(12.25)_{10} = ()_2$

- (b) What do you understand by binary coding ? Explain with an example.

3

Contd.

- (c) State De Morgan's theorem of Boolean Algebra. 2
- (d) Simplify $Y = \overline{abc} + abc + \bar{a} + \bar{a}bc$ using Boolean algebraic techniques. 2
- (e) Draw the symbol of an X-NOR gate and write down the truth table of the same. 2
- (f) Describe the function of a 4:2 Encoder with truth table, block diagram, logic diagram. 5
- (g) Convert $Y = ab + c$ into Canonical SOP form. 3
2. (a) Define Maxterm and explain with an example. 3
- (b) Simplify $Y = \sum m(0, 1, 3, 5, 9, 10, 11, 12, 14) + d(2, 13)$ using K-map method. 6
- (c) Describe JK latch with logic diagram, truth table. 5
- (d) Design a 1:8 De-multiplexer. 5

- (e) How many control lines are needed to design a 16:1 Multiplexer. 1
3. (a) Describe 4-bit asynchronous counter with block diagram, timing diagram and necessary table. 7
- (b) Design a Mod-5 Counter with JK flip-flop. 11
- (c) Distinguish between truth table and transition table. 2
4. (a) Draw the State Transition diagram of a JK flip-flop. 3
- (b) Derive the characteristic equations of a JK flip-flop. 3
- (c) Simplify $Y = \overline{xyz + xy + z} + (x + \bar{y})(x + yz) + xz$ using Boolean algebraic techniques. 3
- (d) Simplify $Y = \prod M(0, 1, 3, 4, 5, 9, 10, 11, 12)$ into POS form using K-map method. 6
- (e) Describe the function of a 4-bit Ripple Carry Adder with block diagram. 4

(f) Find out the 2's complement of
111001111. 1

5. (a) Design a Full subtractor using
minimum basic logic gates. 6

(b) Explain the operation of a pulse-
triggered SR latch. 4

(c) Draw the block diagram of a Negative-
edge triggered master-slave JK flip-flop. 2

(d) Draw the State Transition diagram of a
SR flip-flop. 2

(e) State Distributive Law of Boolean
Algebra. 2

(f) Draw the block diagram of a 3-bit
synchronous counter using JK flip-flop. 2

(g) Draw the block diagram of a 3-bit
Register using D flip-flop. 2

6. (a) Design a Mod-7 Counter using D flip-
flop. 10

(b) Convert the following : 2

(i) $(F12)_{16} = ()_2$

(ii) $(1101.01)_2 = ()_{10}$

(c) Use only NOR gate to implement
 $Y = ab + c$. 3

(d) Use only NAND gate to implement
 $Y = \overline{a}b + c$. 3

(e) Derive the characteristic equations of
a D flip-flop. 2

7. (a) Use basic logic gates to implement
 $Y = \overline{a}b + abcd + a\overline{b}c + \overline{a}bcd$. 3

(b) State Commutative Law of Boolean
Algebra. 1

(c) Draw the logic diagram of a 1-bit
comparator. 2

(d) Distinguish between combinational and
sequential logic. 2

(e) Prove that $\overline{a + b + c} = \overline{a} \cdot \overline{b} \cdot \overline{c}$. 2

(f) Draw the logic diagram of a D latch. 2

(g) Draw the block diagram of a 8:1 multiplexer. 1

(h) Draw the symbol of a Positive-edge triggered, master-slave flip-flop. 1

(i) Prove that $x + \bar{x}y + \bar{x}yz = x + y$. 1

(j) Define Minterm. 1

(k) $1 \oplus 1 \oplus 0 \oplus 1 \oplus 0 =$ _____. 1

(l) Ex-3 code of 91 = _____. 1

(m) BCD code of 41 = _____. 1

(n) Prove that $(x + yz)(x + w\bar{x})(x + \bar{y}z) = x$. 1
