

2018

**ELECTRICAL MEASUREMENTS
AND INSTRUMENTS**

Paper : IE 402

Full Marks : 100

Time : Three hours

*The figures in the margin indicate
full marks for the questions.*

Answer any five questions.

1. (a) Describe the dynamic behaviour of Galvanometer and derive the expression for deflection θ . Also, discuss the response of the Galvanometer under different conditions.

10

- (b) Explain the difference in constructional details of Ballistic Galvanometer and a d'Arsonval Galvanometer.

5

- (c) The inductance of a moving iron instrument is given by :

$$L = (50 + 2\theta - \theta^2) \mu H$$

where θ is the deflection in radian from zero position. The spring constant is $12 \times 10^{-6} \text{ Nm/rad}$. Estimate the deflection for a current of 2A.

5

2. (a) Describe the constructional details and working of an electrodynamic type instrument. Also, derive the equation for deflection under a.c. operation.

10

- (b) Derive the expression for a electrostatic type of instrument using spring control.

5

- (c) Explain the working of a Quadrant Electrometer using a suitable diagram.

5

3. (a) Explain the working of a rectifier type of Voltmeter using a suitable diagram.

5

- (b) A basic d'Arsonval movement with a full scale reading of 100 mA and an internal resistance of 1000Ω is available. It is to be converted into a

$0-1 \text{ A}$, $0-10 \text{ A}$, $0-100 \text{ A}$ multirange Ammeter, calculate the value of the individual shunts.

6

- (c) Describe the working of a Current Transformer. Also, draw the equivalent circuit and phasor diagram.

9

4. (a) Explain the construction and basic principle of operation of an Energymeter. Show that in a single phase Energymeter, the total number of revolutions of the disc is directly proportional to energy.

10

- (b) Describe the following applications of D.C Potentiometer with suitable diagrams :

10

(i) Calibration of Voltmeter

(ii) Calibration of Ammeter

(iii) Measurement of unknown resistance

(iv) Measurement of Power.

5. (a) Describe a method for the measurement of the following : 10

(i) Insulation resistance

(ii) Earth resistance.

(b) Derive the expression for bridge sensitivity for a Wheatstone bridge. Also, determine the expression for the current through the Galvanometer in the Wheatstone bridge. 10

6. (a) The four arms of a Maxwell's capacitance bridge at balance are : arm ab , an unknown inductance L_1 , having a resistance R_1 ; arm bc a non-inductive resistance of 1000Ω ; arm cd , a capacitor of $0.5\mu F$ in parallel with a resistance of 1000Ω ; arm da , a resistance of 1000Ω .

Derive the equations of balance for the bridge and determine the value of R_1 and L_1 . 5

(b) Describe a method for the measurement of unknown capacitance. 5

(c) Draw the diagram of Anderson's bridge and derive the equations of balance. 6

(d) Using a suitable diagram, explain how eddy current damping is produced in an electrical instrument. 4

7. Write short notes on : (any two)

10×2=20

(i) M.I. Instruments

(ii) A.C. Potentiometer

(iii) Megger

(iv) Vibration Galvanometer.