

2018

**POWER ELECTRONICS**

Paper : IE 602

Full Marks : 100

Time : Three hours

***The figures in the margin indicate full marks for the questions.***

***Answer any five questions.***

1. (a) Draw the I-V characteristics of an SCR. Define the terms — forward blocking region, holding current, latching current. 8
- (b) Give a comparison between Power MOSFET and BJT. 6
- (c) Draw the equivalent circuit of —  
(i) IGBT (ii) MCT 3×2=6
2. (a) How a GTO can be turned off? Explain. 10

*Contd.*

(b) How a thyristor can be protected against high  $dv/dt$  and high  $di/dt$ ? Explain with neat diagram. 10

3. (a) A single phase 230V, 1kW heater is connected across 1-phase, 230V, 50Hz supply through an SCR. For firing angle delays of  $45^\circ$  and  $90^\circ$ , calculate the power absorbed in the heater element. 5

(b) A dc battery is charged through a resistor  $R$  as shown in fig.1. Derive an expression for the average value of charging current in terms of  $V_m$ ,  $E$ ,  $R$ , etc. on the assumption that SCR is fired continuously. 7

(i) For an ac source voltage of 230V, 50Hz, find the value of average charging current for  $R = 8\Omega$  and  $E = 150V$ . 7

(ii) Find the power supplied to battery and that dissipated in the resistor.

(iii) Calculate the supply pf. 10

(c) Explain the working of a single phase half wave controlled rectifier with RL load. 8

4. (a) What is a Chopper? Explain the control strategies of a chopper. 8

(b) For a type-A chopper, dc source voltage is 230V, load resistance is  $10\Omega$ . Take a voltage drop of 2V across chopper when it is on. For a duty cycle of 0.4, calculate —

(i) average and rms values of output voltage

(ii) chopper efficiency. 6

(c) A step-up chopper has input voltage of 220V and output voltage of 660V. If the conducting time of thyristor-chopper is  $100\mu s$ , compute the pulse width of output voltage.

In case output-voltage pulse width is halved for constant frequency operation, find the average value of new output voltage. 6

5. (a) What is an Inverter? Give the steady state analysis of a single phase inverter. 10

(b) Explain different modes of a modified McMurray Half bridge Inverter. 10

6. (a) What is SMPS? Explain any one configuration of SMPS. 10

(b) A separately excited dc motor is supplied from 230V, 50Hz source through a single phase half wave controlled converter. Its field is fed through 1-phase semiconverter with zero degree firing-angle delay. Motor resistance  $r_a = 0.7\Omega$  and motor constant =  $0.5V \text{ sec/rad}$ . For rated load torque of  $15Nm$  at  $1000 \text{ rpm}$  and for continuous ripple free currents, determine —

- (i) firing-angle delay of the armature converter
- (ii) rms value of thyristor and free wheeling diode currents
- (iii) input power factor of the armature converter. 10

7. Write short notes on:  $10 \times 2 = 20$

(a) UPS

(b) Cycloconverter.

\_\_\_\_\_