

Total No. of printed pages = 7

END SEMESTER EXAMINATION, NOVEMBER-2018

Semester – 3rd (New Course)

Subject Code : EI-304

ELEMENTS OF ELECTRICAL ENGINEERING

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.

Instructions :

1. *All* questions of PART – A are compulsory.
2. Answer any *five* questions from PART – B

PART – A

Marks – 25

1. Fill in the blanks :

$1 \times 10 = 10$

- (a) The flow of electric current in a conductor is due to flow of _____.
- (b) One volt is equal to _____.
- (c) Electric pressure is also called _____.

[Turn over

- (d) The resistance of wire varies inversely as _____.
 - (e) Electrical conductivity is measured in _____.
 - (f) With rise in temperature the insulating property of an insulator _____.
 - (g) The ratio of rms value to average value is called the _____ factor.
 - (h) The fuse wire is made of _____.
 - (i) The generator operates on the principle of _____ induced emf.
 - (j) A network having one or more than one source of emf is known as _____ network.
2. Write true or false : $1 \times 10 = 10$
- (a) For a series as well as parallel circuit powers are additive.
 - (b) Resistance is an active element in a circuit.
 - (c) A network having one or more than one source of emf is known as passive network.

- (d) Kirchhoff's current law is applicable only to junction in a network.
 - (e) DC voltage has one polarity.
 - (f) The emf induced in a DC motor opposes the applied voltage.
 - (g) The standard supply frequency in India is 60 Hz.
 - (h) The DC generator works on the principle of Fleming's left hand rule.
 - (i) DC motor converts mechanical power into electrical power.
 - (j) Transformer is a rotating device.
3. Choose the correct answer : $1 \times 5 = 5$
- (a) In which of the following substance, the resistance decreases with increase of temperature ?

(i) carbon	(ii) constantan
(iii) copper	(iv) silver

(b) If a phasor is multiplied by operator J , then

- (i) only its magnitude changes
- (ii) only its direction changes
- (iii) both magnitude and direction changes
- (iv) None of the above

(c) The time period of an alternating quantity is 0.02 second, its frequency will be

- (i) 25 Hz
- (ii) 50 Hz
- (iii) 100 Hz
- (iv) 0.02 Hz

(d) The power factor of an AC circuit is given as

- (i) sine of phase angle
- (ii) cosine of phase angle
- (iii) tangent of phase angle
- (iv) q -factor of a circuit

(e) In a parallel R-L-C circuit admittance is defined as the reciprocal of

- (i) resistance
- (ii) reactance
- (iii) impedance
- (iv) susceptance

143/EI-304/EoEl.Engg.(N)

(4)

PART - B

Marks - 45

4. (a) Write three properties of good conductors and good insulators. 3

(b) Define work, power and energy with units. 3

(c) Find the relation between kWh and kcal. 3

5. (a) Write the advantages of parallel circuit. 2

(b) State and explain Kirchhoff's laws. 4

(c) A resistance R is connected in series with a parallel combination of 12 ohm and 8 ohm. Calculate R if the total power dissipated in the circuit is 70 watt when the applied voltage is 20 volt. 3

6. (a) What is back emf of DC motor ? 2

(b) What are the different types of DC motor ? Explain with diagrams. 4

(c) A four pole lap wound armature has 960 conductors and a flux per pole of 20 mwb. Calculate the emf generated when running at 400 rpm. Also find the emf generated if the armature is wave wound. 3

143/EI-304/EoEl.Engg.(N)

(5)

[Turn over

7. (a) Define the term rms value of alternating current. 3

(b) A sinusoidal voltage of frequency 50 Hz has a maximum value of $200\sqrt{2}$ volts. At what time measured from a positive maximum value will the instantaneous voltage be 141.4 volts ? 4

(c) Discuss the importance of power factor. 2

8. (a) Define the following terms in an AC circuit : 6

(i) impedance

(ii) power factor

(iii) inductive reactance

(b) A circuit with $100\mu\text{F}$ is connected in series with a resistance of 25Ω across 250 volts 50Hz supply. Calculate : 3

(i) reactance

(ii) impedance

(iii) current

143/EI-304/EoEI.Engg.(N) (6)

9. (a) Explain the working principle of a single phase transformer with the help of diagram. 6

(b) Explain the term transformation ratio. 3

10. Describe the principle of an induction motor.

A six pole 50 cycle, induction motor is running at 950 rpm.

Find the slip, slip speed and synchronous speed. 9

143/EI-304/EoEI.Engg.(N) (7) 2300(V)