

Total number of printed pages-5

53 (EC 201) BAEL

2019

BASIC ELECTRONICS

Paper : EC 201

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer **any five** questions out of 7.

1. (a) Describe the breakdown mechanism of a p-n junction ϕ draw the I-V characteristics. 3+3
- (b) Why capacitor filter/peak rectifier is necessary in the chain of AC-to-DC conversion? Describe its operation and hence derive the expression for ripple voltage. 2+8
- (c) Write a short note on extrinsic semiconductors. 4

Contd.

2. (a) Explain the full-wave rectification using Bridge rectifier circuit and hence derive expressions for average and r.m.s value of output voltage. 6+2+2

(b) Describe the operation of n MOSFET in triode mode and plot $I_D \sim V_{DS}$ & $I_G \sim V_{GS}$ characteristics. 6+2+2

3. (a) Classify the types of feedback amplifiers and give a detail comparison of these amplifiers with reference to voltage gain, current gain, Input impedance and output impedance. 2+8

(b) $(8A)_{16}$, $(3E)_{16}$, $(83)_8$: Convert these numbers into decimal equivalent and its corresponding binary equivalent. 3+2

(c) Describe the Early Effect in BJT in brief. 4

4. (a) Draw the block diagram of ramp-type Digital Multi Meter (DMM) and explain its basic operation. 10

(b) How does an Light Emitting Diode unit light? Explain.

(c) $Y = (A + B)$: Implement this Boolean expression using universal gates. (NAND 2 input) 4

5. (a) $Y = (A.B)$: Implement the Boolean expression using 2 input NOR gate. 4

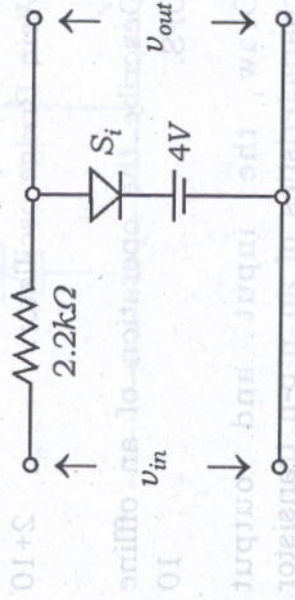


Fig 1

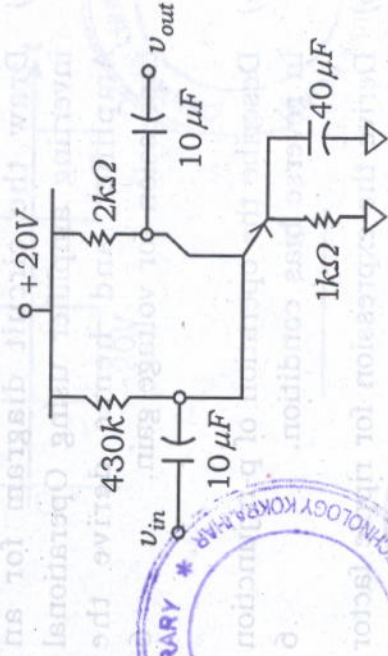


Fig 2

(b) An input sine wave of 14V peak-to-peak, 60Hz is applied to the input of Fig 1, so draw the output waveform exactly below the input. 4

(c) Describe the Barkhausen's criterion for oscillation, and derive the expression for the frequency of oscillation in an Wein Bridge oscillator. 2+10

6. (a) Describe the operation of an offline UPS. 10

(b) Draw the input and output characteristics of an n-p-n transistor in Common-Base mode. 2+2

(c) Draw the circuit diagram for an inverting amplifier using Operational Amplifier and hence derive the expression for voltage gain. 6

7. (a) Describe the operation of p-n junction in reverse bias condition. 6

(b) Derive the expression for ripple factor in a half-wave rectifier. 6

(c) Explain the working principle and plot the output waveform for the following circuit. (the input waveform is shown below). 8

