

Full Marks: 70

Pass Mark: 28

Time: 3 Hrs

Course Code: CAI-301

Course Title: Principles of Electrical & Electronics Engineering

**PART A**

1. Pick the right answer [10 X 2=20]

(a) Kirchhoff's current law is applicable only

- (i) Closed loops in a network
- (ii) Electronic circuit
- (iii) Junctions in a network
- (iv) Electric circuits

(b) Kirchhoff's voltage law is concerned with

- (i) IR drops
- (ii) Battery e.m.f.
- (iii) Junction voltages
- (iv) Both (i) and (ii)

(c) According to KVL, the algebraic sum of all IR drops and e.m.f.s in any closed loop of a network is always

- (i) Zero
- (ii) Positive
- (iii) Negative
- (iv) Determined by battery e.m.f.s

(d) The algebraic sign of an IR drop is primarily dependent upon the

- (i) Amount of current flowing through it
- (ii) Value of R
- (iii) Direction of current flow
- (iv) Battery connection

(e) What is the relation between energy and power?

- (i)  $\text{Energy} = \text{Power} \times \text{Time}$
- (ii)  $\text{Energy} = \text{Power} \div \text{Time}$
- (iii)  $\text{Energy} = \text{Power} + \text{Time}$
- (iv)  $\text{Energy} = \text{Power} - \text{Time}$

(f) Write the unit of work.

- (i) Watt
- (ii) Joule
- (iii) Calorie
- (iv) Second

(g) Write the unit of power.

- (i) Watt
- (ii) Joule
- (iii) Calorie
- (iv) Second



- (h) Write the polar form of  $-5-6j$ .
- $7.81 \angle 50.18^\circ$
  - $11 \angle 30.8^\circ$
  - $10.7 \angle -11.8^\circ$
  - $7.81 \angle -129.8^\circ$
- (i) If a 220 V heater is used on 110 V supply, heat produced by it will be
- One-half
  - Twice
  - One-fourth
  - Four times
- (j) Active materials of a lead acid cell are:
- Lead peroxide
  - Sponge lead
  - Dilute sulphuric acid
  - All the above




2. Fill in the blanks [5x1=5]
- The capacity of a cell is measured in \_\_\_\_\_.
  - After doping semiconductor material is known as \_\_\_\_\_ material.
  - Two windings of a transformer are designated as primary winding and \_\_\_\_\_ winding.
  - Transformer action requires \_\_\_\_\_ magnetic flux.
  - Rating of transformers is expressed in \_\_\_\_\_.

### **PART B**

**(Answer any five from the following)**

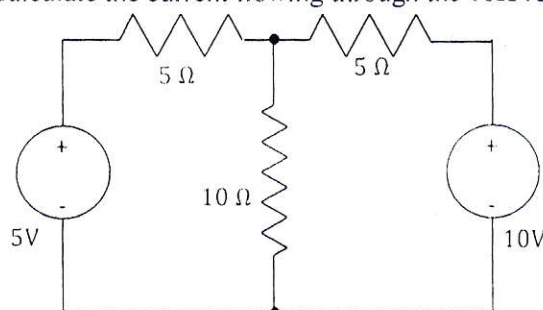3. (a) What do you mean by phase difference? Explain with suitable example. [4]  
 (b) An alternating current of frequency 50Hz has a maximum value of  $200\sqrt{2}$  A. Reckoning the time from the instant the current is zero and becoming positive, find the time taken by the current to reach a value of 141.4 A for a first and second time. [5]
4. Do the following operation- [3X3=9]
- $(5 \angle 150^\circ) \div 4j$
  - $(5 \angle 30^\circ) + (-3 + 4j)$
  - $(-5 + 5j) - (5 \angle -30^\circ)$
5. (a) What is an ideal transformer? [4]  
 (b) The emf per turn for a single phase, 2310/220 V, 50 Hz transformer is approximately 13 volts. Calculate the number of primary and secondary turns. [5]
6. (a) Write the statement of KCL and KVL? [4]  
 (c) Calculate the current flowing through the  $10\Omega$  resistance of the following figure. [5]



7. (a) Write about the different parts of a lead-acid battery. [4]  
(b) Write the chemical changes during discharging and charging of a lead-acid cell? [5]
8. (a) Draw the circuit diagram of a bridge rectifier, together with its input and output waveforms. [4]  
(b) Calculate the values of collector current  $I_C$  and emitter current  $I_E$  for a BJT with emitter-to collector current gain  $\alpha_{dc} = 0.97$  and base current  $I_B = 50 \mu A$ . Determine base-to collector gain  $\beta_{dc}$  for the device. [5]

\*\*\*\*\*

