

**END SEMESTER/ RE-TEST EXAMINATION, 2020  
(OLD&NEW)**

**Semester: 5<sup>th</sup> semester**

**Subject code: ET -503**

**Subject: Power Electronics**

**Full Marks= (Part A-25 + Part B- 45)**

**Duration: 3 hours**

***Questions on Part-A are compulsory  
Answer any five questions from Part-B***

**Q1. Fill in the blanks:**

**1X10=10**

1. a. A SCR IS two -----analogy.
1. b. A TRIAC is a ----- directional thyristor.
1. c. A thyristor can be turned on by ----- gate signal.
1. d. IGBT is a----- controlled device.
1. e. The conversion of ac to dc is known as-----.
1. f. Rectifier circuit using thyristors are known as -----
1. g. An inverter is a ----- converter.
1. h. SMPS is multistage ----- supply and is used for high rating.
1. i. UPS stands for ----- .
1. j. A ----- Regulator gives an output voltage which is more than input voltage.

**Q.2. Write true or false.**

**1X10=10**

2. a. SCR is a unidirectional device.
2. b. A TRIAC has two terminals.
2. c. All inverter uses forced commutation.
2. d . A switching regulator uses PWM.
2. e. A SMPS have four different configurations.
2. f. A CSI (Current Source Inverter) has simple commutation circuit.
2. g. Both MOSFET and IGBT have high input impedance.
2. h. A snubber circuit uses L and C in series.
2. I.The output voltage of a controlled rectifier is maximum when firing angle is zero.
2. j. SMPS stands for Single Mode Power Supply.



Q.3. Choose the correct answer:

1X5=5

3. a. The two-transistor model of a thyristor consists of two transistors

- i) One n-p-n and other p-n-p
- ii) Both p-n-p
- iii) Both n-p-n
- iv) One n-p-n and other UJT

3. b. Freewheeling diode is useful when the load is

- i) Inductive
- ii) Capacitive
- iii) Resistive
- iv) None of the above

3. c. Which rectifier requires two diodes and two SCRs

- i) Half wave controlled rectifier
- ii) Full wave controlled bridge rectifier
- iii) Half controlled bridge rectifier
- iv) Semi converter

Q.3.d. UPS is never used in

- i) Street lighting
- ii) Computers
- iii) Communication link
- iv) Instrumentation

3e. If we need a low noise device, we should use

- i) BJT
- ii) FET
- iii) Thyristor
- iv) UJT

**PART B**  
**MARK-45**

Q.4.

Q.4.a. What is a thyristor? 2

Q.4.b. Name the members of Thyristor family. 5

Q.4.c. Draw the symbol of SCR, DIAC, TRIAC and IGBT. 2

Q.5.

Q.5.a. What is a power diode? 2

Q.5.b. Name some applications of power diode 3

Q.5.c. Compare power MOSFET and IGBT. 4

Q.6.

Q.6.a. What is a controlled rectifier. 2

Q.6.b. Explain the working of a single phase half wave controlled rectifier feeding a purely resistive load. 5

Q.6.c Draw the waveform of input voltage, firing pulses, output voltage and output current. 2

Q.7.

Q.7.a. What is an inverter? 2



Q.7.b. Give a brief classification of inverter.	3
Q.7.c. Draw a neat circuit diagram of voltage driven inverter and explain its working.	4
Q.8.	
Q.8.a. what is SMPS? What are the different configurations of SMPS?	4
Q.8.b.Explain the principle of operation of Buck regulator with a proper circuit diagram.	5
Q.9.	
Q.9.a. What is UPS? How is it classified?	5
Q.9.b. Explain the working of OFF-LINE UPS in brief with a proper diagram.	4
Q.10. What is an ac regulator? Explain the working of static load tap changer with a proper circuit diagram.	9
Q.11. State and explain various methods of speed of control of stepper motor.	9
<b>OR</b>	
State and explain various methods of speed of control of DC motor.	9
Q.12. Write a notes on Snubber circuit and three phase bridge inverter.	9

\*\*\*\*\*

