

**2021**

**FUNDAMENTALS OF ELECTRICAL AND ELECTRONICS  
ENGINEERING**

*Full Marks: 60*

Time: 2 hours

*The figures in the margin indicate full marks for the questions.*

A. Multiple Choice Questions

1 x 20=20

1. Which of the following is a semiconductor?
  - a. Copper
  - b. Platinum
  - c. Germanium
  - d. Iron
2. The number of valance electrons in silicon are
  - a. 1
  - b. 2
  - c. 3
  - d. 4
3. Which of the following is a pentavalent impurity?
  - a. Aluminum
  - b. Arsenic
  - c. Boron
  - d. Cadmium
4. Bipolar Junction Transistor has how many terminals?
  - a. 1
  - b. 2
  - c. 3
  - d. 4

5. Which layer of BJT is heavily doped?
  - a. Emitter
  - b. Base
  - c. Collector
  - d. Both a and c.
6. In the output characteristics of a Bipolar Junction Transistor, the output current  $I_c$  is zero in \_\_\_\_\_
  - a. active region
  - b. saturation region
  - c. cutoff region
  - d. both b and c.
7. The purpose of using a capacitor in a voltage regulator circuit is to
  - a. rectify the ac voltage.
  - b. filter the ripples.
  - c. regulate the output voltage.
  - d. step down the input voltage.
8. The SI units of potential difference, electric current, electric power and energy are
  - a. Volt, ampere, joule and watt respectively
  - b. Volt, ampere, watt-hr and joule/sec respectively
  - c. Volt, ampere, joule/sec and joule respectively
  - d. None of the above
9. A junction where two or more than two network elements meet is known as a
  - a. node
  - b. branch
  - c. loop
  - d. mesh
10. The period of a wave is
  - a. the same as frequency
  - b. time required to complete one cycle
  - c. expressed in ampere

- d. none of the above
11. The peak value of a sine wave is 200V. It's average value is
- 127.4 V
  - 141.4 V
  - 282.8 V
  - 200 V
12. In the complex number  $(4+j7)$ , 4 is called the \_\_\_\_\_ component.
- real
  - imaginary
  - in-phase
  - quadrature
13. For a frequency of 200Hz, the time-period will be
- 0.055 s
  - 0.005 s
  - 0.0005 s
  - 0.5 s
14.  $V_{th}$  is found across the \_\_\_\_\_ terminals of the network
- Input
  - Output
  - Neither input nor output
  - either input nor output
15. Least current will flow through
- 18 ohm resistor
  - 5 ohm resistor
  - 10 ohm resistor
  - 25 ohm resistor
16. The algebraic sum of voltages around any closed path in a network is equal to
- Infinity
  - 1
  - 0

- d. Negative polarity
17. All \_\_\_\_\_ are loops but all \_\_\_\_\_ are not meshes
- loops, meshes
  - meshes, loops
  - branches, loops
  - nodes, branches
18. An ideal voltage source has
- Infinite internal resistance
  - 2 ohm internal resistance
  - Zero internal resistance
  - Very small internal resistance
19. Kirchhoff's voltage law is applied
- At a junction only
  - Across a branch only
  - In Thevenin's loop
  - In a closed electric path
20. SI unit of resistance is
- $\Omega\text{-m}$
  - $\Omega\text{-cm}$
  - $\Omega^{-1}$
  - $\Omega$

B. Very Short Question

2\*6=12


- What do you mean by extrinsic and intrinsic semiconductor?
- What will happen to PN junction diode when it is forward bias?
- Two resistors  $3\Omega$  and  $6\Omega$  are connected in parallel and this combination is connected with 22V DC supply. Estimate the total power loss in this circuit.
- An ideal voltage source of 18V is in series with a  $10\Omega$  resistor. Obtain its current source equivalent.
- An AC voltage wave is represented by ' $v = 120 \sin(314.t)$ '. Find the maximum value and frequency.
- A sinusoidal AC current wave makes 120 cycles per minute. What is its

frequency?


C Short Question

4\*7=28

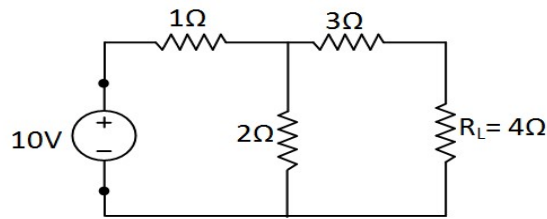1. How a Bipolar Junction Transistor is operated in CB or CE configuration? Explain with a diagram. Also, draw the output characteristics for the particular configuration.
2. Describe the working of a half wave rectifier using suitable diagrams? What do you mean by ripple factor of a rectifier?
3. What is the function of filter circuit in a voltage regulator? Explain with a diagram.
4. Calculate  $V_{th}$  for the given circuit.  $R_L = 4\Omega$  is given as the load resistance.



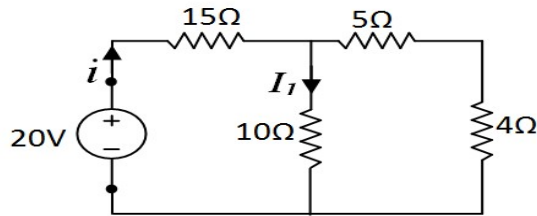5. In the circuit shown below, calculate circuit current ' $i$ ' and branch current ' $I_1$ '.



6. Given,  $A = (4-j2)$  and  $B = (1-j5)$ . Perform the operation  $A \cdot B$  and represent the result in polar form.
7. Define the following terms associated with sinusoidal AC quantities –  
Amplitude, frequency, time period and average value

\*\*\*\*\*