

END SEMESTER/ RETEST EXAMINATION, 2020

PRINCIPLES OF ELECTRICAL AND ELECTRONICS ENGINEERING

CAI – 301

MARKS: 70

Time 3 hrs.

PART A

1. Fill in the blanks:

1X10=10

- (a) In a series R-L circuit, V_L leads V_R by _____ degrees.
- (b) The number of depletion layers in a transistor is _____.
- (c) Duration of one cycle is known as _____.
- (d) The process of adding impurities to pure semiconductor is called _____.
- (e) Every mesh is a loop but every loop is not a _____.
- (f) The minimum number of wattmeter(s) required to measure 3-phase, 3 wire balanced or unbalanced power is _____.
- (g) A transformer works on _____ only.
- (h) A Zener diode is a _____ device.
- (i) The NAND gate is AND gate followed by _____ gate.
- (j) If $e_1 = A \sin \omega t$ and $e_2 = B \sin(\omega t - \phi)$, then e_2 _____ e_1 by ϕ .

2. Write True or False:

1X10=10

- (a) Semiconductor materials have covalent bonds.
- (b) A transistor is a current operated device.
- (c) When an input signal 1 is applied to a NOT gate, the output is 0.
- (d) KCL is applied in the mesh.
- (e) An n-type semiconductor is positively charged.
- (f) A semiconductor has generally 4 valence electrons.
- (g) A pn junction acts as a unidirectional switch.
- (h) A pentavalent impurity has 6 valence electrons.
- (i) The base of a transistor is lightly doped.
- (j) Kirchhoff's voltage law is applied at node or junction.



3. Choose the correct answer:

1X5=5

- (a) A semiconductor has _____ temperature coefficient of resistance.
 - (i) positive
 - (ii) zero
 - (iii) negative
 - (iv) none of the above
- (b) Without a d.c. source, a clipper acts like a
 - (i) rectifier
 - (ii) clamper
 - (iii) demodulator
 - (iv) chopper

(c) The following relationships between α and β are correct except

- (i) $\beta = \frac{\alpha}{1-\alpha}$ (iii) $\alpha = \frac{\beta}{1+\beta}$
(ii) $\alpha = \frac{\beta}{1-\beta}$ (iv) $1-\alpha = \frac{1}{1+\beta}$

(d) A trivalent impurity has _____ valence electrons

- (i) 4 (iii) 6
(ii) 5 (iv) 3


(e) If the arrow of crystal diode symbol is positive w.r.t bar, then diode is _____ biased

- (i) forward (iii) either forward or reverse
(ii) reverse (iv) none of the above

PART B

Answer Q.No.8 and any three from the rest

4. (a) Calculate the Current A2

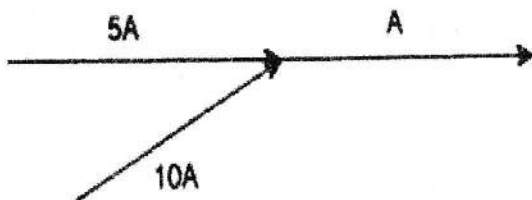

(b) Define the following terms:

Cycle, Phase difference, Current

3

(c) Compute the average and rms values of the square voltage wave shown in fig(i)

5


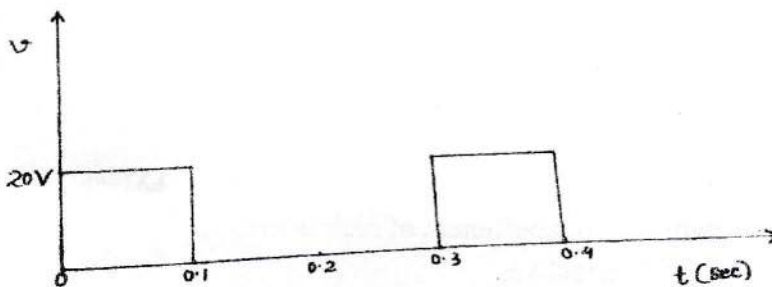


fig (i)

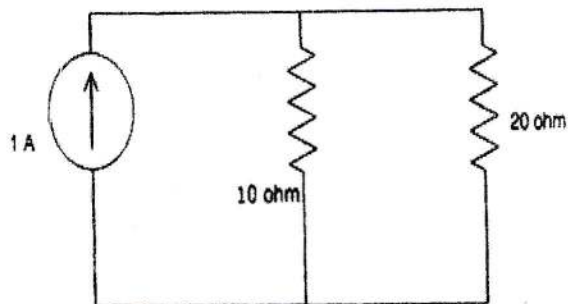

5. (a) Describe the working principle of transformer? 2

(b) Calculate the current across the 20Ω resistor 3



(c) A transformer takes a current of 0.6A and absorbs 64W when primary is connected to its normal supply 200V, 50 Hz; the secondary being open-circuit. Find the magnetising and iron loss currents. 5

6. (a) What is intrinsic and extrinsic semiconductor? 2

(b) Describe forward and reverse biasing of a pn junction. 3

(c) A crystal diode having internal resistance $r_f = 20\Omega$ is used for half-wave rectification. If the applied voltage $v = 50 \sin \omega t$ and load resistance $R_L = 800\Omega$. Find:

- (i) I_m, I_{dc}, I_{rms} (iii) a.c. power input and d.c. power
- (ii) D.C. output voltage (iv) efficiency of rectification 5

7. (a) What are the basic logic gates? What are universal gates? 2

(b) Describe the centre-tapped full-wave rectifier. 3

(c) In a common base connection, current amplification factor is 0.9. If the emitter current is 1 mA, determine the value of base current. 5

8. Write short note on (any three): 3X5=15

- (a) R-L series circuit
- (b) Relation between line current and phase currents in star connected 3-phase system.
- (c) Zener diode as voltage stabiliser
- (d) Full-wave bridge rectifier
- (e) Power measurement by two wattmeter method