

Total No. of printed pages = 10

END SEMESTER EXAMINATION – 2020

Subject Code : CAI-401

BASIC ELECTRICAL CIRCUITS

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.

*The Question Paper consists of two parts :
Part – A and Part – B. Both are compulsory.*

PART – A

Marks – 25


(All questions are compulsory.)

1. Choose the correct answer : $1 \times 15 = 15$

(a) According to KVL, the algebraic sum of all IR drops and emfs in any closed loop of a network is always

- (i) zero
- (ii) positive
- (iii) negative
- (iv) determined by battery emfs

[Turn over

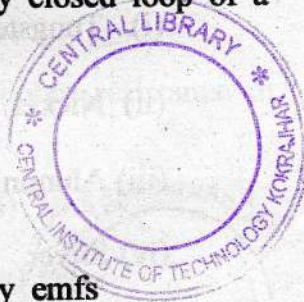

- (b) EMF in a circuit
- (i) increases circuit resistance
 - (ii) decreases circuit resistance
 - (iii) maintains potential difference
 - (iv) None of the above
- (c) The value of α (temperature co-efficient of resistance) depends on
- (i) length of material
 - (ii) x-sectional area of the material
 - (iii) volume of the material
 - (iv) nature of the material and temperature
- (d) The filament of an electric bulb is made of
- (i) Tungsten
 - (ii) Nickel
 - (iii) Aluminium
 - (iv) Silver

(e) A DC circuit usually has _____ as load.

- (i) resistance
- (ii) inductance
- (iii) capacitance
- (iv) Both inductance and capacitance

(f) Electrical appliances are not connected in series because

- (i) series circuit is complicated
- (ii) power loss is more
- (iii) appliances have different current ratings
- (iv) None of the above

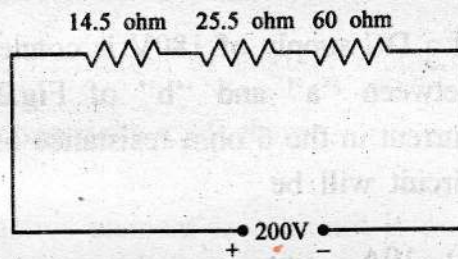


Fig.1

(g) Voltage drop across 14.5 ohm resistance in the above Fig.1 is

- (i) 29 V
- (ii) 30.5 V
- (iii) 14 V
- (iv) 18 V

6/CAI-401/BEC

(3)

[Turn over

- (j) An electric fan and a heater are marked as 100W, 220V and 1000W, 200V respectively. The resistance of heater is
- (i) zero
 - (ii) greater than that of fan
 - (iii) less than that of fan
 - (iv) equal to that of fan
- (k) Kirchoff's current law at a junction deals with
- (i) conservation of energy
 - (ii) conservation of momentum
 - (iii) conservation of angular momentum
 - (iv) conservation of charge
- (l) An active element in a circuit is one which
- (i) receives energy
 - (ii) supplies energy
 - (iii) both receives and supplies energy
 - (iv) None of the above

(h) When cells are arranged in parallel

- (i) the current capacity increases
- (ii) the current capacity decreases
- (iii) the EMF increases
- (iv) the EMF decreases

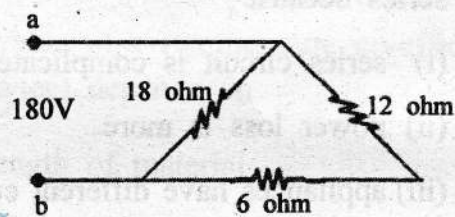


Fig. 2

(i) If a DC supply of 180V is connected across between "a" and "b" of Fig.2, then the current in the 6 ohm resistance of the above circuit will be

- (i) 10A
- (ii) 5A
- (iii) 12A
- (iv) 6A



(m) In the circuit shown below (Fig.3), there are _____ junctions.

- (i) Three (ii) Four
(iii) Two (iv) None of these

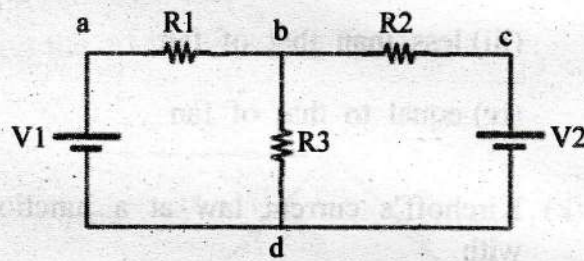


Fig. 3

(n) The circuit of Fig.3 has _____ branches.

- (i) Two (ii) Four
(iii) Three (iv) None of these


(o) The circuit of Fig.3 has _____ loops.

- (i) Two
(ii) Four
(iii) Three
(iv) None of the above



2. Write "true" or "false" : 1×5=5
- (i) Norton's theorem is the converse of Thevenin's theorem.
 - (ii) Under the conditions of maximum power transfer the efficiency is 50%.
 - (iii) Delta/Star or Star/Delta transformation technique is applied to two terminal networks.
 - (iv) The node-equation method is based directly on Kirchhoff's current law.
 - (v) A real voltage source can be converted to an equivalent real current source and vice-versa.
3. Match the resistor values in Column – A with the correct colour coding from Column – B. 1×5=5

Column – A	Column – B
(i) 200 Ω	(a) Green-Violet-Brown
(ii) 43 Ω	(b) Yellow-Violet-Red
(iii) 570 Ω	(c) Yellow-Orange-Black
(iv) 6 KΩ	(d) Red-Black-Brown
(v) 4.7 KΩ	(e) Blue-Black-Red

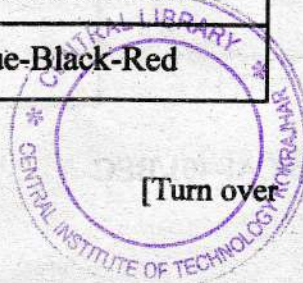


PART - B

Marks - 45


Answer any five questions. $9 \times 5 = 45$

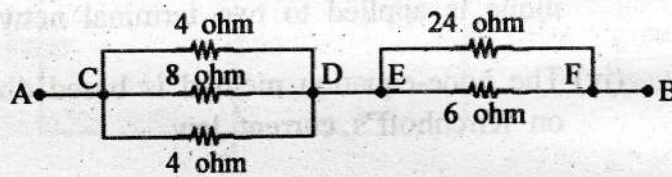4. (a) A battery having emf of 12V is connected across terminals AB of the circuit. Find
(i) current flowing in each resistance and
(ii) total power absorbed by the circuit. 6



- (b) State and explain Kirchoff's laws. 3

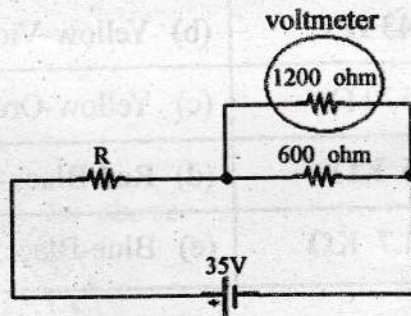5. (a) A 35V DC supply is connected across a resistance of 600 ohm in series with an unknown resistance R. A voltmeter having a resistance of 1200 ohm is connected across 600 ohm and shows a reading of 5V. Find the value of resistance R. 5




6/CAI-401/BEC

(8)

50(W)

(b) Find the voltage V_{AB} in the following circuit :

4

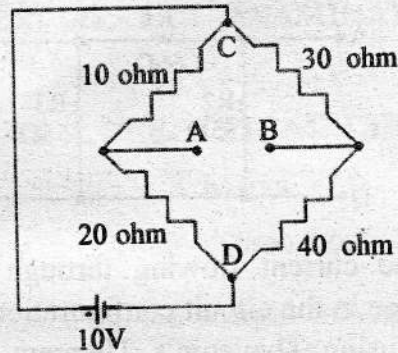

6. Prove that for a sinusoidal current

(a) $I_{rms} = 0.707I_m$

(b) $I_{av} = 0.637I_m$

9

7. (a) In a pure resistive circuit the instantaneous voltage and current are given by


$$v = 250 \sin 314t; \quad i = 10 \sin 314t$$

Determine the peak power and the average power.


4

(b) Prove that power absorbed in a pure capacitance in an AC circuit is zero.


5

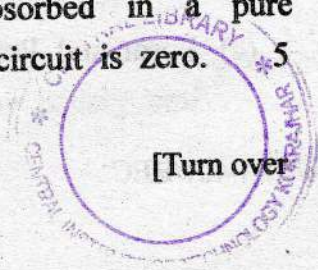

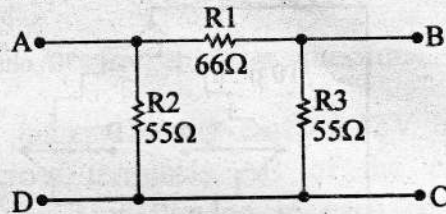8. Convert the following delta to its equivalent star connection : 9



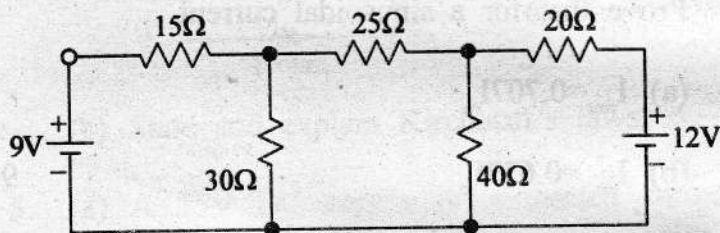9. Find the current flowing through the 25 ohm resistance in the circuit configuration of the figure below, using Thevenin's Theorem. 9



10. State and prove the "Maximum Power Transfer Theorem" mathematically as applicable to DC networks. 9

11. Write short notes on : $3 \times 3 = 9$

- (a) Power factor
- (b) Resonance
- (c) Form and Peak Factor

