

Total No. of printed pages = 8

END SEMESTER EXAMINATION – 2020

Semester : 4th

Subject Code : CAI-404

ELECTRONIC CIRCUITS AND DEVICES - I

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.

Instructions :


1. Questions of PART-A are compulsory.
2. Answer any *five* questions from PART-B.

PART – A

Marks – 25

1. Fill in the blanks : 1×10=10
 - (a) The cut in voltage for Si diode is approximately _____.
 - (b) Clipper circuits always _____ some part of the input signals.
 - (c) In a transistor lightly doped part is _____.


[Turn over

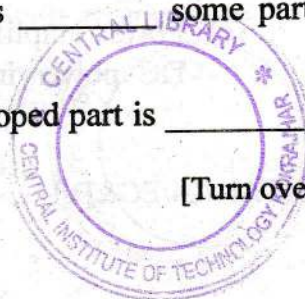

- (d) The oscillator is an amplifier with _____ feedback.
- (e) In FET channel is _____ doped.
- (f) An Ideal Op-Amp has _____ CMRR.
- (g) The push pull amplifier is free from _____.
- (h) A voltage follower has gain _____.
- (i) The function of transistor is _____.
- (j) The charge carriers in an N channel JFET are _____.

2. Write true or false : 1×10=10

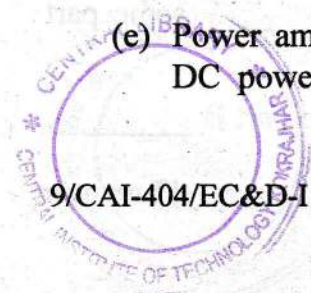
- (a) Knee voltage is defined as the forward voltage at which the current through the junction starts decreasing rapidly.
- (b) The diode depletion width shrinks in forward bias which results in having a majority flow across the junction.
- (c) In saturation region operation of a transistor both junctions are forward biased.
- (d) Common collector arrangement is generally used for impedance matching.
- (e) Power amplifier converts a part of the input DC power into AC power.



- (f) A FET differs from a bipolar transistor as it has high input impedance.
- (g) An Ideal Op-Amp has large bandwidth.
- (h) Intermediate stage of an Op-Amp provides some additional gain.
- (i) An Op-amp is a non-linear IC.
- (j) Astable multivibrator has two Quasi stable state.

3. Choose the correct answer : 1×5=5

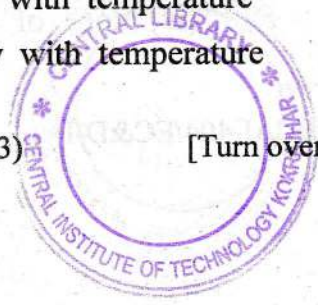- (a) The emitter of a transistor is generally doped the heaviest because it
 - (i) has to supply the charge carriers
 - (ii) has to dissipate maximum power
 - (iii) is the first region of the transistor
 - (iv) must possess low resistance
- (b) In a transistor the reverse saturation current I_{co}
 - (i) Doubles for every 1° C rise in temperature
 - (ii) Doubles for every 10° C rise in temperature
 - (iii) Increase linearly with temperature
 - (iv) Decrease linearly with temperature



(c) Negative feedback reduces distortion in an amplifier only when


- (i) it is part of its output
- (ii) it is generated within it
- (iii) it comes as a part of input signal
- (iv) it exceeds a certain safe level

(d) The common mode gain is

- (i) very high
- (ii) very low
- (iii) always unity
- (iv) None of the above

(e) Oscillator must employ

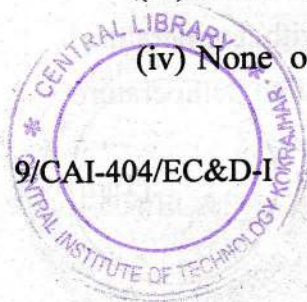
- (i) positive feedback
- (ii) negative feedback
- (iii) neither positive nor negative feedbacks
- (iv) None of the above



PART – B

Marks – 45

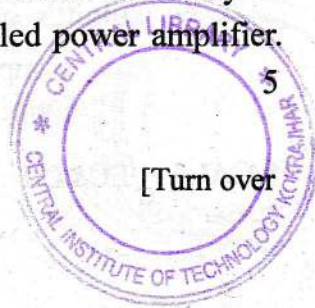4. (a) Discuss the behaviour of PN junction under no bias condition. 3
- (b) Explain the working principle of npn transistor. 4
- (c) Draw the circuit diagram of CE transistor configuration. 2
5. (a) Explain the operation of BJT as a switch. 3
- (b) What do you mean by DC load line? 1
- (c) With a neat circuit diagram explain self-bias method of transistor. 5
6. (a) What is power amplifier? Differentiate between classes A, B and C power amplifier. 1+3=4
- (b) Derive the maximum collector efficiency of class A transformer coupled power amplifier. 5



7. (a) A resistor load of 4Ω is matched to the collector impedance of an amplifier by means of a transformer having turn ratio of 50:1. The amplifier uses a DC supply voltage of 12 V in the absence of input signal. When signal is present at the base, the collector voltage swings between 24V and 2 V while the collector current swings between 0.9A and 0.04 A. Determine :

(i) Collector impedance

(ii) Signal power output

(iii) DC power input and

(iv) Collector efficiency. 4

(b) Explain the operation of push pull amplifier. 5

8. (a) What is condition for sustained oscillations ?

Draw the circuit diagram of a transistor

Colpitt's oscillator. Explain the functions of

each component. 1+5=6



(b) In a Colpitt's oscillator, the desired frequency is 500 kHz. Estimate L assuming $C = 1000 \text{ pF}$.

3

9. (a) List the ideal characteristics of an Op-amp.

4

(b) Why an Op-amp can not be used in open loop configuration for linear applications ?

2

(c) State the realistic assumptions related to an Op-amp and state their uses.


3

10. (a) Draw the circuit of non-inverting amplifier and derive the gain.

5

(b) Find the output of the following Op-amp circuit :


4

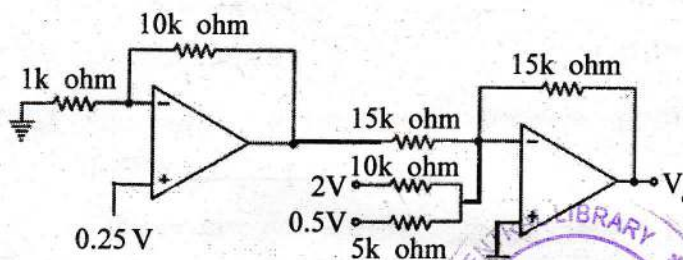

9/CAI-404/EC&D-I

(7)

[Turn over

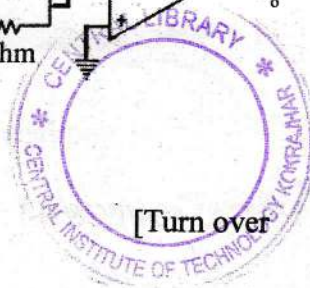

11. Explain the operation of N-channel FET and draw its characteristics. 9

12. Write short notes on any two :

(i) CMOS

(ii) Enhancement MOSFET

(iii) Bistable multivibrator

(iv) Feedback amplifier. $4\frac{1}{2} \times 2 = 9$

