

Total No. of printed pages = 7

END SEMESTER EXAMINATION-2021

Semester : 5th (New)

Subject Code : CAI-504

POWER ELECTRONICS

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Instruction :

The question paper consists of two parts : PART-A and
PART-B both are compulsory.

PART-A


Marks -25

1. Determine the correct options for the following
questions : $1 \times 10 = 10$

(i) Which is not a method of SCR turn on ?

- (a) gate triggering
- (b) dv/dt triggering
- (c) negative gate triggering
- (d) light triggering

[Turn over

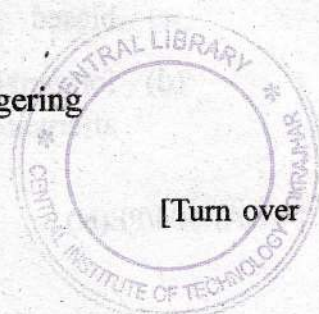

- (ii) The Schottky barrier diode has
- (a) Semiconductor-semiconductor contact
 - (b) Metal-semiconductor contact
 - (c) Metal-metal contact
 - (d) None of the above
- (iii) IGBT is a
- (a) Current controlled device
 - (b) Voltage controlled device
 - (c) Phase controlled device
 - (d) None of the above
- (iv) A single phase half wave controlled rectifier circuit has an R-load. A freewheeling diode is also in the circuit. When freewheeling diode is conducting the SCR
- (a) is forward biased
 - (b) is reverse biased
 - (c) may be forward biased or reverse biased
 - (d) forward biased initially but reverse biased afterwards

(v) Second breakdown is present in

- (a) MOSFET
- (b) BJT
- (c) IGBT
- (d) SCR

(vi) A thyristor can be protected against high dv/dt by

- (a) connecting an inductor in series with the thyristor
- (b) connecting a capacitor in series with the thyristor
- (c) connecting an inductor in parallel with the thyristor
- (d) connecting a capacitor in parallel with the thyristor

(vii) Type A chopper operates in

- (a) 4th quadrant
- (b) 2nd quadrant
- (c) 1st quadrant
- (d) 3rd quadrant

(viii) Inverter converts

- (a) AC to DC
- (b) DC to DC
- (c) AC to AC
- (d) DC to AC

(ix) The condition for step up operation for a step up/step down chopper is

(a) $0 \leq \alpha \leq 0.5$ (b) $0.5 \leq \alpha \leq 1$

(c) $\alpha = 0$ (d) $\alpha = 1$

(x) In a step down chopper, if $V_s = 100$ V and the chopper is operated at a duty cycle of 75%. Find the output voltage.

(a) 100 (b) 75

(c) 50 (d) 0

2 State whether the following statements are true or false : 1×10=10

(i) GTO can be turned off by applying a negative gate pulse.

(ii) A TRIAC has 6 semiconductor regions.

(iii) UJT is a three terminal device.

(iv) The equivalent circuit of IGBT consists of two BJTs.

(v) SCR remains turned on after removal of the gate signal.

(vi) Type E chopper is a 2 quadrant chopper.

(vii) The peak inverse voltage of bridge rectifier is one-fourth of peak inverse voltage of midpoint rectifier.

(viii) In 180° mode of operation of a 3 phase bridge inverter, two thyristors conduct at one time.

(ix) In a chopper circuit the output voltage can be varied by varying duty cycle.

(x) Output of a phase controlled rectifier will be same as the output of a diode rectifier if firing angle, $\alpha = 90^\circ$.

3 Fill in the blanks :

1×5=5

(i) BJT has _____ on state loss compared to MOSFET. (higher/lower/equal)

(ii) Holding current of SCR is _____ than latching current. (higher/lower/equal)

(iii) _____ has negative resistance region in its I-V characteristics. (BJT/UJT/IGBT)

(iv) Cycloconverter converts _____ from one level to another level. (voltage/current/frequency)

14/CAI-504/PE(N)

(5)

[Turn over



(v) Duty cycle of a chopper is _____.

$$\left(\frac{T_{\text{on}}}{T_{\text{off}}} / \frac{T}{T_{\text{on}}} / \frac{T_{\text{on}}}{T} \right)$$

PART-B

Marks - 45

- 4 A DC battery is charged through a resistor R as shown in Fig. 1. Derive an expression for average value of charging current in terms of V_m , E, R etc. on the assumption that the SCR is fired continuously. 9

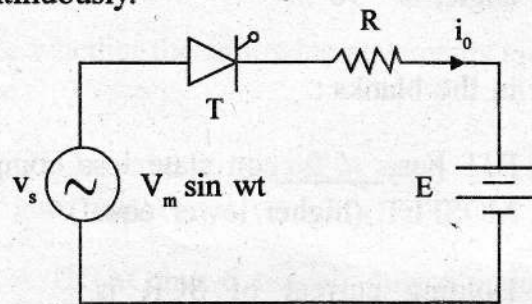


Fig. 1

- (i) For an AC source of 230V, 50Hz find the value of average charging current if $R = 8\Omega$ and $E = 150V$.
- (ii) Find the power supplied to the battery and that dissipated in the resistor.
- (iii) Calculate the supply pf.

- 5 For a type a chopper of Fig. 2, DC source voltage = 230V and load resistance = 10Ω . The voltage drop across the chopper is 2 V when it is on. For a duty cycle of 0.4 calculate 6

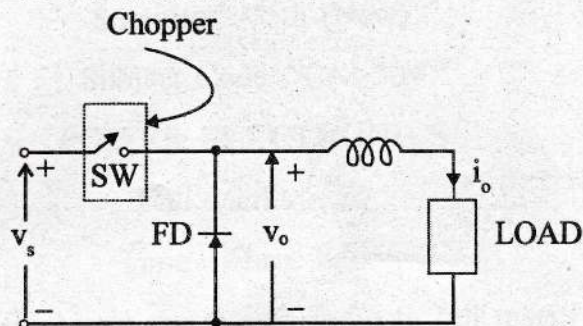


Fig. 2

- (i) average and rms values of output voltage
(ii) chopper efficiency.
- 6 What is an Cycloconverter ? Explain the working principle of a single phase to single phase step up cycloconverter. 10
- 7 Explain the working of a single phase halfwave converter drive for DC motor control. 8
- 8 Give the steady state analysis and draw the load voltage and current waveforms of a single phase bridge inverter for R-load, RL-load and RLC-load.

$7+1+1+1+2=12$

