

Total No. of printed pages = 4

CAI-504/PE/5th Sem/2016/N

## POWER ELECTRONICS

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

1. (a) What do you mean by cut-in voltage of a diode? Describe the reverse recovery characteristics of a diode and define its softness factor. 1+4=5
- (b) What do you understand by the term 'second breakdown' in power transistor? 2
- (c) Explain the significance of junction temperature in semiconductor devices. 2
- (d) Explain the different modes of operation of SCR with the help of its I-V characteristics. 5

[Turn over

2. (a) The intrinsic stand-off ratio of a UJT is 0.67. If  $R_{B_1} = 4 \text{ K}\Omega$ , find the value of  $R_{B_2}$ .

2

- (b) In the figure 1 given below, the maximum gate current ( $I_{gm}$ ) and voltage ( $V_{gm}$ ) of the SCR are 200 mA and 2V respectively. Determine :

4+4=8

- (i)  $R_1$  and  $R_2$  so that  $I_{gm}$  and  $V_{gm}$  do not exceed their maximum ratings.
- (ii) Find a suitable value for  $R_2$  so that the firing angle will be  $60^\circ$ , if the gate turn-on voltage  $V_{gt} = 0.8\text{V}$ .

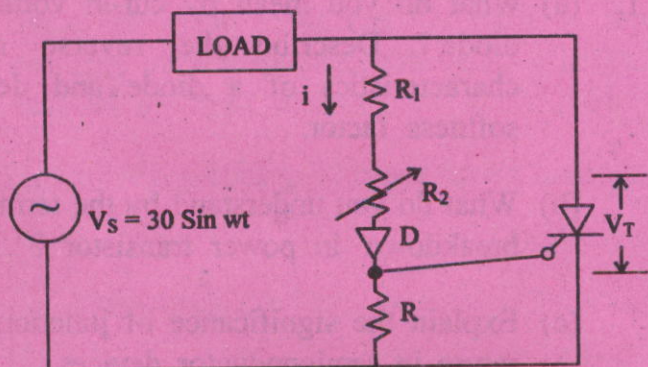


Figure - 1

- (c) Describe the method of line commutation to turn-off a thyristor.

4



3. (a) With the help of voltage and current waveforms, explain the working of single phase half-wave circuit with R-L load. 8

(b) In the circuit given below, the thyristor 'T' is turned on at  $t = 0$ . Determine : 6

(i) resonant frequency of the circuit

(ii) conduction time of thyristor

(iii) voltage across thyristor after it is turned off.

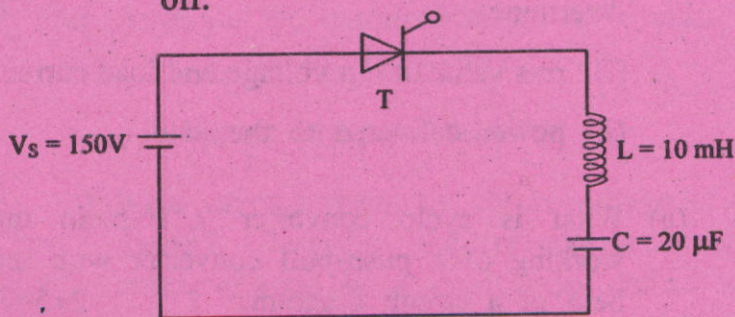


Figure - 2

4. (a) What is the function of chopper ? Explain its principle of operation. 1+4=5

(b) For a type A chopper, calculate the average and rms values of output voltage and chopper efficiency, if D.C source = 200V, Load  $R = 10\Omega$ , Duty cycle = 0.4 and Voltage drop across chopper when it is on 2V. 6

- (c) Mention some advantages of a single phase full-bridge inverter over half-bridge inverter. 3
5. (a) Explain the working of a single phase half-wave A.C voltage controller. 10
- (b) A single phase half-wave A.C voltage controller feeds a load of  $R = 20\Omega$  with an input voltage of 230V, 50 Hz. If both the thyristors are fired at an angle of  $45^\circ$ , determine : 4
- (i) rms value of o/p voltage and load current
- (ii) power delivered to the load.
6. (a) What is cyclo converter ? Explain the working of a push-pull converter with the help of a circuit diagram. 2+5=7
- (b) Explain the working of basic series inverter. 7
7. Explain the working of any *two* : 7×2=14
- (a) GTO
- (b) TRIAC
- (c) PUT.