

Total No. of printed pages = 6

CAI-2201/BEC/4th Sem/2013

## BASIC ELECTRICAL CIRCUITS


Full Marks – 100

Pass Marks – 30

The figures in the margin indicate full marks for the questions.


Answer any *five* questions.

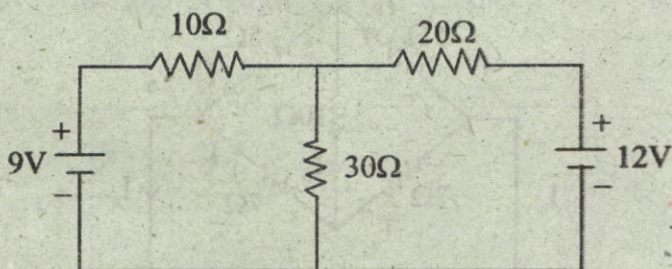1. (a) Find the value of loop currents  $I_1, I_2$  using loop current method. 10




[Turn over

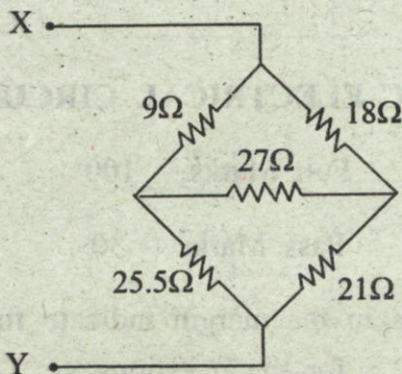- (b) Using  $\Delta \rightarrow \lambda$  transformation, find the equivalent resistance between terminals X and Y. 10



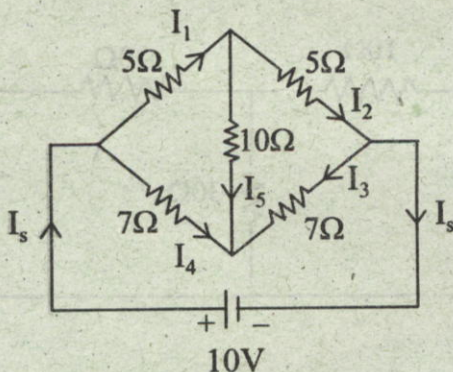2. (a) Find the value of currents  $I_1, I_2, I_3, I_4, I_5$  and  $I_s$  by Kirchoff's law. 10







(b) State and explain Kirchoff's current and voltage law. 6

(c) Write the statement of Ohm's Law. Give a suitable example. 4

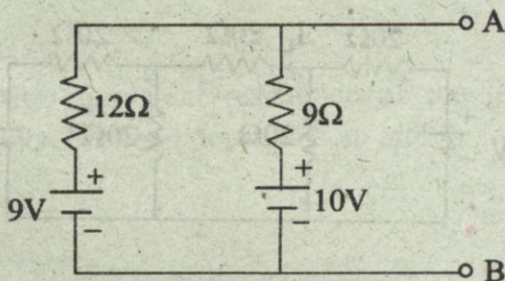3. (a) Convert the following circuit to an circuit containing one current source and resistance. 10



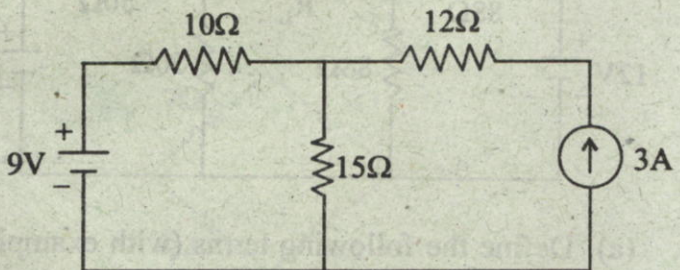(b) Using superposition theorem, find the current flowing through  $15\Omega$  resistance. 10



4. (a) Use Thevenin's theorem to verify your answer of the previous question [3(b)].


10

- (b) State and prove maximum power transfer theorem.

10


5. (a) Using Nodal analysis find the load current  $I_L$ .

10

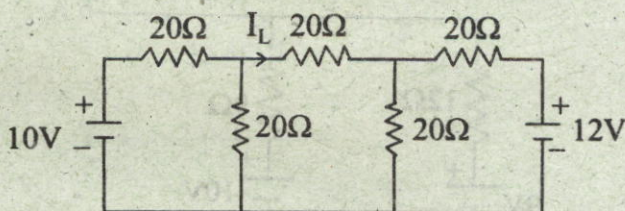

- (b) Find the value of  $R_L$  which will extract maximum power from the circuit.

10

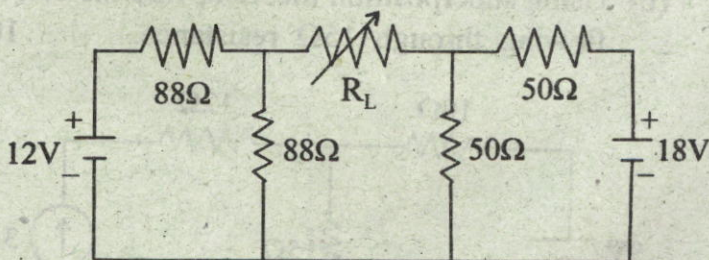


6. (a) Define the following terms (with examples) :

Loop, Mesh, Bilateral circuit, Junction, Node.

10



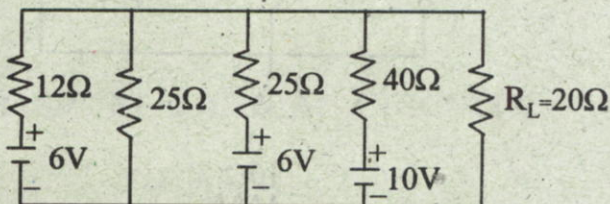- (b) Use Millman's theorem to find out the current flowing through  $20\Omega$  resistance. 10



7. Find the equivalent resistance of the following networks between terminals a and b :

$$5 \times 4 = 20$$

