

Total No. of printed pages = 4

CAI-301/PE&EE/3rd Sem/2013/M

**PRINCIPLES OF ELECTRICAL AND  
ELECTRONICS ENGINEERING**

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks  
for the questions.

Answer question No. 1 and any *four* from the rest.

1. Fill in the blanks : 1×10=10

(i) The direction of induced emf can be found  
by \_\_\_\_\_ law.

(ii) A Zener diode operates on \_\_\_\_\_ bias.

(iii) The maximum value of an alternating current  
is 50A. Its RMS value will be \_\_\_\_\_.

(iv) Total number of electrons in the outermost  
shell of germanium is \_\_\_\_\_.

(v) Conversion of AC to DC is called \_\_\_\_\_.

(vi) In series resonance, current in the circuit is  
\_\_\_\_\_.

[Turn over

- (vii) The unit of angular velocity is \_\_\_\_\_.
- (viii) Electron-volt is the unit of \_\_\_\_\_.
- (ix) A pentavalent impurity has \_\_\_\_\_ valence electrons.
- (x) In pure capacitive circuits, voltage \_\_\_\_\_ the current.

2. (a) What do you mean by an ideal transformer? 2

(b) An ideal 25 KVA transformer has 500 turns on the primary winding and 40 turns on the secondary winding. The primary is connected to 3000 Volt, 50 Hz supply.

Calculate :

(i) Primary and secondary currents on full-load

(ii) Secondary emf and

(iii) The maximum core flux. 8


(c) Derive the emf equation of a transformer. 5

3. (a) Show that in a pure inductive circuit current lags behind the voltage by  $90^\circ$ . 5

- (b) A choke coil takes a current of 2.5A when connected across 250V, 50 Hz mains and consumes 400 watts.

Find :

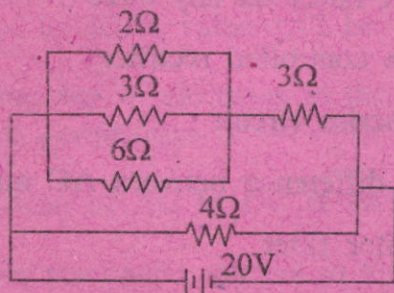- (i) The power factor  
(ii) Resistance of the coil  
(iii) Inductance of the coil. 5
- (c) Prove that the average value of alternating current in a complete cycle is zero. 5
4. (a) A battery consisting of 10 cells in series has two of the cells reversed. EMF of each cell is 1.5V and internal resistance is  $0.1\Omega$ . The resistance of the external circuit is  $4\Omega$ . Find the reduction in current due to the two cells being reversed connected. 6
- (b) For the following circuit, calculate the power loss in the  $2\Omega$  resistor. 9



5. (a) Write any three properties of semiconductors. 3
- (b) What do you mean by doping ? Explain how a p-type semiconductor material can be formed from intrinsic semiconductor by the process of doping. 7
- (c) With neat diagram, explain the behaviour of a PN-junction in reverse bias mode. 5
6. (a) What are the different characteristics of a transistor in CB-mode ? Explain with necessary diagrams. 7
- (b) With neat circuit diagram, explain the operation of a npn-transistor in CB-mode. 4
- (c) The base current in a transistor is 0.01 mA and emitter current is 1 mA. Calculate the values of  $\alpha$  and  $\beta$ . 4
7. Write short notes on any *three* : 5×3=15
- (a) Silicon controlled rectifier
- (b) RLC series circuit
- (c) Phase difference between AC quantities
- (d) Capacitor filter
- (e) Series resonance.