

Total No. of printed pages = 4

CAI-301/PEEE//3rd Sem/2013/N

**PRINCIPLES OF ELECTRICAL AND
ELECTRONICS ENGINEERING**

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Answer any *five* questions.

1. (a) Define ampere. 1

- (b) Force between two parallel conductors carrying currents in opposite direction is 3.2 N/m when they are placed 50 mm apart in air. If current flowing in one conductor is 1000 A , find the current in the other conductor. Mention whether it is a force of attraction or repulsion. 6

[Turn over

- (c) An electric kettle needs 6 minutes to boil 2 kg of water from the initial temperature of 20°C . The cost of electrical energy required for this operation is 12 paise, the rate being 40 paise per kwh. Find the kw rating and the overall efficiency of the kettle. 7
2. (a) Define the following terms : 2
- (i) Form factor
- (ii) Average value.
- (b) A tungsten filament bulb rated at 500W, 100V is to be connected to series with a capacitance across 200V, 50 Hz supply. Calculate :
- (i) The value of capacitor such that the voltage and power consumed by the bulb are according to the rating of the bulb.
- (ii) P.f. of the circuit.
- (iii) Draw the phasor diagram. 6
- (c) The following three vectors are given :
- $A = 20 + i20$, $B = 30 \angle -120^{\circ}$, $C = 10 + i10$.
- Perform the following indicated operations
- (i) $\frac{AB}{C}$ (ii) $\frac{BC}{A}$ 6

3. (a) Mention four important properties of semiconductor materials. 4
- (b) With neat diagram, explain the operation of a full-wave bridge rectifier. 6
- (c) Explain the operation of a clamping circuit. 4
4. (a) Establish a relation between α and β . 3
- (b) Explain the operation of a NPN transistor. 6
- (c) What do you mean by forward blocking mode of a thyristor? 5
5. (a) A platinum coil has a resistance of 3.146Ω at 40°C and 3.767Ω at 100°C . Find the resistance at 0°C and the temperature co-efficient of resistance at 40°C . 6
- (b) A resistance R is connected in series with a parallel combination of two resistances of 12Ω and 8Ω . Calculate R if the total power dissipated in the circuit is 70W , when the applied voltage is 20V . 8
6. (a) What are the indications of a fully charged lead-acid cell? 4

(b) Write in brief any three characteristics of a lead-acid cell. 5

(c) It is desired to charge a 12V car battery at 6A from a 230V, dc source. The dc source and battery are connected in series with a group of 60W 220V bulbs in parallel. How many lamps are required for the purpose? 5

7. Write short notes on any two : $7 \times 2 = 14$

(a) Zener diode

(b) Lagging and leading power factor

(c) Choke input filter

(d) Pure capacitive circuit with sinusoidal AC voltage source.