

Total No. of printed pages = 4

CAI-301/PEEE/3rd Sem/2014/N

**PRINCIPLES OF ELECTRICAL AND  
ELECTRONICS ENGINEERING**

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks  
for the questions.

Answer any *five* questions.

1. (a) What do you mean by specific resistance of a material ? What is its unit ? 1+1=2
- (b) Find the resistance of 1000 meters of copper wire 25 sq.mm in cross-section. The resistance of copper is 1/58 ohm per meter length and 1 sq.mm cross-section. What will be the resistance of another wire of the same material, three times as long and one-half of the cross-sectional area ? 12

Or

- (a) What do you mean by temperature coefficient of resistance ? 2

[Turn over

- (b) A  $50\ \Omega$  resistor is in parallel with a  $100\ \Omega$  resistor. The current in  $50\ \Omega$  resistor is  $7.2\text{A}$ . What is the value of third resistance to be added in parallel to make the line current  $12.1\text{A}$  ? 6
- (c) A pure resistance is connected across an AC voltage source. Show that the circuit current and voltage are in same phase. 6
2. (a) Write the KCL and KVL and explain with necessary diagrams.  $2+2=4$
- (b) A Wheatstone bridge ABCD is arranged as follows :  $AB = 20\ \Omega$ ,  $BC = 5\ \Omega$ ,  $CD = 4\ \Omega$  and  $DA = 10\ \Omega$ . A galvanometer of resistance  $6\ \Omega$  is connected between B and D. A  $10\text{V}$  DC supply of negligible resistance is connected between A and C with A +ve. Find the magnitude and direction of galvanometer current. 10

Or


- (a) In a certain  $50\ \text{kVA}$  transformer, the number of turns on the primary and secondary windings are 834 and 58 respectively. If primary is connected to a  $3300\text{V}$  supply, find
- (i) secondary voltage
- (ii) primary and secondary currents when the transformer is fully loaded. Neglect the losses.  $5+5=10$



(b) Derive the EMF equation of a 1- $\phi$  transformer.

4

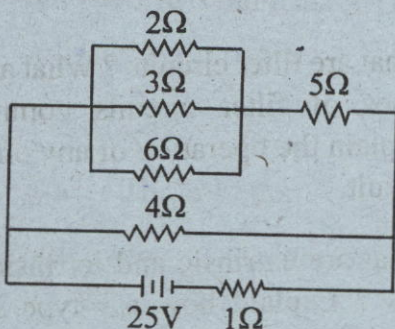3. (a) For the following circuit, calculate the power loss in the  $2\Omega$  resistor. 8



- (b) Express the following in polar form with diagrams : (i)  $6 - j8$  (ii)  $-50 - j75$ .

3+3=6

4. (a) Define the following : 3

- (i) Time period
- (ii) Maximum value
- (iii) Form factor.

- (b) An alternating current is given by  $i = 141.4 \sin 314t$ , calculate 4

- (i) maximum value
- (ii) frequency
- (iii) time period
- (iv) instantaneous value.

- (c) A series circuit consists of a resistor of  $10\Omega$ , an inductor having an inductance of  $0.159\text{H}$  and a capacitor having a capacitance of  $1.06 \times 10^{-4}\text{F}$ . It is connected to a  $230\text{V AC}$  supply. Calculate (i) circuit current (ii) the power consumed (iii) the power factor. 7
5. (a) What are filter circuits? What are the different types of filter circuits commonly used? Explain the operation of any one type of filter circuit. 8
- (b) What are extrinsic and intrinsic semiconductors? Explain how a p-type semiconductor can be formed from intrinsic semiconductor by the process of doping. 6
6. (a) Explain the following terms related to SCR.  
(i) Breakover voltage (ii) Forward current rating.  $2+2=4$
- (b) With the help of a neat circuit diagram, explain the characteristics of common emitter connecting of a NPN transistor. 10
7. Write short notes on any two :  $7 \times 2 = 14$
- (a) Series resonance
- (b) Full-wave rectifier
- (c) Semiconductors.