Total No. of printed pages = 4 CAI-301/POE&EE/3rd Sem/2015/M

PRINCIPLES OF ELECTRICAL AND ELECTRONICS ENGINEERING

Full Marks - 70

Pass Marks – 28

Time - Three hours

The figures in the margin indicate full marks for the questions.


Answer any five questions.

1. (a) What do you mean by heating effect of electric current? Explain with an example.


5

- (b) An electric kettle marked 1 kW, 230V takes 7.5 minutes to bring 1 kg of water at 15°C to boiling point. Find the efficiency of the kettle.
- (c) Explain the Fleming's left hand rule.

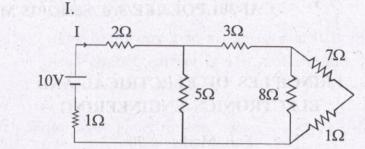2. (a) In the following circuit, calculate the current



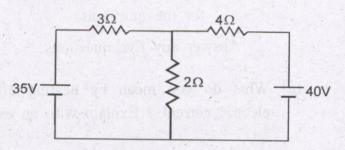(b) Write Kirchhoff's current law and Kirchhoff's voltage law. Calculate the current in each resistor in the given circuit using KCL and KVL. 2+2+6=10



- 3. (a) A resistance of 5Ω is connected in series with a pure inductance of 0.01H to a 100V, 50 Hz supply. Calculate:
 - (i) impedance
 - (ii) current and
 - (iii) power absorbed.

C

(b)	Define the following terms: 5
	(i) Instantaneous value
	(ii) RMS value
	(iii) Cycle
	(iv) Peak factor
	(v) Average value.
(a)	Write the different characteristics of a lead
	acid cell. 5
(b)	Write the names of different parts of a lead
	acid cell. 5
(c)	What are the indications of a fully charged
	lead acid cell?

5. (a) Explain the working of PN junction diode in forward and reverse bias mode. 6

(b) Explain the operation of full-wave bridge type rectifier with necessary diagrams. 8

6. (a) What are the different types of transistor connections? Discuss the CB-connection for NPN transistor with necessary diagrams.

10

4.

(b) What do you mean by leakage current in PN junction?

The base current in a transistor is 0.01 mA and emitter current is 1 mA. Calculate the values of α and β . 1+3=4

- 7. Write short notes on any two: $7 \times 2 = 14$
 - (a) RC series circuit with sinusoidal supply
 - (b) Significance of J-operator
 - (c) Zener diode.