

Total No. of printed pages = 7

CAI-301/POE&EE/3rd Sem/2017/N

**PRINCIPLES OF ELECTRICAL AND
ELECTRONICS ENGINEERING**

Full Marks - 70

Pass Marks - 28

Time - Three hours

The figures in the margin indicate full marks
for the questions.

PART - A

1. Pick up the right answer : $10 \times 2 = 20$
- (a) Kirchoff's Current law is applicable only in
- (i) closed loops in a network
 - (ii) electronic circuit
 - (iii) junctions in a network
 - (iv) electric circuits.
- (b) Kirchoff's voltage law is concerned with
- (i) IR drops
 - (ii) Battery emf
 - (iii) Junction voltages
 - (iv) Both (i) and (ii) above.

[Turn over

- (c) According to KVL, the algebraic sum of all IR drops and emfs in any closed loop of a network is always
- (i) zero
 - (ii) positive
 - (iii) negative
 - (iv) determined by battery emfs.
- (d) The algebraic sign of an IR drop is primarily dependent upon the
- (i) amount of current flowing through it
 - (ii) value of R
 - (iii) direction of current flow
 - (iv) battery connection.
- (e) What is the relation between energy and power ?
- (i) Energy = Power - Time
 - (ii) Energy = Power \times Time
 - (iii) Energy = Power + Time
 - (iv) Energy = Power \div Time.

(f) The unit of work is

- (i) Watt
- (ii) Joule
- (iii) Calorie
- (iv) Second.

(g) The unit of power is

- (i) Watt
- (ii) Joule
- (iii) Calorie
- (iv) Second.

(h) The polar form of $-5 - 6j$ is

- (i) $7.81 \angle 50.18^\circ$
- (ii) $11 \angle 30.8^\circ$
- (iii) $10.7 \angle -11.8^\circ$
- (iv) $7.81 \angle -129.8^\circ$

(i) If a 220 V heater is used on 110 V supply, heat produced by it will be

- (i) One-half
- (ii) Twice
- (iii) One-fourth
- (iv) Four times.

(j) Active materials of a lead acid cell are :

- (i) Lead peroxide
- (ii) Sponge lead
- (iii) Dilute sulphuric acid
- (iv) All of the above.

2. Fill in the blanks : 5 × 1 = 5

- (a) The capacity of a cell is measured in _____.
- (b) After doping semiconductor, material is known as _____ material.
- (c) Two windings of a transformer are designated as primary winding and _____ winding.

- (d) Transformer action requires _____ magnetic flux.
- (e) Rating of transformers is expressed in _____.


PART - B

Answer any *five* questions from the following :

5×9=45

3. (a) What do you mean by phase difference ?
Explain with suitable example. 4
- (b) An alternating current of frequency 50Hz has a maximum value of $200\sqrt{2}$ A. Reckoning the time from the instant the current is zero and becoming positive. Find the time taken by the current to reach a value of 141.4 A for a first and second time. 5
4. Do the following operation : 3×3=9
- (a) $(5\angle 150^\circ) \div 4j$
- (b) $(5\angle 30^\circ) + (-3 + 4j)$
- (c) $(-5 + 5j) - (5\angle -30^\circ)$.

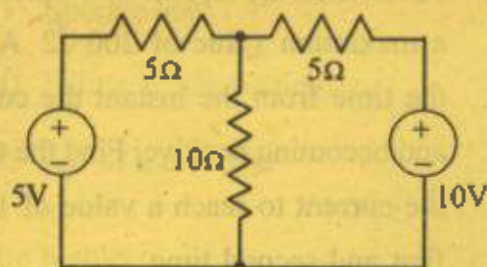5. (a) What is an ideal transformer ? 4
- (b) The emf per turn for a single phase, 2310/220V, 50 Hz transformer is approximately 13 volts. Calculate the number of primary and secondary turns. 5
6. (a) Write the statement of KCL and KVL. 4
- (b) Calculate the current flowing through the 10Ω resistance of the following figure : 5



7. (a) Write about the different parts of a lead-acid battery. 4
- (b) Write the chemical changes during discharging and charging of a lead-acid cell. 5

8. (a) Draw the circuit diagram of a bridge rectifier, together with its input and output waveforms.

4

- (b) Calculate the values of collector current I_C and emitter current I_E for a BJT with emitter-to collector current gain $\alpha_{ec} = 0.97$ and base current $I_B = 50\mu\text{A}$. Determine base-to collector gain β_{ec} for the device.

5