

Total No. of printed pages = 3

CAI-303/DC/3rd Sem/2013/M

## DIGITAL CIRCUITS

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

1. (a) Convert the following : 2×3=6

(i)  $65_{10}$  into BCD code

(ii)  $11101101_2$  into Gray code

(iii) 30 (decimal to Excess-3 code).

(b) Define and give the truth tables for OR, EXOR and NOR gates. What type of gate is equivalent to a NAND gate followed by an inverter ? 8

[Turn over

2. (a) Reduce the following Boolean expressions :

(i)  $\overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$

(ii)  $\overline{A}B\overline{C} + B + B\overline{D} + A\overline{B}\overline{D} + \overline{A}C$       3+3=6

(b) Describe the operation of following arithmetic circuits :      5+3=8

(i) Full adder

(ii) Half subtractor.

3. (a) Reduce the following expression using K-map and implement it.      5

$\sum m(5, 6, 7, 9, 10, 11, 13, 14, 15)$

(b) What do you understand by even and odd parity ?      2

(c) What is an even parity generator ?      3

(d) What are SOP and POS forms of Boolean expression ?      4

4. (a) What do you mean by combinational circuit ? Describe the operations performed by the following circuits :      10

(i) Decoder

(ii) Encoder.

- (b) Design a circuit for a demultiplexer and explain its working. 4
5. (a) Explain the difference between a sequential system and combinational systems giving example of each. 5
- (b) Describe the working of a RS flip-flop. How it differs from D flip-flop ? 5
- (c) Explain the working of a JK flip-flop. 4
6. (a) What do you understand by a register ? Explain the working of a serial-in-serial out shift register.  $2+5=7$
- (b) What is a counter ? What is MOD of a counter ? Draw a MOD-3 binary counter.  $2+2+3=7$
7. Write short notes on any *two* :  $7 \times 2 = 14$
- (i) PROM
- (ii) Multiplexer
- (iii) DTL
- (iv) CMOS.