

Total No. of printed pages = 5

CAI-303/DC/3rd Sem/2018/M

## DIGITAL CIRCUITS

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks  
for the questions.

### PART – A

(Compulsory)

Marks – 25

1. (i) Covert the following : 4

(a)  $(15)_{10} = (\dots)_2$

(b)  $(A10)_{16} = (\dots)_2$

(c)  $(1001)_2 = (\dots)_{10}$

(d)  $(11F)_{16} = (\dots)_{10}$

[Turn over

(ii) Answer the following questions :  $1 \times 10 = 10$

- (a) Obtain the 2's complement of 100100.
- (b) Represent the decimal number 12 in BCD code .
- (c) Number of control inputs needed to implement 16:1 multiplexer is \_\_\_\_\_.
- (d) Write down 2 bit gray code sequence .
- (e)  $1101 \times 101 =$  \_\_\_\_\_.
- (f) Number of outputs present in 1:8 Demultiplexer is \_\_\_\_\_.
- (g)  $A + ABC =$  \_\_\_\_\_.
- (h) Find out the min term, if the variables a,b,c, is taking values 0,1,0.
- (i) Subtracted value of  $10110 - 01101$  is \_\_\_\_\_.
- (j) Find out the max term, if the variables a, b, c, is taking values 0,1,1.

(iii) Write down whether the following statements are true/false :  $1 \times 11 = 11$

- (a) D-latch is a combinational circuit.
- (b)  $x + y = y + x$  is an example of commutative law.

- (c) Multiplexer is a data selector circuit.
- (d) Half Adder can be used to add 2 bits.
- (e) 3 bit register can count upto 16.
- (f) Asynchronous circuit uses external clk to enable all the circuit.
- (g) If two inputs of a xor gate is 1 then the output is 0.
- (h)  $x + x' = 0$ .
- (i) ASCII code is an example of alphanumeric code.
- (j)  $(x'y'x')' = xyz$ .
- (k)  $(x+x'y')(x+x'y) = x$ .

### PART - B

Answer any *three* questions.

1. (i) Simplify using Boolean algebraic method :

$$2 \times 2 = 4$$

(a)  $abc' + ab'c' + a'b'c + ab'c + a'bc$

(b)  $(x+y'+z')' + (x'y'z)' + xy$

(ii) Simplify using K-map method:  $5+6=11$

a)  $f(w,x,y,z) = \sum m(2,4,5,6,9,10,11,12,13)$

(b)  $f(a,b,c,d) = \sum m(0,1,2,3,4,5,6,12,13) + d(7,8)$

2. (i) Use basic gates to implement  $Y = ab'(c+d) + ab(c'+d)$  3

(ii) Use NAND gate only to implement  $Y = ab + cd$  4

(iii) Prove that  $(a+b+c)' = a' \cdot b' \cdot c'$  (ii) 3

(iv) Why NAND, NOR gates are called universal gate. 2

(v) Write down distributive, commutative, associative law of boolean algebra. 3

3. (i) Design a Full Adder. 6

(ii) Write down truth table of a 2 to 4 Decoder. 2

(iii) Write down function table of a 4:1 Multiplexer. 2

(iv) Distinguish between combinational and sequential circuits. 3

(v) Use Nor gate only to implement  $Y = a+b$ . 2

4. (i) Explain the operation of S-R latch with circuit diagram, truth table. 5
- (ii) Draw the logic diagram of a J-K latch. 2
- (iii) Explain the operation of a master slave flip-flop with logic diagram, truth table. 6
- (iv) Draw the logic diagram of a D latch. 2
5. (i) Describe the function of a 3 bit Counter with block diagram, timing diagram. 10
- (iii) Design a 1:8 De-Multiplexer. 5
6. (i) Use 1's Complement method to subtract 1110 - 1001. 2
- (ii) Describe the functions of a 3 bit Register with block diagram, timing diagram. 10
- (iv) What do you mean by binary coding. Explain with example. 3