

Total No. of printed pages = 4

CAI-303/Digital Circuits/3rd Sem/2014/N

## DIGITAL CIRCUITS

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

1. (a) Using Boolean algebra, simplify the following expressions as much as possible.  $2 \times 2 = 4$

(i)  $A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}C$

(ii)  $AB + \overline{AB}C + A$

- (b) Draw the logic circuit represented by below expression

$$Y = A + B [ C + D(B + \bar{C})] \quad 3$$

- (c) Use K-map method to simplify the following Boolean function : 5

$$Y = f(w, x, y, z) = \sum m (0, 2, 4, 5, 8, 10, 12, 14, 15)$$

[Turn over

(d) (i) Convert  $(1001)_2$  to decimal.

(ii) Convert  $(DAF1)_{16}$  to binary.  $1 \times 2 = 2$

2. (a) Show how the following expressions can be implemented using NAND gate only.

(i)  $Y = ABC$  (ii)  $Y = \overline{ABC}$ .  $3 \times 2 = 6$

(b) Show how the following expressions can be implemented using NOR gate only.

(i)  $Y = A + B$  (ii)  $Y = A + B + \bar{C}$   $3 \times 2 = 6$

(c) Use basic gates to implement  $Y = AB + \bar{B}C$ .  $2$

3. (a) Implement Half Adder logic circuit.  $5$

(b) Show how a 2 to 4 decoder logic circuit can be implemented starting from its truth table.  $5$

(c) (i) Convert decimal 26 to BCD.  $1 \times 2 = 2$

(ii) Convert BCD 10101011 to decimal.

(d) Apply DeMorgan's law to

$Y = \overline{\overline{A+B+C} + \bar{d}.b}$   $2$

4. (a) Design a 4:1 multiplexer logic circuit starting from its function table. 6
- (b) Describe the truth table of a S-R latch. 3
- (c) Draw the logic diagram of J-K latch and describe its truth table. 3+2=5
5. (a) Draw the block diagram of 2 bit binary parallel adder. 3
- (b) Use 1's complement method to perform the subtraction  $1010 - 0100$ . 3
- (c) Use K-map method to simplify  
 $Y = f(x, y, z) = \sum m(0, 2, 4)$  with don't care conditions  $d(3, 5)$ . 5
- (d) Convert  $f(x, y, z) = xy + x'y'$  to canonical SOP form. 2
- (e) 2's complement of 10010001 is ..... 1
6. (a) Explain the operation of a 2 bit ripple counter with block diagram, timing diagram. 7
- (b) What are the main differences between synchronous and asynchronous logic? 3

- (c) Describe the truth table of D-latch. . . . . 3
- (d) Multiplied value of  $101 \times 11$  is ..... . 1
7. (a) Implement full subtractor circuit. 7
- (b) Design a 4 to 2 encoder logic circuit starting from its truth table. 5
- (c) Convert  $(243)_8$  to binary. 1
- (d) Convert  $(40)_{10}$  to binary. 1