

Total No. of printed pages = 6

CAI-401/BEC/4th Sem/2013/M

## BASIC ELECTRICAL CIRCUITS


Full Marks – 70

Pass Marks – 28


The figures in the margin indicate full marks for the questions.

Answer question No. 1 and any *four* from the rest.

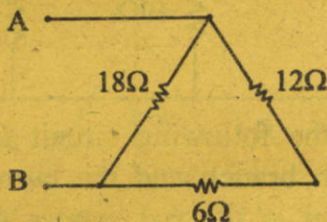1. (a) If d.c supply of 180V is connected across the terminals AB in the following figure, then what will be the current flowing through  $6\Omega$  resistance ? 3



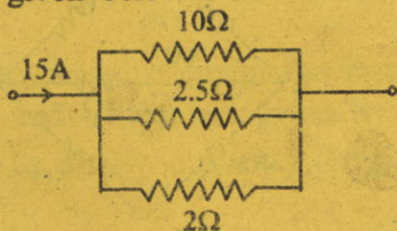
- (b) Find the voltage drop across the parallel circuit given below : 3



[Turn over


- (c) Using superposition theorem, find the current in each branch of the network shown below :

8

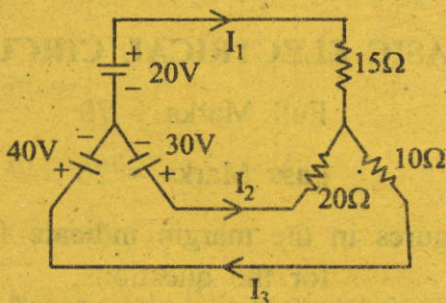


2. (a) Use nodal analysis to find the various currents in the branches of the circuit shown below :

9

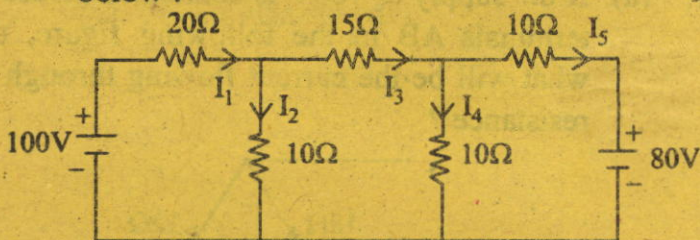


- (b) In the following circuit find the current in each branch and the current in the battery. What is the p.d. across A and C?


5

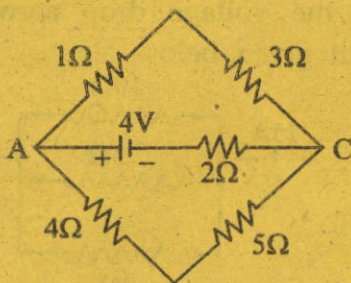

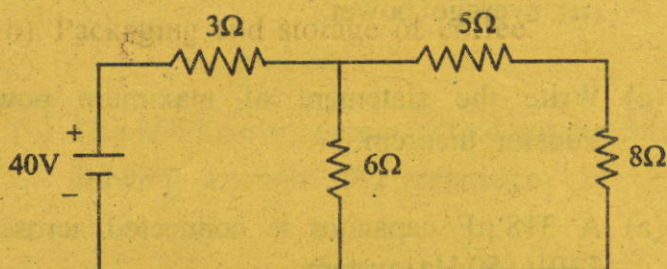3. (a) Using Thevenin's theorem find out the current flowing through  $8\Omega$  resistance. 7



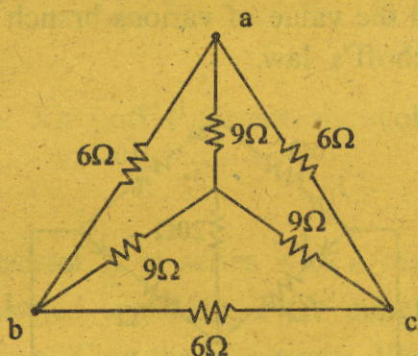- (b) Verify the answer of the previous question.  
 3(a) using Norton's theorem. 7
4. (a) Find the equivalent resistance between terminals a and b. 7



- (b) In a pure resistive circuit the instantaneous voltage and current are given by : 5  
 $v = 250 \sin 314t$ ;  $i = 10 \sin 314t$

Determine :

(i) the peak power

(ii) average power.

(c) Write the statement of maximum power transfer theorem. 2

5. (a) A  $318 \mu\text{F}$  capacitor is connected across a 230V, 50 Hz system. 6


Determine :

(i) the capacitive reactance

(ii) r.m.s value of current

(iii) equation for voltage and current.

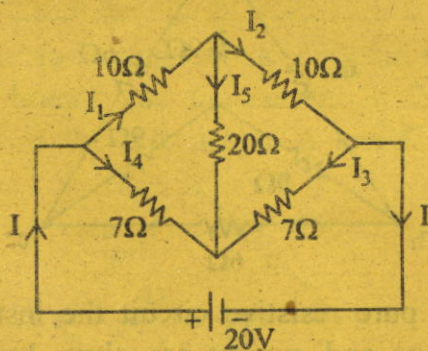(b) Find the value of various branch currents by Kirchoff's law. 6




(c) State the Ohm's law. 2

6. (a) Define the following terms with example :

Node, Branch, Mesh, Loop, Unilateral circuit,  
Junction. 6

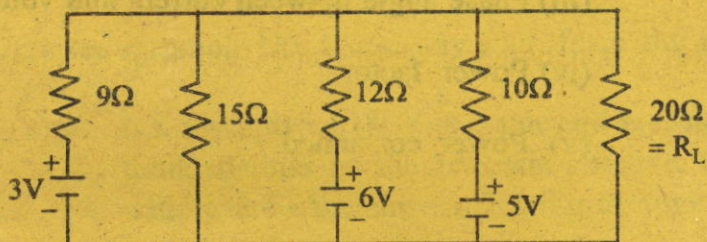(b) Use Millman's theorem to find out the current  
flowing through  $20\Omega$  resistance. 6



(c) State Kirchoff's current and voltage law. 2

7. (a) A resistor  $R$  in series with a capacitor  $C$  is  
connected to 50 Hz, 240V supply. Find the  
value of  $C$  so that  $R$  absorbs 300W at 100V.  
Find also the maximum charge and maximum  
energy stored in  $C$ . 7

- (b) A 230V, 50 Hz a.c supply is applied to a coil of  $0.06\text{H}$  inductance and  $2.5\Omega$  resistance connected in series with a  $6.8\ \mu\text{F}$  capacitor.

7

Calculate :

- (i) Impedance
- (ii) Current
- (iii) Phase angle between current and voltage
- (iv) Power factor
- (v) Power consumed.