

Total No. of printed pages = 5

CAI-401/BEC/4th Sem/2013/N

BASIC ELECTRICAL CIRCUITS

Full Marks - 70

Pass Marks - 28

Time - Three hours


The figures in the margin indicate full marks for the questions.

Answer any *five* questions.


1. (a) What colour bands will be found on the following resistances ?
 - (i) Nominal value of $1\text{ M}\Omega$ and tolerance of $\pm 5\%$.
 - (ii) Nominal value of $1\text{ K}\Omega$ and tolerance of $\pm 5\%$.
 - (iii) Nominal value of $10\text{ K}\Omega$ and tolerance of $\pm 10\%$. 2×3=6
- (b) Two coils connected in series have a resistance of 18Ω and when connected in parallel have a resistance of 4Ω . Find the value of resistances of the two coils. 5

[Turn over


- (c) Find the value of V_{xy} . 3

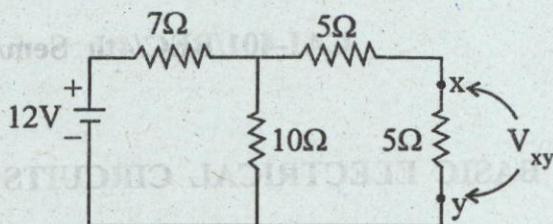

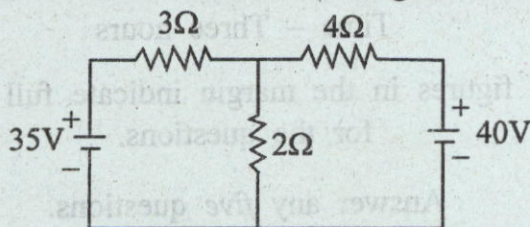
2. (a) Using Kirchoff's law, calculate the current in 2Ω resistor of the following network. 5



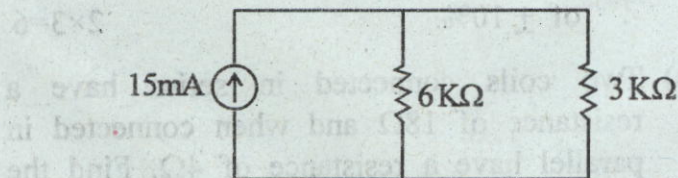
- (b) When a $1\text{ K}\Omega$ load is connected across a 20 mA current source, it is found that only 18 mA current flows in the load. What is the internal resistance of the source? 6
- (c) Calculate the current in the $3\text{ K}\Omega$ resistor by converting the current source into a voltage source. 3



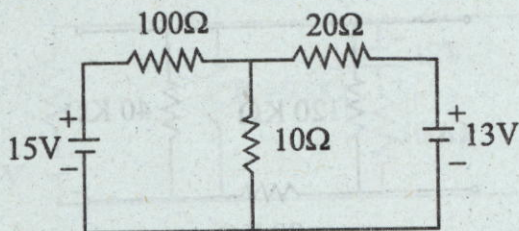3. (a) In the following network find the magnitude and direction of each branch current by using Mesh Current Method. 7




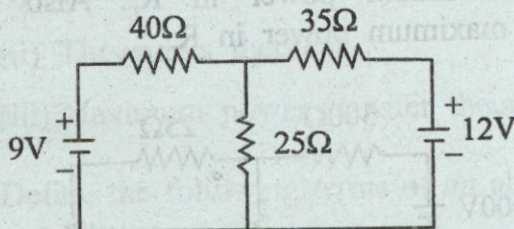- (b) Using Nodal analysis, find the current through 25Ω resistance. 7




4. (a) Verify the answer of Q. 3(a) using superposition theorem. 7

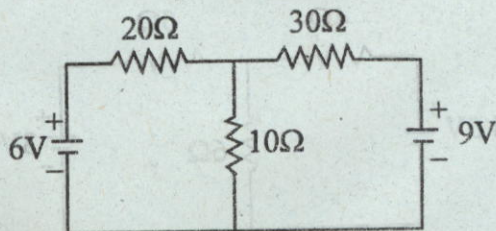
- (b) Using Thevenin's theorem, find the value of current flowing through 10Ω resistor. 7



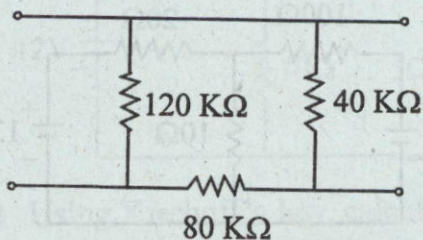
5. (a) Convert the following π -network to an equivalent λ -network. 7



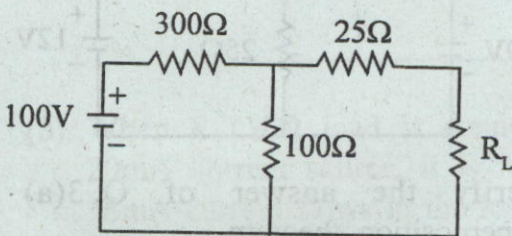
- (b) Find the value of R_L necessary to obtain maximum power in R_L . Also find the maximum power in R_L . 7



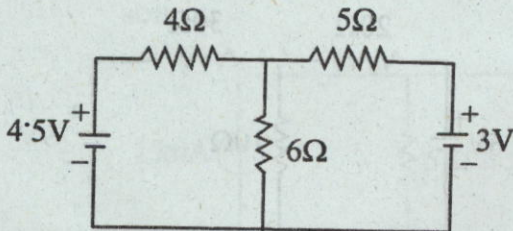6. (a) Using Norton's theorem, find the current in 6Ω resistor. 7



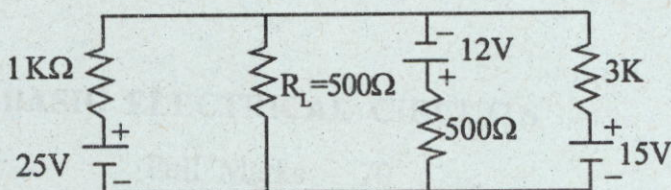- (b) Using Millman theorem, find the current through load resistance R_L in the following network. 7



7. (a) Write short notes on : 9
- (i) Kirchoff's current and voltage laws
 - (ii) Thevenin's theorem
 - (iii) Maximum power transfer theorem.
- (b) Define the following terms of an alternating quantity —
- rms value, form factor, peak factor, average value, phase. 5