

Total No. of printed pages = 3

CAI-401/BEC/4th Sem/2014/N

BASIC ELECTRICAL CIRCUITS

Full Marks - 70


Pass Marks - 28

Time - Three hours


The figures in the margin indicate full marks for the questions.

Answer any *seven* questions.

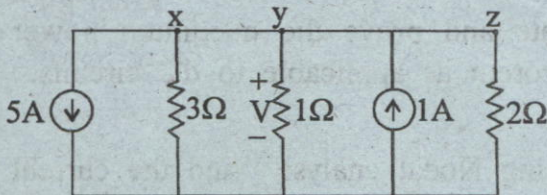1. Find 'V' and the magnitude and direction of the unknown currents in the branches xn, yn and zn in the following circuit : 10




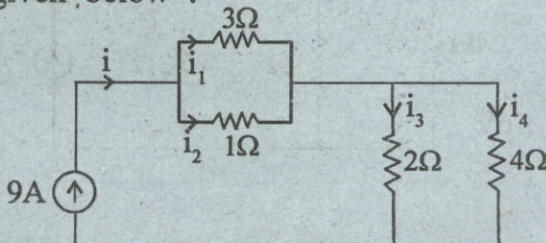2. (a) Find the currents i_1 , i_2 , i_3 and i_4 in the circuit given below : 5



[Turn over

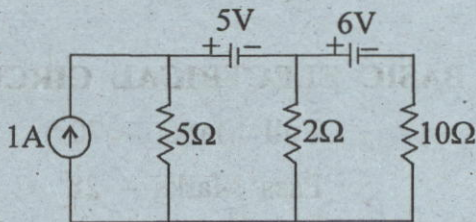- (b) Find the current and power dissipated in the 5Ω resistance. 5




3. (a) State the Kirchoff's laws giving suitable examples. 5

- (b) Define the following terms : 5


Branch, Mesh, Loop, Unilateral circuit, Junction.

4. State and prove the maximum power transfer theorem as applicable to d.c circuits. 10

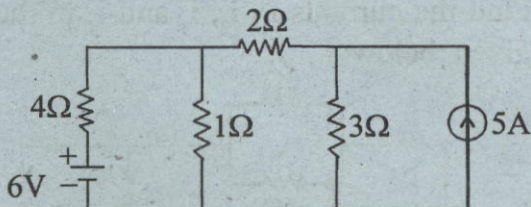5. Using Nodal analysis, find the current flowing through the 1Ω resistance. 10



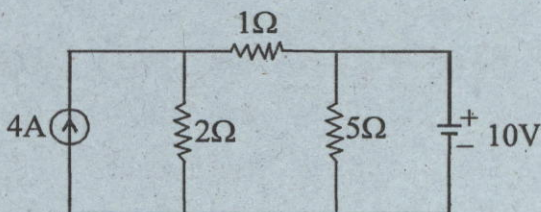6. Using Thevenin's theorem, find the current flowing through 5Ω resistance. 10



7. Verify the answer of the previous question (Q.6) using Norton's theorem. 10

8. Write short notes on any *four* : $2.5 \times 4 = 10$

- (i) Resonance
- (ii) Impedance
- (iii) Power factor
- (iv) Form factor
- (v) Ohm's law.