

Total No. of printed pages = 5

CAI-401/BEC/4th Sem/2016/N

## BASIC ELECTRICAL CIRCUITS

Full Marks – 70


Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer any *seven* questions.

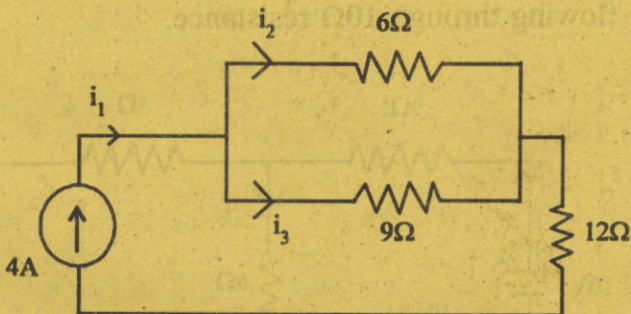
1. (a) Find the currents in  $i_1$ ,  $i_2$  and  $i_3$  in the following circuit : 5




- (b) State Kirchoff's laws giving suitable examples. 5

[Turn over

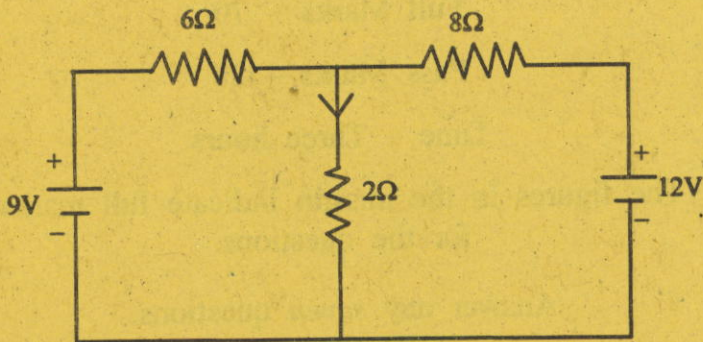2. State and prove the 'Maximum Power Transfer Theorem' as applicable to d.c circuits. 10
3. Using Nodal analysis find the current flowing through  $2\Omega$  resistance. 10




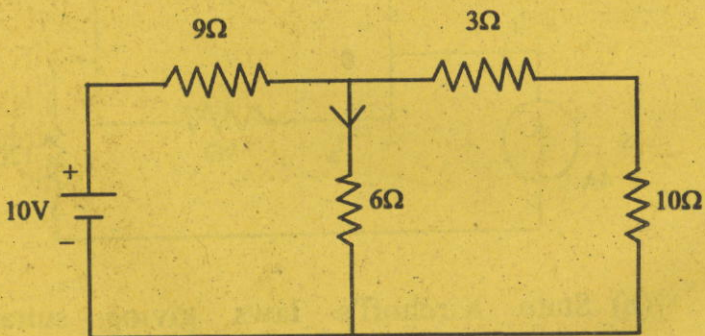4. Using Thevenin's theorem find the current flowing through  $10\Omega$  resistance. 10






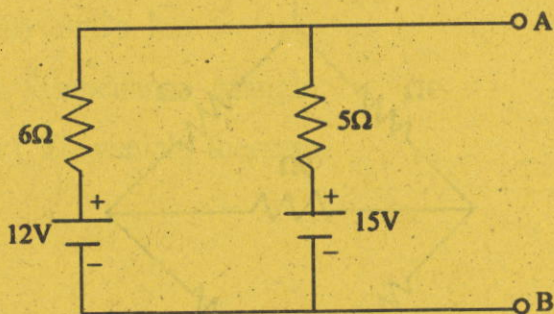
5. Simplify the following circuit to an equivalent circuit containing one current source and one resistance. 10



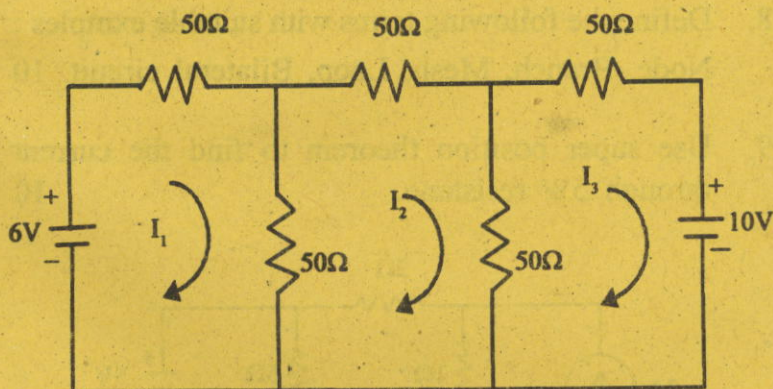6. Find the value of loop currents  $I_1$ ,  $I_2$  and  $I_3$  using loop-current method. 10




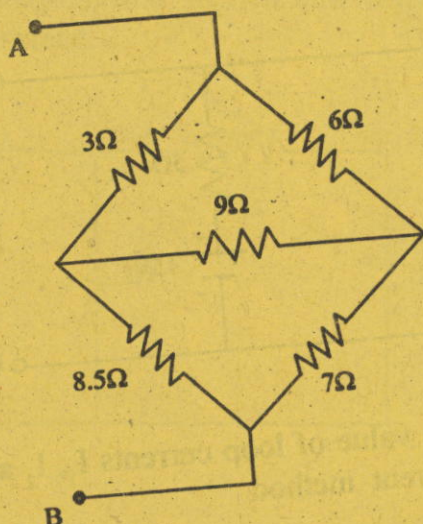7. Using  $\Delta - \lambda$  transformation, find the equivalent resistance between terminals A and B. 10



4.

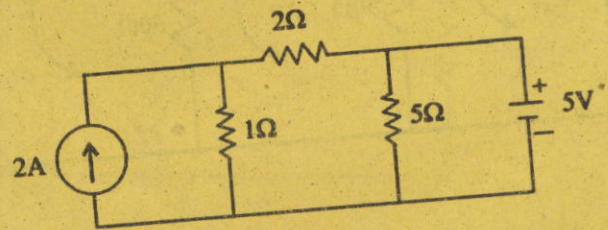8. Define the following terms with suitable examples :  
 Node, Branch, Mesh, Loop, Bilateral circuit. 10
9. Use super position theorem to find the current through 5Ω resistane. 10





10. Write short notes on any *four* :

10

- (i) Resonance
- (ii) Form factor
- (iii) Ohm's law
- (iv) Impedance triangle
- (v) Thevenin's theorem.

le  
5  
r