

Total No. of printed pages = 10

CAI-401/BEC/4th Sem/2018/M

BASIC ELECTRICAL CIRCUITS

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks for the questions.

The question paper consists of two parts : PART-A and PART-B. Both are compulsory.

PART – A

Marks – 25

All questions are compulsory.

1. Answer the following questions : 5

- (i) A 10 watt resistor has a value of 120Ω . What is the rated current through the resistor ?
- (ii) Three 2 ohm resistors are connected to form a triangle. What will be the resistance between any two corners of the triangle ?

[Turn over

- (iii) Should the resistance of a voltmeter be low or high ?
- (iv) A uniform wire of resistance R is divided into 10 equal parts and all of them are connected in parallel. What will be the equivalent resistance ?
- (v) An electric fan and a heater are marked 100W, 220V and 1000W, 220V respectively. What are the resistances of the heater and the fan ?

2. Choose the correct answer : 10

- (i) The current provided by an AC generator is alternating current that has
- (a) Square waveform
 - (b) Triangular waveform
 - (c) Sine or cosine waveform
 - (d) None of the above.

(ii) The capacity of a charged body to do work is called its

- (a) Electric resistance
- (b) Electric capacitance
- (c) Electric potential
- (d) None of the above.

(iii) The opposition offered by a substance to the flow of electric current is called its

- (a) Resistance
- (b) Capacitance
- (c) Power
- (d) None of the above.

(iv) The resistance R of a conductor depends on

- (a) Its length
- (b) Its area of X-section
- (c) Temperature
- (d) All of the above.

- (v) The reciprocal of resistance of a conductor is called its
- (a) Conductivity
 - (b) Conductance
 - (c) Resistivity
 - (d) None of the above.
- (vi) The rate at which work is done in an electric circuit is called its
- (a) Electric power
 - (b) Electric resistance
 - (c) Electric capacitance
 - (d) Electric potential
- (vii) The unit of electrical energy will be
- (a) Watt-sec
 - (b) Watt-hour
 - (c) Kilowatt-hour
 - (d) All of the above.

(viii) In case of liquids, Ohm's law is

- (a) Fully obeyed
- (b) Partially obeyed
- (c) There is no relation between current and p.d.
- (d) None of the above.

(ix) The characteristics of a parallel circuit

- (a) Voltage across each resistor is the same
- (b) Current through any resistor is inversely proportional to its resistance
- (c) Total current in the circuit is equal to the sum of currents in its parallel branches
- (d) All of the above.

(x) When there is a break in any part of a circuit, that part is said to be

- (a) Open circuited
- (b) Short circuited
- (c) All of the above.
- (d) None of the above.

3. Match the following statements in column A with the correct answer from column B. 5

Column A	Column B
Unilateral circuit	Parallel sources
Superposition theorem	$\pm 20\%$
Tolerance for blank stripe	Junctions of network
Millman's theorem	Multiple sources
Kirchhoff's current law	Diode rectifier

4. Read the following statements. Write true or false against each : 5

- (i) Charge of an electron is 1.987×10^{-19} coulomb.
- (ii) When the number of valence electrons of an atom is less than 4, the material is usually a metal and a conductor.
- (iii) A substance which has very few free electrons is called an insulator of electricity.
- (iv) One ampere of current is said to flow through a wire if at any cross-section one coulomb of charge flows in one second.
- (v) When the magnitude of current does not change with time, it is called a steady current.

PART-B

Marks - 45

Answer any *five* questions.

5. (a) Find the equivalent resistance between terminal A and B as shown in Fig.1. 3

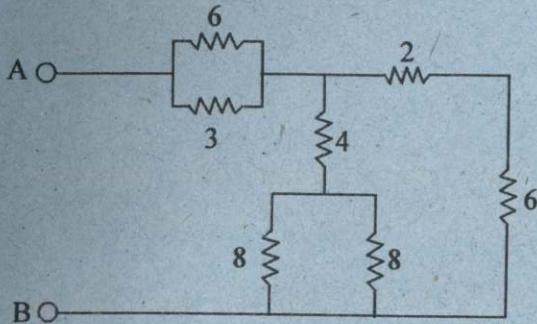


Fig. 1

- (b) Using Star to Delta conversion, find the resistance between the terminals B and C of circuit shown in Fig. 2. 6

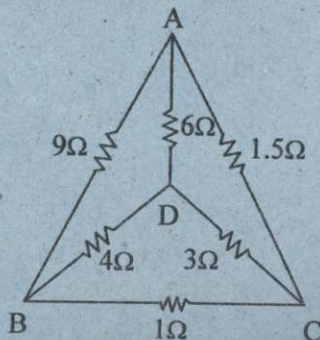


Fig. 2

6. (a) Find the value of I_1 , I_2 and I_3 in Fig. 3.

6

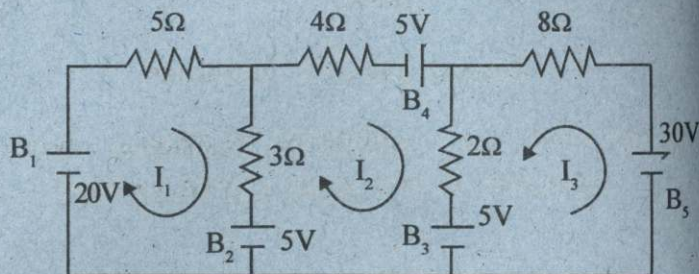



Fig. 3

- (b) State and explain the Kirchoff's laws applied to electric circuits.

3

7. (a) Using Nodal Analysis find out the current flowing through the 0.5Ω resistance (I_2) in Fig. 4.


6

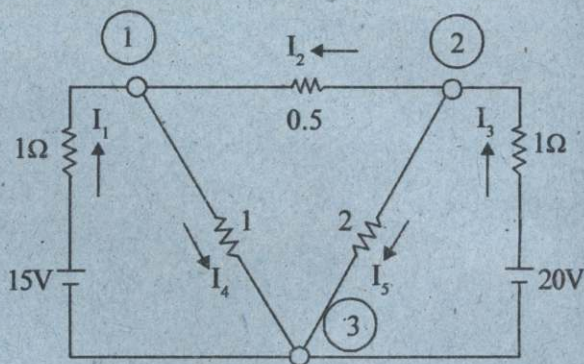


Datum Node

Fig. 4

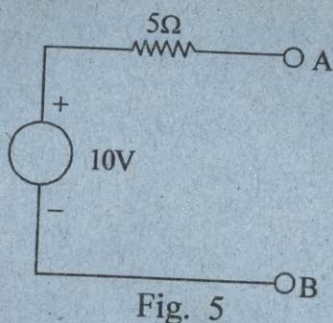- (b) Convert the voltage source of Fig. 5 into an equivalent current source. 3



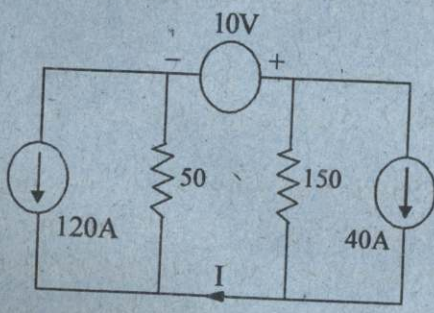8. (a) Apply Superposition theorem to find the value of current "I" in the network shown in Fig. 6. 6



- (b) A pure resistance of 50Ω is in series with a pure capacitance of $100\mu\text{F}$. The series combination is connected across 100V, 50 Hz supply.

Find (a) the impedance (b) current (c) power factor. 3

9. (a) Prove using Thevenin's theorem that the current in the R_2 resistance (value is 12Ω) of the network shown in Fig. 7 is 4A. 6

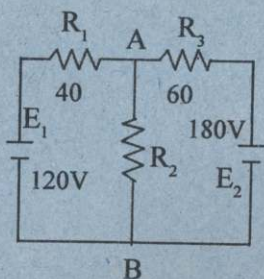


Fig. 7

- (b) What do you understand by the terms active, reactive and apparent power? 3
10. (a) Prove that the average value of H.W. Rectified Alternating Current is I_m/π . 5
- (b) A resistance of 20Ω , an inductance of $0.2H$ and a capacitance of $100\ \mu F$ are connected in series across $220V$, $50\ Hz$ mains. Determine the following (i) impedance, (ii) current, (iii) voltage across R , L and C , (iv) power in watts and VA. 4
11. Write short notes on : $3 \times 3 = 9$
- (i) Maximum power transfer theorem
 - (ii) Resonant frequency
 - (iii) Form and peak factor.