

Total No. of printed pages = 6

CAI-404/EC&D-I/4th Sem/2018/M

## ELECTRONICS CIRCUITS AND DEVICES – I

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks  
for the questions.

### PART – A

*All questions are compulsory.*

1. Answer the following multiple choice questions :

1×6=6

(a) The cut-in voltage for Ge diode is approximately

(i) 0.2V

(ii) 0.6V

(iii) 1.1V

(iv) None of the above

[Turn over

- (b) The width of the depletion layer of a junction
- (i) decreases with light doping
  - (ii) increases with heavy doping
  - (iii) is independent of applied voltage
  - (iv) is increased under reverse biased.
- (c) In active region operation of a transistor
- (i) emitter junction is reversed bias while collector junction is forward bias
  - (ii) emitter junction is forward bias while collector junction is reverse bias
  - (iii) both junctions are reversed biased
  - (iv) both junctions are forward biased
- (d) A JFET can operate in
- (i) depletion mode only
  - (ii) enhancement mode only
  - (iii) either depletion or enhancement mode at a time
  - (iv) both depletion and enhancement modes simultaneously

- (e) An ideal Op-Amp has CMRR
- (i) Zero
  - (ii) Small
  - (iii) Large
  - (iv) Infinite
- (f) A voltage follower
- (i) is non-inverting
  - (ii) has gain one
  - (iii) has no feedback resistor
  - (iv) All of the above

2. Fill in the blanks : 1×12=12

- (a) An Op-Amp is a \_\_\_\_\_ IC.
- (b) Open loop gain of ideal Op-Amp is \_\_\_\_\_.
- (c) The ratio of differential gain to common mode gain is \_\_\_\_\_.
- (d) The base of transistor is \_\_\_\_\_ than emitter.
- (e) The function of transistor is \_\_\_\_\_.
- (f) The gate to source voltage that gives zero drain current in a FET is \_\_\_\_\_.
- (g) When the collector current flows only during the positive half cycle of the input signal the power amplifier is \_\_\_\_\_.

- (h) Overall efficiency of Class A power amplifier is \_\_\_\_\_.
- (i) The oscillator is an amplifier with \_\_\_\_\_ feedback.
- (j) A bistable multivibrator has \_\_\_\_\_ stable states.
- (k) A circuit that generates square waves is called a \_\_\_\_\_.
- (l) The JFET can operate in \_\_\_\_\_ mode only.
3. State whether the following statements are true or false:  $1 \times 7 = 7$
- (a) Operating point of transistor means IC and Vbe.
- (b) Power amplifier are large signal amplifiers.
- (c) Audio frequency range is 20 Hz to 20 KHz.
- (d) A bistable multivibrator has stable states.
- (e) The frequency of oscillation of an astable multivibrator depends mainly on width of input pulse.
- (f) Output resistance of ideal Op-Amp is infinity.
- (g) Input impedance of MOSFET is less than FET.

PART-B

Answer any *three* questions.

1. (a) What is power amplifier? Differentiate between voltage amplifier and power amplifier.

1+3=4

(b) Differentiate between Class A, Class B and Class C power amplifier.

3

(d) Find overall efficiency of Class A power amplifier.

5

(e) For a power amplifier working in Class A operation, the zero signal collector current is 100 mA. If d.c supply voltage  $V_{cc}=12V$ , determine (a) maximum a.c power output, (b) power rating of transistor, (c) maximum collector efficiency.

3

2. (a) What is oscillator? Give the classification of oscillators based on the frequency ranges.

1+2=3

(b) State the conditions under which a feedback amplifier works as an oscillator.

2

(c) Describe Colpiits' oscillator circuit and explain its action.

7

- (d) A Colpitts' oscillator is designed with  $C_1=100 \text{ pF}$ ,  $C_2=7500 \text{ pF}$  and an inductor. Determine inductance value if the frequency of oscillation is  $950 \text{ KHz}$ . 3
3. (a) What is an Op-Amp? Define CMRR. 1+2=3
- (b) Describe the characteristics of an ideal Op-Amp. 4
- (c) Explain the following: 2×4=8
- (i) Subtractor
- (ii) Integrator
4. (a) Explain the operation of N channel FET with static characteristics curve. 8
- (b) Name the factors which make JFET superior to BJT. 2
- (c) Write short notes on any *one* of the following: 5
- (i) MOSFET
- (ii) Push Pull amplifier
- (iii) Multivibrator.