

Total No. of printed pages = 3

CAI-404/EC&D-I/4th Sem/2013/M

ELECTRONIC CIRCUITS AND DEVICES – I

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.


Answer any *five* questions.

1. (a) Briefly explain the working principle of class A amplifier and derive its efficiency. 7+3+4=14
(b) What do you mean by magnetic feedback? Explain its significance.
(c) A CE class A amplifier is coupled to a load resistance of 12Ω by a transformer of primary to secondary turns ratio 8:1. The signal has a peak to peak swing of 250 mA. Calculate its output power. 7+3+4=14

2. (a) What do you mean by buffer amplifier? Explain the operation of OPAMP as subtractor and integrator. 2+8+4=14

[Turn over

(b) When will the OPAMP get saturated?

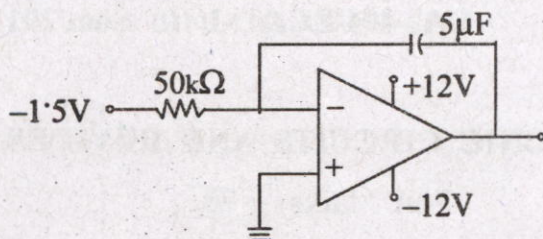


3. (a) What are the two criteria that must be followed by the oscillator circuits?

$$2+6+6=14$$

(b) Describe the construction and operation of Hartley oscillator.

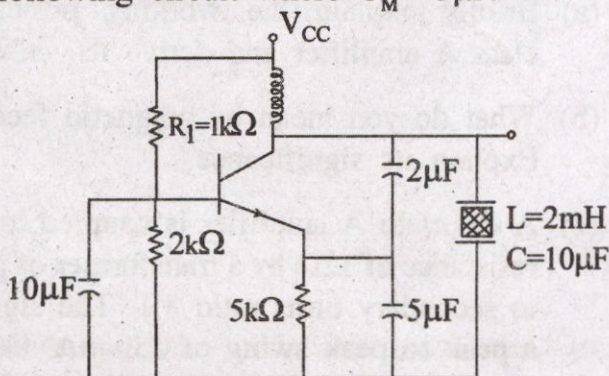(c) Calculate the frequency of oscillation for the following circuit where $C_M = 5\mu\text{F}$.



4. (a) Determine the equation of output resistance and input resistance of a transistor amplifier using h-parameters.

(b) Explain the operation of voltage series feedback amplifier.

$$8+6=14$$

5. (a) Explain the operation of monostable multivibrator.
- (b) Determine the value of capacitor to be used in an astable multivibrator to provide train of pulse $2\mu\text{s}$ wide at a repetition rate of 100 kHz if $R_1 = R_2 = 20\text{ k}\Omega$. $10+4=14$
6. (a) What is pinch off voltage ? Explain the principle of operation of PJFET.
- (b) Describe the working principle of depletion mode MOSFET. $2+6+6=14$
7. Write short notes on any *four* of the following : $3\frac{1}{2}\times 4=14$
- (i) Push-pull amplifier
 - (ii) NMOS
 - (iii) Current series feedback amplifier
 - (iv) Application of OPAMP as computational unit
 - (v) BJT as amplifier.