

Total No. of printed pages = 3

CAI-404/EC&D-I/4th Sem/2013/N/C

ELECTRONIC CIRCUITS AND DEVICES – I

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

1. (a) Derive the expression of input resistance, voltage gain and current gain in terms of h parameters of a transistor amplifier.
- (b) Explain the working of class C tuned amplifier. 9+5=14
2. (a) Describe the operation of Wien bridge oscillator with necessary circuit diagram.
- (b) Explain how a parallelly connected crystal oscillator works.
- (c) State the Barkhausen criterion. 6+6+2=14

[Turn over

3. (a) Discuss the working of voltage series and current shunt feedback amplifier using transistors.


(b) The frequency of a Hartley oscillator is set at 60 kHz using a tank circuit with the following components : $L_1 = 60 \text{ mH}$, $C = 20 \text{ nF}$. Determine the other inductor to be connected to yield the required frequency.

$$12+2=14$$

4. (a) Explain how an OPAMP can be used as an adder and subtractor.

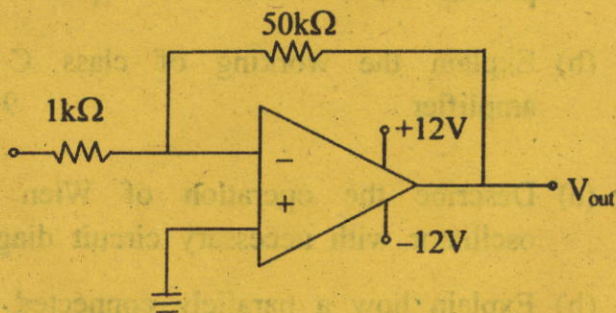(b) Calculate the voltage gain for the amplifier with the following components. Find the output voltage V_{out} if the input voltage is

$$V_{in} = 0.5 \sin 100 \pi t \text{ volt.} \quad 8+6=14$$



5. (a) Explain the working of enhancement mode MOSFET.

(b) Describe the circuit operation of JFET with circuit diagram.

(c) What do you mean by pinch off voltage ?

$$6+6+2=14$$

6. (a) What do you mean by saturation and breakdown state of JFET ? 2

(b) Explain the principle of operation of NMOS. 6

(c) Describe the construction and operation of nJFET. 6

7. Write short notes on any *four* of the following :

$$3\frac{1}{2} \times 4 = 14$$

(i) Depletion mode MOSFET

(ii) Voltage shunt feedback amplifier

(iii) Push pull amplifier

(iv) Astable multivibrator

(v) Wien bridge oscillator.