

• Total No. of printed pages = 4

CAI-404/EC&D-I/4th Sem/2014/N

ELECTRONIC CIRCUITS AND DEVICES - I

Full Marks -70

Pass Marks - 28


Time - Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

- (a) Explain the input characteristics of a CE mode transistor. 4

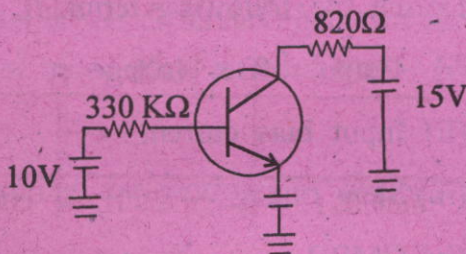(b) Calculate the base current and collector current from the following circuit diagram where $\beta = 200$. 4



[Turn over

- (c) Derive the power efficiency of a class A amplifier. 6
2. (a) Obtain the expression of current gain and voltage gain in terms of h parameters of a transistor amplifier. 8
- (b) Describe the operation of voltage series feedback amplifier with necessary circuit diagram. 6
3. (a) Describe how Colpitt's oscillator works. 5
- (b) Determine the oscillation frequency of a transistor hartley oscillator with components $L_1 = 1 \text{ mH}$, $L_2 = 100 \mu\text{H}$, $M = 50 \mu\text{H}$ and $C = 100 \text{ nF}$. 4
- (c) What is the main advantage of crystal oscillator over other oscillator ? Explain the working of parallely connected crystal oscillator. 1+4=5
4. (a) Define the following terms : 4
- (i) Output offset voltage
- (ii) Input bias current
- (iii) Slew rate
- (iv) CMRR.

- (b) Describe how an OPAMP can act as a differentiator. 5
- (c) For an OPAMP having slew rate of $SR = 2V/\mu S$, what is the maximum closed loop voltage gain that can be used when the input signal varies by $0.5V$ in $10\mu S$? 5
5. (a) Explain the working of a monostable multivibrator. 8
- (b) Describe the different region of operation of a JFET with the help of V-I characteristics. 6
6. (a) Describe the principle of operation of PMOSFET. 6
- (b) What is the difference between an enhancement mode and depletion mode MOSFET? 2
- (c) Describe the working of a CMOS. 6

7. Write short notes on any *four* of the following :

- (i) Push-pull amplifier
- (ii) Transistor as an amplifier
- (iii) Current shunt feedback amplifier
- (iv) OPAMP as an adder
- (v) nJFET.

$3\frac{1}{2} \times 4 = 14$