

Total No. of printed pages = 5

CAI-404/EC&D-I/4th Sem/2017/M

ELECTRONIC CIRCUITS AND DEVICES-I

Full Marks – 70

Pass Marks – 28

Time – Three hours


The figures in the margin indicate full marks
for the questions.

Answer any *five* questions.

1. (a) What is transistor ? Draw the circuits of various transistor configuration. 4
- (b) Why the width of the base region of a transistor is kept very small compared to other regions ? 1
- (c) How α and β are related to each other ? 1
- (d) What do you understand by transistor biasing? What is the need for bias stabilization ? 3


[Turn over

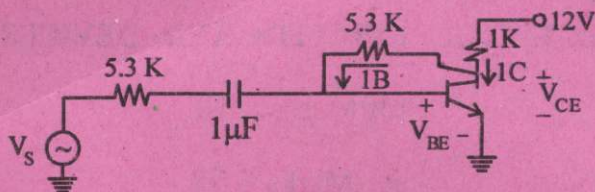- (c) In the circuit shown transistor has $\beta = 60$ and $V_{BE} = 0.7V$. Find the operating point. 5



2. (a) Derive the expression of input resistance, voltage gain and current gain in terms of h parameters of a transistor amplifier. 9

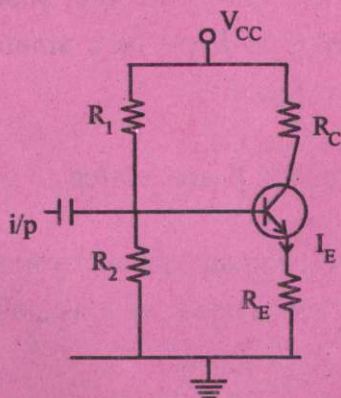- (b) In the CE amplifier of figure, $I_E = 1mA$, $R_E = 1000\Omega$ and $\beta = 49$. Find the values of R_1 and R_2 such that the stability factor does not exceed 5. Assume $V_{CC} = 5$ volts and $V_{BE} = 0$. 5



3. (a) Differentiate the following : $3+3=6$

(i) Voltage amplifier and power amplifier.

(ii) Class A and class B power amplifier.

(b) Find the efficiency of class A power amplifier. 4

(c) A class A, CE amplifier operates from $V_{CC} = 25V$, draws a no signal current of $6A$ and feeds a load of 30Ω through a step up transformer of $n_2 : n_1 = 2.5$. Find effective input resistance at collector end for maximum power transfer and conversion efficiency at maximum signal input. 4

4. (a) What is an oscillator ? Give the two conditions for oscillation in feedback amplifier.

$1+2=3$


(b) How does Hartley oscillator differ from Colpitt's oscillator in construction ? Explain with neat diagram the working of a typical inductance type high frequency oscillator.

$1+5=6$

- (c) A Hartley oscillator is designed with $L_1 = 5\text{mH}$, $L_2 = 25\mu\text{H}$ and a variable capacitance. Determine the range of capacitance values, if the frequency of oscillation is varied between 850 KHz and 2030 KHz. 4
- (d) The oscillator is an amplifier with _____ feedback. 1
5. (a) List the characteristics of an ideal Op-Amp. 4
- (b) Define following : 4
- (i) CMRR
 - (ii) Slew Rate
 - (iii) Input offset voltage
 - (iv) PSRR
- (c) Explain how Op-Amp can be used as – 2+2=4
- (i) Voltage follower
 - (ii) Integrator.

(d) Find output of the given circuit :

2

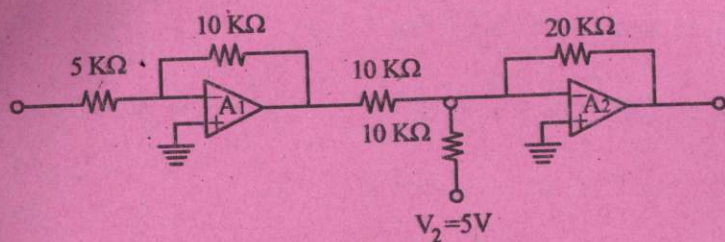

6. (a) Draw the circuit diagram of CMOS NAND gate and explain its operation. 6

(b) Describe construction, working and characteristics of N-channel FET. 6

(c) Calculate the minimum value of V_{DS} required for an NMOSFET to operate in pinch-off condition when $V_{GS} = 1\text{V}$, $V_P = -2\text{V}$, $I_{DSS} = 10\text{mA}$. Also find the corresponding drain current. 2

7. Write short notes on any two : $7 \times 2 = 14$

(i) Push-pull amplifier

(ii) Multivibrator

(iii) Depletion mode MOSFET

(iv) nMOS.

