

Total No. of printed pages = 5

CAI-404/EC&D-I/4th Sem/2015/M

ELECTRONIC CIRCUITS AND DEVICES - I

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

1. (a) Derive the expressions for current gain, voltage gain, input impedance and output impedance for common emitter amplifier using h-parameter model. 8


(b) For the following circuit with given values of $h_{ic}=1k\Omega$, $h_{fe}=100$, $h_{oc}=25\mu S$ and $h_{re}=5\times 10^{-4}$. 6

Calculate :

(i) Draw the h-parameter equivalent circuit of the amplifier.

[Turn over

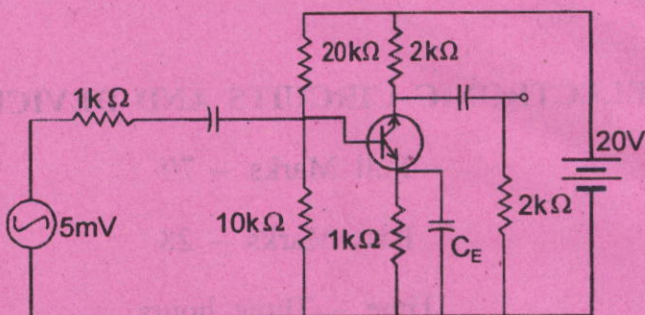- (ii) Calculate the input impedance, output impedance, current gain and voltage gain.



2. (a) Draw the circuit diagram of transformer coupled class A power amplifier and describe its operation. 5
- (b) A transformer coupled class A power amplifier draws a current of 200mA from a collector supply of 20V, when no signal is applied to it. Determine 5
- Maximum output power
 - Maximum collector efficiency
 - Power rating of the transistor.
- (c) Distinguish between the following :
- Positive feedback and negative feedback.
 - JFET and MOSFET. 4

3. (a) Show that the maximum efficiency of class B operation will not exceed 78.5 percent.

6

- (b) For a class B amplifier providing 25V peak signal to 15Ω load and a power supply of $V_{CC}=30V$, determine the input power, output power and circuit efficiency.

4

- (c) Deduce the relation for voltage gain in an opamp inverting amplifier.

4

4. (a) Describe the basic principle of feedback in amplifier and deduce the relation for voltage gain with feedback.

6

- (b) Explain the operation of astable multivibrator (using B.J.T) with the help of a circuit diagram.

8

In an astable multivibrator circuit with the given values.

$$R_1 = R_2 = 10k\Omega, R_3 = R_4 = 1k\Omega \text{ and } C_1 = C_2 = 0.01\mu F.$$

Determine

- (i) The time period and frequency of circuit oscillation.
- (ii) Minimum value of transistor β .

5. (a) Draw the circuit diagram for the following using opamp.

(i) Adder

(ii) Subtractor

(iii) Integrator

(iv) Differentiator.

Also, mention the corresponding expressions for output voltage in each case. 8

2.

(b) With the help of a structural diagram, describe the operation of FET. Also draw the I-V characteristics for FET. 6

6. (a) A JFET has $V_p = -5V$, $I_{DSS} = 10mA$ and $I_{DS} = 2.5mA$. Determine the transconductance. 5

(b) Describe the principle of operation of a Hartley oscillator with the help of a circuit diagram. 6

(c) Determine the oscillation frequency of a transistor Hartley oscillator with circuit values $L_1 = 150 \mu H$, $L_2 = 1.5mH$, $M=75\mu H$ and $C=150pF$. 3

7. (a) Draw the structural diagram of N-channel MOSFET and explain its working. 5

5/M

(b) Describe the operation of Biastable multivibrator using a circuit diagram. 5

- I

(c) Draw the following gates using CMOS

(i) AND

(ii) OR

4

8. Write short notes on the following : $7 \times 2 = 14$

(i) Colpitt's oscillator

(ii) Multivibrator using 555 Timer IC.

uin,
put
ier
8

ies
nd
6

nit