

Total No. of printed pages = 9

**END SEMESTER EXAMINATION - 2019**

Semester : 5th

Subject Code : CAI-504

**POWER ELECTRONICS**

Full Marks -70

Time - Three hours

The figures in the margin indicate full marks for the questions.

**Instructions :**

1. *All* questions of PART - A are compulsory.
2. Answer any *five* questions from PART - B.

**PART - A**

Marks - 25

1. Fill in the blanks : 1×7=7
  - (i) BJT has \_\_\_\_\_ on state loss compared to MOSFET.
  - (ii) Holding current of SCR is \_\_\_\_\_ than latching current.

[Turn over

(iii) SCR is a \_\_\_\_\_.

(iv) SCR is turned off when anode current falls below \_\_\_\_\_.

(v) Snubber circuits are used for protection from \_\_\_\_\_ in SCR.

(vi) IGBT has characteristics of both \_\_\_\_\_ and \_\_\_\_\_.

(vii) A MOSFET is a \_\_\_\_\_ controlled device.

2. Write true or false :

1×5=5

(i) GTO can be turned off by applying a negative gate pulse.

(ii) A TRIAC has 6 semiconductor regions.

(iii) UJT is a three terminal device.

(iv) The equivalent circuit of IGBT consists of two BJTs.

(v) Firing circuits are used for commutation of SCR.



3. Choose the correct answer :

1×13=13

(a) Which is not a method of SCR turn on ?

(a) gate triggering

(b)  $dv/dt$  triggering

(c) negative gate triggering

(d) light triggering

(b) The Schottky barrier diode has

(a) Semiconductor-semiconductor contact

(b) Metal-semiconductor contact

(c) Metal-metal contact

(d) None of the above

(c) IGBT is a

(a) Current controlled device

(b) Phase controlled device

(c) Voltage controlled device

(d) None of these

- (d) A single phase half-wave controlled rectifier circuit has an R-load. A freewheeling diode is also in the circuit. When freewheeling diode is conducting the SCR
- (a) is forward biased
  - (b) is reverse biased
  - (c) may be forward biased or reverse biased
  - (d) forward biased initially but reverse biased afterwards
- (e) Second breakdown is present in
- (a) MOSFET
  - (b) BJT
  - (c) IGBT
  - (d) SCR
- (f) A thyristor can be protected against high  $\frac{dv}{dt}$  by
- (a) connecting an inductor in series with the thyristor
  - (b) connecting a capacitor in series with the thyristor
  - (c) connecting an inductor in parallel with the thyristor
  - (d) connecting a capacitor in parallel with the thyristor



- (g) A Thyristor is a \_\_\_\_\_ switch.
- (a) one directional
  - (b) two directional
  - (c) three directional
  - (d) four directional
- (h) A TRIAC is a \_\_\_\_\_ switch.
- (a) unidirectional
  - (b) bidirectional
  - (c) three directional
  - (d) None of the above
- (i) A diac has \_\_\_\_\_ terminals.
- (a) four
  - (b) three
  - (c) two
  - (d) None of these
- (j) Chopper control for DC motor provides variation in
- (a) Frequency
  - (b) Input current
  - (c) Input voltage
  - (d) Input impedance

(k) In an SCR, the angle of conduction is changed by changing \_\_\_\_\_.

- (a) Anode voltage
- (b) Forward current
- (c) Reverse Breakdown voltage
- (d) Gate current

(l) An SCR has \_\_\_\_\_ PN junctions.

- (a) four
- (b) three
- (c) two
- (d) one

(m) Which of the following is an uncontrolled device ?

- (a) MOSFET
- (b) IGBT
- (c) Diode
- (d) BJT

PART - B  
Marks - 45

4. (a) Why equalization circuits are required in SCR series or parallel operation ? 4

(b) How an UJT can be used as a relaxation oscillator ? Explain. 5

5. Deduce the expression for average and RMS value of load voltages for the following circuits :

(a) Single phase full-wave rectifier with resistive load.

(b) Single phase half-wave rectifier with RL load. Also, draw the circuit diagram and relevant waveforms in each case. 9

6. (a) Draw the circuit diagram for step up and step down chopper with relevant voltage waveforms. Also, determine the expression for average value of output voltage in each case. 6

(b) Describe the operation of two quadrant chopper with a suitable circuit diagram. 3



7. (a) Draw the circuit diagram for three phase half-wave rectifier with resistive load and determine the expression for average value of load voltage. 7
- (c) A step up chopper has input voltage of 110 V and output voltage of 330 V. If the conducting time of thyristor chopper is 200 $\mu$ s, determine the pulse width of the output voltage. 2
8. (a) What is an inverter? Explain the working principle of an inverter. 4
- (b) Describe the operation of a single phase to single phase step up cycloconverter using a suitable circuit diagram. 5
9. (a) Give the steady state analysis of a single phase inverter. 6
- (b) What do you mean by latching current and holding current in an SCR? 3
10. (a) A single phase half-wave rectifier is operated from 230V, 50 Hz source and the load resistance is  $R=12\Omega$ . For a firing angle delay of  $30^\circ$ , determine the RMS value of load voltage. 4

44/CAI-504/PE

(8)

70(W)

- (b) Describe the different methods of SCR triggering. 5

11. Draw suitable circuits for the following applications using SCR or Traic and explain in brief:

- (i) Temperature Control of a Heater
- (ii) Battery Charger
- (iii) Fan Regulator. 9

12. Describe how separately excited DC motors and DC series motors are controlled by the following methods:

- (i) Single phase DC Drives.
- (ii) Chopper Drives.

Draw suitable circuit diagrams.

9

44/CAI-504/PE

(9)

70(W)

