

Total No. of printed pages = 7

CAI-506/EC&D-II/5th Sem/2017/N

ELECTRONIC CIRCUITS AND DEVICES -II

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks
for the questions.

PART – A

All questions are compulsory.

1. Choose the correct answer from the given
options : 1×6=6

(a) An electronic oscillator is

(i) An amplifier

(ii) An amplifier with feedback

(iii) Converter of AC to DC

(iv) Just like an alternator

[Turn over

(b) For generating 1 KHz frequency the most suitable circuit is

- (i) Hartley oscillator
- (ii) Wein bridge oscillator
- (iii) Colpitt's oscillator
- (iv) Tuned collector oscillator

(c) In RC phase shift oscillator circuit

- (i) There is no need for feedback
- (ii) $BA < 1$
- (iii) Pure sine wave output is possible
- (iv) Transistor parameters determine oscillator frequency

(d) The negative feedback in an amplifier

- (i) Reduces the voltage gain
- (ii) Increases the voltage gain
- (iii) Does not affect the voltage gain
- (iv) None of the above

(e) SCR can be used as

- (i) Converter
- (ii) Inverter
- (iii) Chopper
- (iv) All of the above

(f) Common mode signals have _____.

- (i) The same amplitude
- (ii) The same phase
- (iii) The same frequency
- (iv) All of the above

2. Fill in the blanks : $1 \times 12 = 12$

- (a) The open loop gain of an ideal OP-AMP is _____.
- (b) A voltage follower has gain _____.
- (c) The use of negative feedback in OP-AMP reduces _____.
- (d) Circuit used to pass a specified band of frequencies while attenuating all the signals outside that band is called as _____.

- (e) The resistance (R) of a low pass filter at a cut off frequency of 15.9 KHz with pass band gain 1.5 is _____.
- (f) The application in which narrow band-reject filter can be used is _____.
- (g) Number of feedback path present in narrow band pass filter _____.
- (h) Differential circuits are less sensitive to _____.
- (i) Output resistance of AC analysis of dual input balanced output differential amplifier is _____.
- (j) Frequency range of DC amplifiers _____.
- (k) Twin-T oscillator is a _____ feedback oscillator.
- (l) Output voltage of IC 7915 is _____.

3. State whether the following statements are true or false. 1×7=7

- (a) Precision rectifier is a circuit with operational amplifier which behave like a power amplifier.


- (b) Feedback in an amplifier always help to increase its gain.
- (c) Many Op-Amp parameters depend on the temperature.
- (d) The change in the output voltage for a given change in the input voltage is called as load regulation.
- (e) Voltage regulation is poor in shunt regulation.
- (f) IC voltage regulators greatly simplifies power supply design.
- (g) RC phase shift oscillator produce 9% of distortion level in the output.

PART – B

Answer any *three* questions.

- 4. (a) Explain with circuit diagram the basic BJT differential amplifier. 4
- (b) Describe DC analysis of BJT differential amplifier. 7

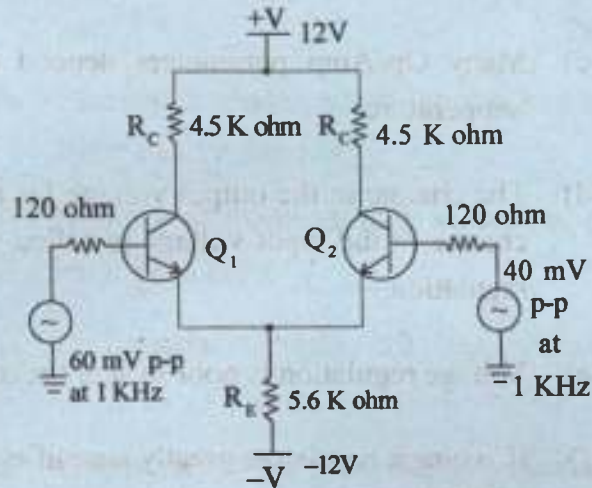- (c) Calculate the operating point of the following circuit : 4



5. (a) What is adjustable voltage regulator ? Derive the expression for the output voltage for LM 317 adjustable voltage regulator. 2+6=8
- (b) What is negative feedback amplifier ? How does negative feedback help in increasing stability ? 5
- (c) What is the advantage of active filters over passive filters ? 2
6. (a) What is tuned amplifier ? Give difference between single tuned and double tuned amplifier. 1+2=3

- (b) Draw and explain circuit diagram of inductive coupling single tuned amplifier with its frequency response. 8
- (c) Explain the working principle of half-wave precision rectifier. 4

7. (a) Explain the operation of Wien bridge oscillator and derive the frequency and condition for oscillation. 8
- (b) Calculate the value of $C_1 = C_2$ for the Wien bridge oscillator to operate at a frequency of 20 KHz. Assume $R_1 = R_2 = 50 K\Omega$. 2
- (c) Write short note on any *one* of the following : 5
- (i) SCR
- (ii) Phase shift oscillator
- (iii) Buck regulator.