

Total No. of printed pages = 4

CAI-506/EC&D-II/5th Sem/2013/M

ELECTRONIC CIRCUITS AND DEVICES – II

Full Marks – 70

Pass Marks – 28

Time – Three hours


The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

1. What do you mean by balanced and unbalanced differential amplifier? Derive the equation of output voltage of a dual input unbalanced differential amplifier.

In a differential amplifier $V_{CC} = 15V$, $V_{EE} = -15V$, $R_E = 50\text{ k}\Omega$, $R_B = 10\text{ k}\Omega$, $R_C = 15\text{ k}\Omega$. Determine the output voltage of Q_1 and Q_2 are identical with $\beta_{dc} = 50$

1+10+3=14

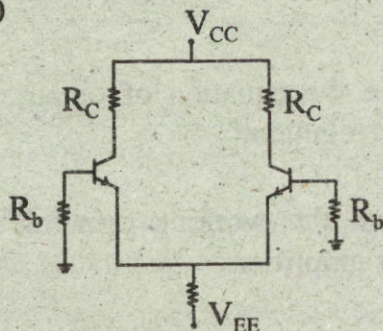


[Turn over

2. (a) Define the following terms : 9

- (i) CMRR
- (ii) input offset voltage
- (iii) output offset voltage
- (iv) input bias current
- (v) buffer amplifier, and
- (vi) slew rate

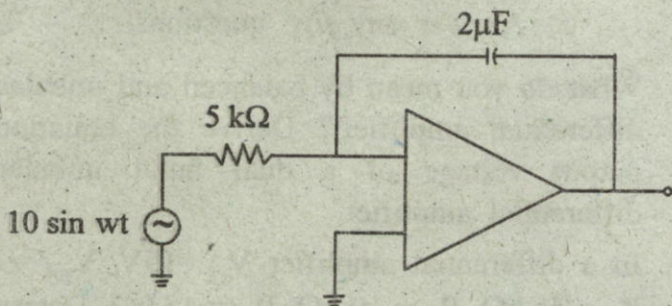(b) Determine the output voltage of the following OPAMP at 10 sec. 5




3. (a) Describe how a single OPAMP regulator works.

(b) Derive the equation of output voltage of a boost regulator. $6+8=14$

4. (a) Explain the working principle of a single tuned amplifier.

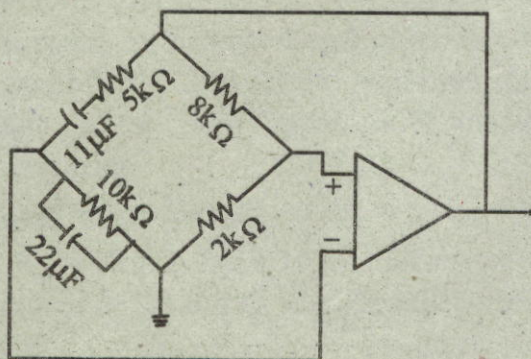- (b) What do you mean by piezoelectric effect ?
- (c) Describe the operation of a parallelly connected crystal as an oscillator. $5+2+7=14$
5. (a) With the help of circuit diagram derive the equation of feedback current of voltage shunt feedback amplifier. 5
- (b) Discuss the effect on input impedance of voltage shunt feedback amplifier. 4
- (c) Determine the frequency of oscillation from the following circuit. 5



6. (a) Differentiate TRIAC from DIAC. Explain any two triggering method of SCR.
- (b) Explain the monostable mode of operation of IC 555 timer. $1+6+7=14$

7. Write short notes on any *four* of the following :
 $3\frac{1}{2} \times 4 = 14$

- (i) Capacitive filter power supply
- (ii) LM 317 IC as voltage regulator
- (iii) Current series feedback amplifier
- (iv) FET amplifier
- (v) Phase shift oscillator.