

Total No. of printed pages = 5

CAI-506/ECD-II/5th Sem/2016/N

**ELECTRONIC CIRCUITS AND  
DEVICES - II**

Full Marks – 70

Pass Marks – 28

Time – Three hours

The figures in the margin indicate full marks  
for the questions.

Answer any *five* questions.

1. What is dual input unbalanced output differential amplifier configuration ? Give its circuit diagram and a.c analysis and derive the following : 14
  - (i) Differential voltage gain
  - (ii) Differential input resistance
  - (iii) Output resistance.
2. (a) For differential amplifier determine voltage gain, input resistance, output resistance and CMRR if  $V_{CC} = 12V$ ,  $V_{EE} = -12V$ ,  $R_C = R_E = 1M\Omega$  and transistor  $Q_1$  and  $Q_2$  are identical with  $\beta_{ac} = 98$ . Determine the output voltage when  $V_{in} = 0$  and  $V_{in} = -2mV$ . 9

[Turn over


(b) In the circuit diagram  $V_{CC} = +15V$ ,  $V_{EE} = -15V$ ,  
 $R_C = 10\text{ k}\Omega$ ,  $R_E = 10\text{ k}\Omega$ ,  $R_B = 20\text{ k}\Omega$

(i) Determine output voltage if transistors  $Q_1$  and  $Q_2$  are identical with  $\beta_{dc} = 80$ .

(ii) Determine base current and base voltages.

(iii) Determine base current and base voltages if transistors  $Q_1$  and  $Q_2$  are identical except  $\beta_{dc}$ .  $Q_1$  has  $\beta_{dc} = 65$  and  $Q_2$  has  $\beta_{dc} = 85$ .

5

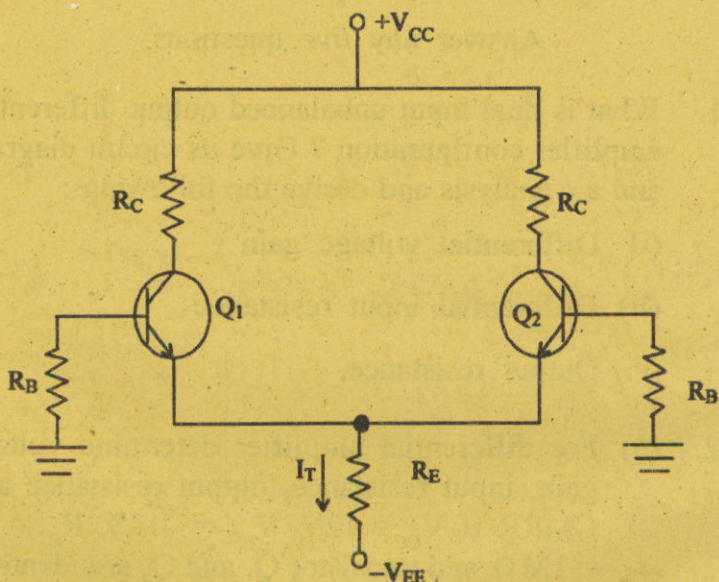



3. (a) Explain the functional block diagram of a typical three terminal IC voltage regulator. 5

(b) Define the following parameters for IC voltage regulator : 4

(i) Line regulation

(ii) Load regulation

(iii) Output resistance.

(iv) Dropout voltage.

(c) Design and draw a Zener regulator circuit to meet the following specification : 5

Load voltage = 6.8V, Input voltage = 25V,

Load current = 0 – 40 mA,  $I_{z\min} = 5\text{mA}$ ,

$P_z = 1$  watt.

4. (a) What is tuned amplifier ? Draw and explain the circuit diagrams of single tuned amplifier and its frequency response. 7

(b) The tuned amplifier with capacitive coupling having  $R = 10\ \Omega$ ,  $L = 20\ \text{mH}$  and  $C = 0.07\ \mu\text{F}$ . Determine :

(i) Resonant frequency

(ii) Q factor of the tank circuit

(iii) Bandwidth.

(c) Differentiate between active filters and passive filters. 4

5. (a) Explain the working of Wein bridge oscillator. Derive the frequency of oscillation and condition for oscillation. Also give the advantage. 3+4+1=8

(b) Explain the operation of full-wave precision rectifier with circuit diagram and give its waveform. 6

6. (a) Explain the working of an SCR giving its construction and V-I characteristics. 7

(b) Give the advantages of negative feedback. 3

(c) If the open-loop gain  $A_v = 10,000$  and feedback ratio  $\beta = \frac{1}{10}$ , then for a negative feedback, find the percentage change in closed loop gain when open loop gain varies 50% with temperature. 3

(d) Positive feedback is used in ..... 1



7. Write short notes on any *two* :  $7 \times 2 = 14$

- (i) Stagger tuned amplifier
- (ii) UJT
- (iii) Crystal oscillator
- (iv) Buck regulator
- (v) Adjustable power supply.

al  
n  
4

ge  
nd  
R<sub>E</sub>  
cal  
ge  
9