

Total No. of printed pages = 8

END SEMESTER EXAMINATION -2019

Semester : 5th

Subject Code : CAI-506

ELECTRONIC CIRCUITS AND DEVICES-II

Full Marks - 70

Time - Three hours

The figures in the margin indicate full marks for the questions.

Instructions :

1. Questions on PART-A are compulsory.
2. Answer any *five* questions from PART-B.

PART - A

Marks - 25

1. Fill in the blanks : 1×14=14

(a) A bipolar junction transistor has _____ PN junctions and _____ terminals.

(b) The quantity β is usually between _____ and _____.

[Turn over

- (c) The quantity β provides a relationship between _____ and _____.
- (d) In a symbol of transistor, the arrow sign indicates _____.
- (e) For amplification purpose, the transistor must operate in the _____ region of its output characteristics.
- (f) When a BJT goes into saturation, both emitter and collector base junctions are _____ biased.
- (g) For a transistor to operate as amplifier, the base emitter junction should be _____ biased.
- (h) $I_c = \alpha I_E + \text{_____}$.
- (i) An improper biased transistor produces _____ in the output.
- (j) The intersection of DC load line with the given base current curve is the _____.
- (k) Tuned amplifier used for _____.
- (l) Positive feedback is employed in _____.



- (m) Negative feedback in amplifiers reduces the gain but _____ bandwidth.
 - (n) A high Q coil has _____ selectivity.
2. Write true or false : 1×9=9
- (a) The resistivity of a semi-conductor depends on the atomic structure of the semi-conductor.
 - (b) The potential barrier in a PN junction increases with reverse bias and reduces with forward bias.
 - (c) A PN junction is forward bias if the N side is connected to the negative terminal of a battery and the P side is connected to the positive terminal.
 - (d) If a PN junction is heavily doped, breakdown voltage will be reduced.
 - (e) Zener diode operates in the reverse bias region.
 - (f) The voltage gain of a transistor increases with the increase in load resistance.
 - (g) A BJT fixed bias configuration has more temperature stability than voltage divider bias.

(h) The most commonly used transistor arrangement is common collector.

(i) I_{CO} of a transistor consist of majority carrier.

3 Choose the correct answer : $1 \times 2 = 2$

(a) A Schmitt trigger converts a slowly varying waveform into a

- (i) sinewave
- (ii) sawtooth wave

(iii) triangular wave (iv) square wave

(b) Oscillators used the following feedback :

- (i) Positive
- (ii) Negative

(iii) Both positive and negative

(iv) None of the above.

PART - B

Marks - 45

4. (a) Determine the expressions for I_B , I_C and V_{CE} for the following biasing circuits for a common emitter NPN transistor

- (i) Fixed bias.
- (ii) Emitter bias

6


46/CAI-506/EC&D-II (4)



(b) In a transistor Colpitt's oscillator, $L = 100 \mu H$, $C_1 = 0.001 \mu F$ and $C_2 = 0.05 \mu F$, determine the operating frequency of the circuit. 3

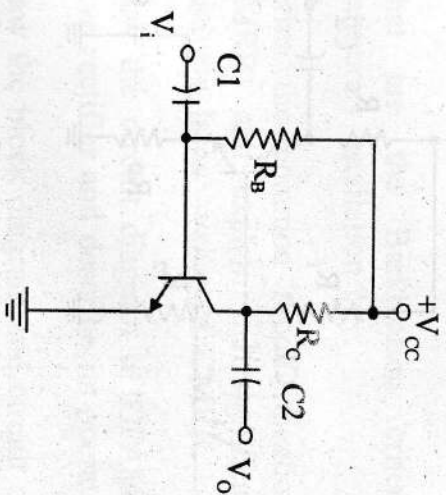5. (a) Deduce the expressions for input impedance, output impedance and voltage gain of the following circuit using r_e model of the transistor.

Calculate gain, when $R_B = 100 k\Omega$, $R_C = 1 k\Omega$, $r_o = 50 k\Omega$, $V_{CC} = 12V$ and $\beta = 100$. 6



(b) What are the advantages of negative feedback in amplifiers ? 3

6. (a) For the potential divider biasing circuit shown in the figure below, draw the h-parameter equivalent circuit. Also, calculate the following:


- (i) Input impedance

46/CAI-506/EC&D-II (5)

[Turn over

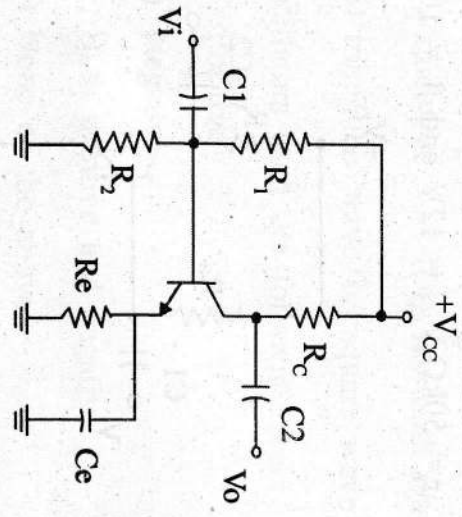- (ii) Output impedance
- (iii) Voltage gain
- (iv) Current gain

[Given : $R_1 = 10 \text{ K}\Omega$, $R_2 = 5 \text{ K}\Omega$, $R_c = 3 \text{ K}\Omega$, $R_E = 1 \text{ K}\Omega$, $V_{cc} = 20 \text{ V}$, $h_{fe} = 1 \text{ K}$, $h_{re} = 100$, $h_{oe} = 20 \mu\text{A/V}$, $h_{re} = 2 \times 10^{-4}$]



- (b) Draw the circuit of a voltage supply comprised of a full wave bridge rectifier, capacitor filter and IC regulator to provide an output of +12V. 3
- 7 Draw the ideal structure and equivalent circuit of series shunt feedback amplifier. Determine the expression for gain, input impedance and output impedance of the amplifier. 9



- 8. (a) Draw the circuit diagram of Colpitt's oscillator and describe its working. 5
- (b) Draw the circuit diagram of the following :
 - (i) Phase Shift Oscillator
 - (ii) Wein Bridge Oscillator

Also write the equation for operating frequency in each case. 4

- 9. (a) What are the Barkhausen criteria for continuous oscillation? 3
- (b) Define the common mode rejection ratio (CMRR) and explain the significance of relatively large value of CMRR. 3
- (c) Draw the circuit diagram of OPAMP half-wave rectifier and describe its operation. 3
- 10. (a) Draw the block diagram and circuit diagram of series voltage regulator. Describe the operation of the circuit in brief. 5
- (b) Describe the working of IC LM317 with a suitable diagram. 4
- 11. (a) Draw the equivalent circuit diagram of Crystal Oscillator and explain its working. 5

- (b) Draw the circuit diagram of a first order active low pass filter and derive the expression for gain. 4
12. (a) Draw the circuit diagram of a tuned amplifier and explain its working. 4
- (b) What are the advantages of using double tuned circuit as compared to the single tuned circuit ? 2
- (c) A tuned amplifier consists of a tank circuit having $R=10\Omega$, $L=50\text{ mH}$ and $C=0.1\ \mu\text{F}$. Determine resonant frequency of the amplifier, Q factor of the tank circuit and bandwidth of the amplifier. 3