

Total No. of printed pages = 8

**RETEST EXAMINATION-2022**

Semester : 5th

Subject Code : CAI-506

**ELECTRONIC CIRCUITS AND DEVICES-II**

Full Marks - 70

Time - Three hours

The figures in the margin indicate full marks  
for the questions.

**Instructions :**


- (i) All questions of PART-A are compulsory.
- (ii) Answer any *five* questions from PART-B.

**PART-A**

Marks-25

- 1 Fill in the blanks : 1×14=14
- (a) A bipolar junction transistor has \_\_\_\_\_ p-n junctions and \_\_\_\_\_ terminals .
  - (b) The quantity  $\square$  is usually between \_\_\_\_\_ and \_\_\_\_\_ .
  - (c) The quantity  $\square$  provides a relationship between \_\_\_\_\_ and \_\_\_\_\_ .

[Turn over

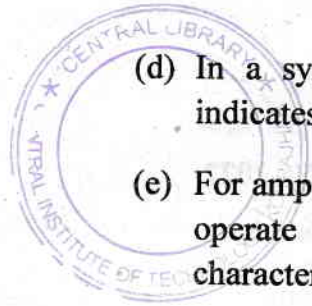

- (d) In a symbol of transistor, the arrow sign indicates \_\_\_\_\_.
- (e) For amplification purpose, the transistor must operate in the \_\_\_\_\_ region of its output characteristics.
- (f) When a BJT goes into saturation, both emitter and collector base junctions are \_\_\_\_\_ biased.
- (g) For a transistor to operate as amplifier, the base emitter junction should be \_\_\_\_\_ biased.
- (h)  $I_C = \alpha I_E + \text{_____}$ .
- (i) An improper biased transistor produces \_\_\_\_\_ in the output.
- (j) The intersection of DC load line with the given base current curve is the \_\_\_\_\_.
- (k) Tuned amplifier used for \_\_\_\_\_.
- (l) Positive feedback is employed in \_\_\_\_\_.
- (m) Negative feedback in amplifiers reduces the gain but \_\_\_\_\_ bandwidth.
- (n) A high Q coil has \_\_\_\_\_ selectivity.

2 Write true or false :  $1 \times 9 = 9$

- (a) The resistivity of a semiconductor depends on the atomic structure of the semiconductor.
- (b) The potential barrier in a p-n junction increases with reverse bias and reduces with forward bias.
- (c) A p-n junction is forward bias if the n side is connected to the negative terminal of a battery and the p-side is connected to the positive terminal.
- (d) If a p-n junction is heavily doped, breakdown voltage will be reduce.
- (e) Zener diode operates in the reverse bias region.
- (f) The voltage gain of a transistor increases with the increase in load resistance.
- (g) A BJT fixed bias configuration has more temperature stability than voltage divider bias.
- (h) The most commonly used transistor arrangement is common collector.
- (i)  $I_{CO}$  of a transistor consists of majority carrier.

3. Choose the correct answers :  $1 \times 2 = 2$

(a) A Schmitt trigger converts a slowly varying waveform into a

(i) sinewave (ii) sawtooth wave

(iii) triangular wave (iv) square wave

(b) Oscillators used following feedback

(i) Positive

(ii) Negative

(iii) Both positive and negative

(iv) None of the above.



**PART - B**

Marks - 45

4. (a) Determine the expressions for  $I_B$ ,  $I_C$  and  $V_{CE}$  for the following biasing circuits for a common emitter NPN transistor :


(i) Fixed Bias (ii) Emitter Bias. 6

(b) In a transistor Colpitt's oscillator,  $L = 100 \mu\text{H}$ ,  $C_1 = 0.001 \mu\text{F}$  and  $C_2 = 0.05 \mu\text{F}$ , determine the operating frequency of the circuit. 3

105/CAI-506/EC&D-II (4)

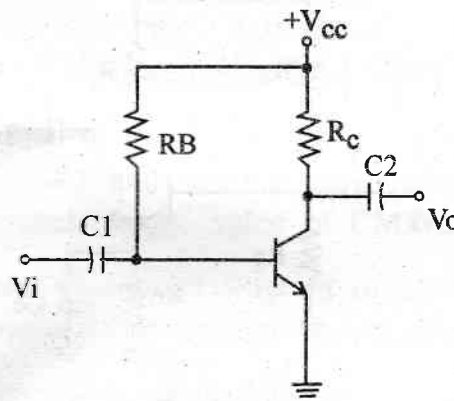5. (a) Deduce the expressions for input impedance, output impedance and voltage gain of the following circuit using  $r_e$  model of the transistor.

Calculate gain, when  $R_B = 100\text{k}\Omega$ ,  $R_C = 1\text{k}\Omega$ ,  $r_o = 50\text{k}\Omega$ ,  $V_{CC} = 12\text{V}$  and  $\beta = 100$ . 6




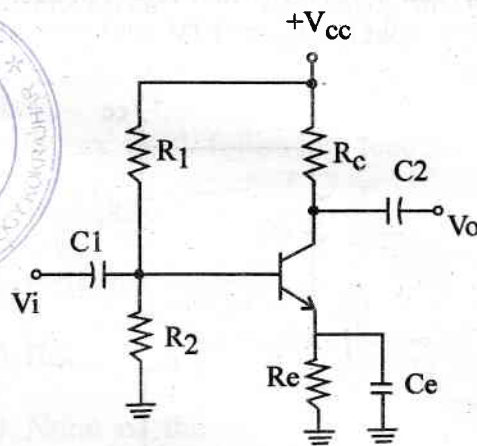- (b) What are the advantages of negative feedback in amplifiers? 3
6. (a) For the potential divider biasing circuit shown in the figure below, draw the h-parameter equivalent circuit. Also, calculate the following :
- (i) Input impedance
  - (ii) Output impedance
  - (iii) Voltage gain
  - (iv) Current gain

105/CAI-506/EC&D-II (5)



[Given :  $R_1 = 10 \text{ K}\Omega$ ,  $R_2 = 5 \text{ K}\Omega$ ,  $R_c = 3 \text{ K}\Omega$ ,  
 $R_E = 1 \text{ K}\Omega$ ,  $V_{cc} = 20 \text{ V}$ ,  $h_{ie} = 1 \text{ K}\Omega$ ,  $h_{fe} = 100$ ,  
 $h_{oe} = 20 \mu\text{A/V}$ ,  $h_{re} = 2 \times 10^{-4}$ ] 6



- (b) Draw the circuit of a voltage supply comprised of a full wave bridge rectifier, capacitor filter and IC regulator to provide an output of +12V. 3
7. Draw the ideal structure and equivalent circuit of series shunt feedback amplifier. Determine the expression for gain, input impedance and output impedance of the amplifier. 9
8. (a) Draw the circuit diagram of Colpitt's oscillator and describe its working. 5

- (b) Draw the circuit diagram of the following :
- (i) Phase Shift Oscillator
  - (ii) Wein Bridge Oscillator
- Also write the equation for operating frequency in each case. 4
9. (a) What are the Barkhausen criteria for continuous oscillation? 3
- (b) Define the common mode rejection ratio (CMRR) and explain the significance of relatively large value of CMRR. 3
- (c) Draw the circuit diagram of OPAMP half-wave rectifier and describe its operation. 3
10. (a) Draw the block diagram and circuit diagram of series voltage regulator. Describe the operation of the circuit in brief. 5
- (b) Describe the working of IC LM317 with a suitable diagram. 4
11. (a) Draw the equivalent circuit diagram of Crystal Oscillator and explain its working. 5
- (b) Draw the circuit diagram of a first order active low pass filter and derive the expression for gain. 4



12. (a) Draw the circuit diagram of a tuned amplifier and explain its working. 4
- (b) What are the advantages of using double tuned circuit as compared to the single tuned circuit? 2
- (c) A tuned amplifier consists of a tank circuit having  $R=10\Omega$ ,  $L=50\text{ mH}$  and  $C=0.1\mu\text{F}$ . Determine resonant frequency of the amplifier, Q factor of the tank circuit and bandwidth of the amplifier. 3

